

# EECS/CSE 70A Network Analysis I

## Homework #4 Solution Key

Problem 1: (Ideal Opamp) Find currents  $i_1$ ,  $i_2$ ,  $i_3$  and the output voltage  $v_o$  (30pts.)

### Problem 1 Solution

In ideal opamp, no current flows into -/+ terminals, and the voltages at those terminals are equal

$$i_1 = \frac{V_- - 12V}{40\Omega}, \quad i_2 = \frac{V_- - 2V}{30\Omega}, \quad i_3 = \frac{V_- - (-6V)}{15\Omega}$$


KCL at - terminal

$$\frac{V_- - 12V}{40\Omega} + \frac{V_- - 2V}{30\Omega} + \frac{V_- - (-6V)}{15\Omega} + \frac{V_- - v_o}{10\Omega} = 0$$

$$27V_- + 4 = 12v_o$$

Using  $V_- = V_+ = 0V$

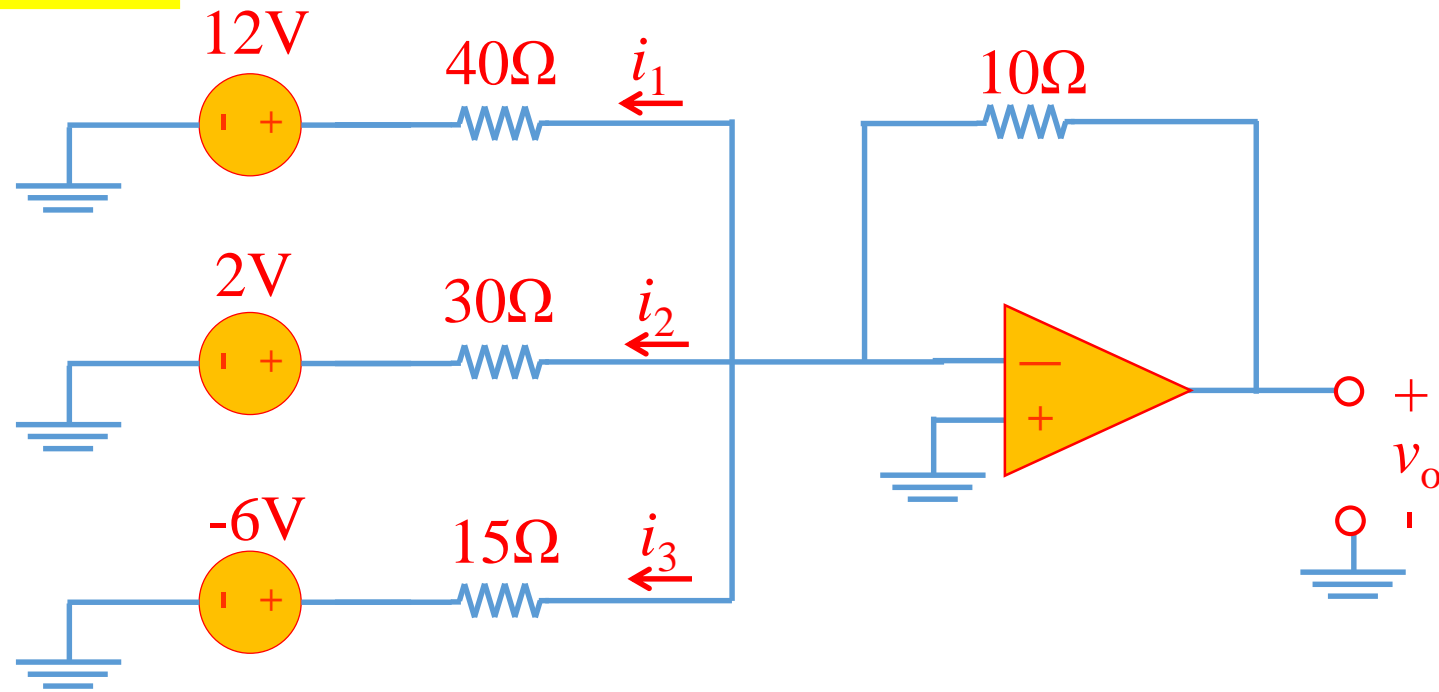
$$v_o = \frac{1}{3}V, \quad i_1 = \frac{-12V}{40\Omega} = -0.3A, \quad i_2 = \frac{-2V}{30\Omega} = -0.066A, \quad i_3 = \frac{6V}{15\Omega} = 0.4A$$




Problem 2: (RC circuit) Write the expression for the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state voltage across the  $3\mu\text{F}$  capacitor (35pts.)
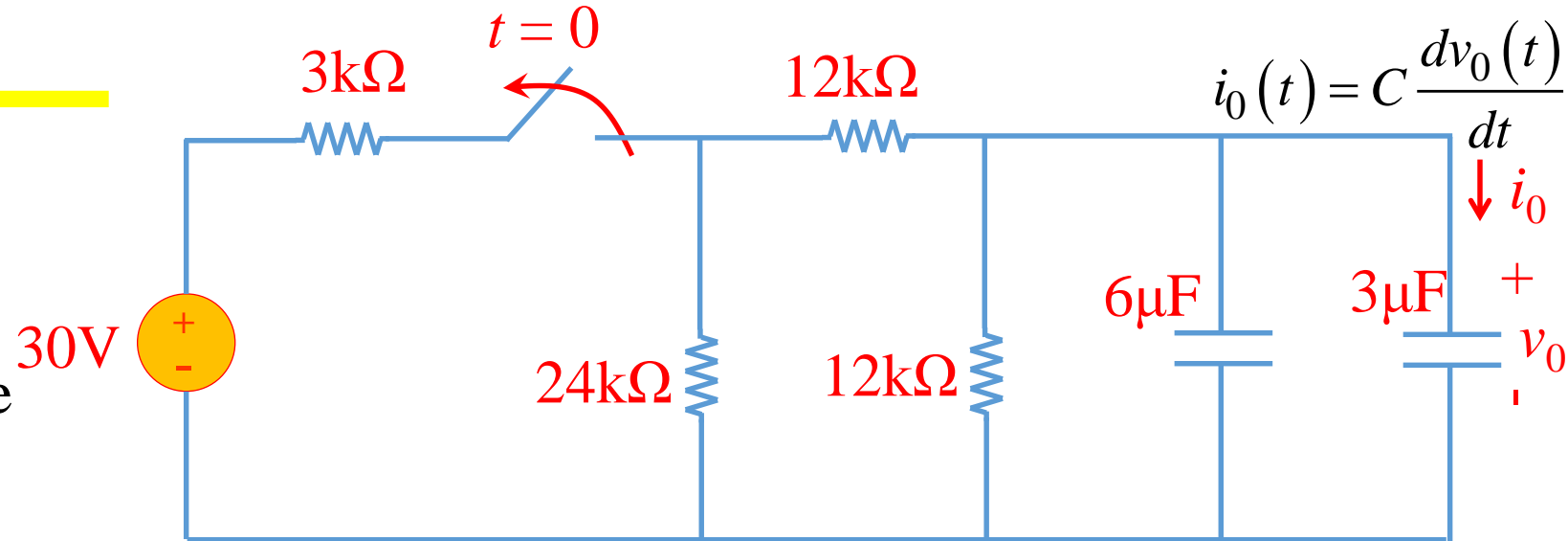
### Problem 2 Solution

The capacitors are in parallel, the voltage across them is equal, we can use the equivalent capacitance of  $9\mu\text{F}$  in the following steps



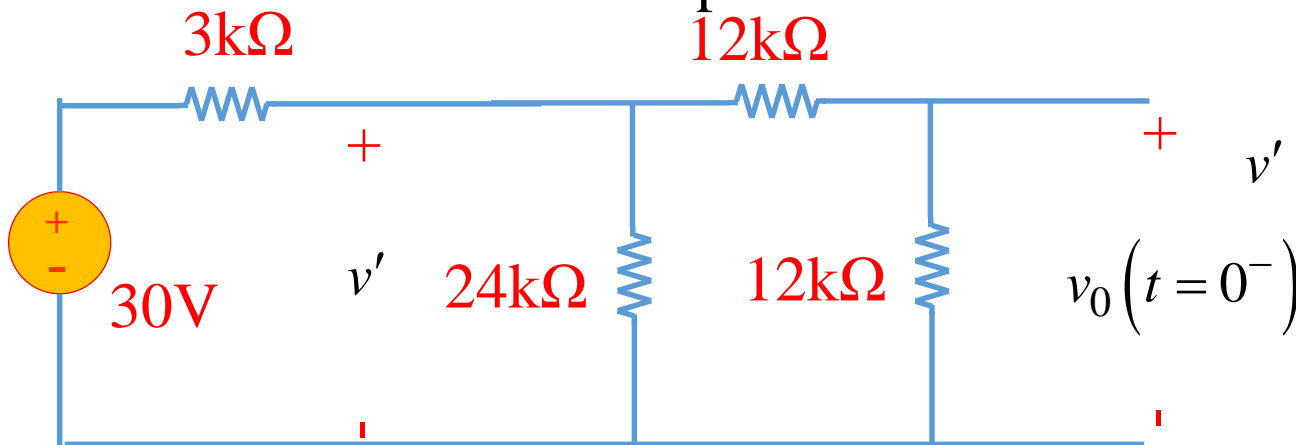@  $t = 0^-$  The capacitors act as open circuit since the circuit was in steady state before the switch is opened. All the time derivatives are zero  $\frac{d}{dt}(\cdot) \rightarrow 0$   $i_0(t = 0^-) = 0$




$$v' = 30\text{V} \frac{(12\text{k}\Omega + 12\text{k}\Omega) \parallel 24\text{k}\Omega}{[(12\text{k}\Omega + 12\text{k}\Omega) \parallel 24\text{k}\Omega] + 3\text{k}\Omega} = 30 \frac{12}{15} = 24\text{V}$$

$$v_0(t = 0^-) = \frac{v'}{2} = 12\text{V}$$


Problem 2: (RC circuit) Write the expression for the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state voltage across the  $3\mu\text{F}$  capacitor (35pts.)

### Problem 2 Solution (cont'd)

$t > 0$

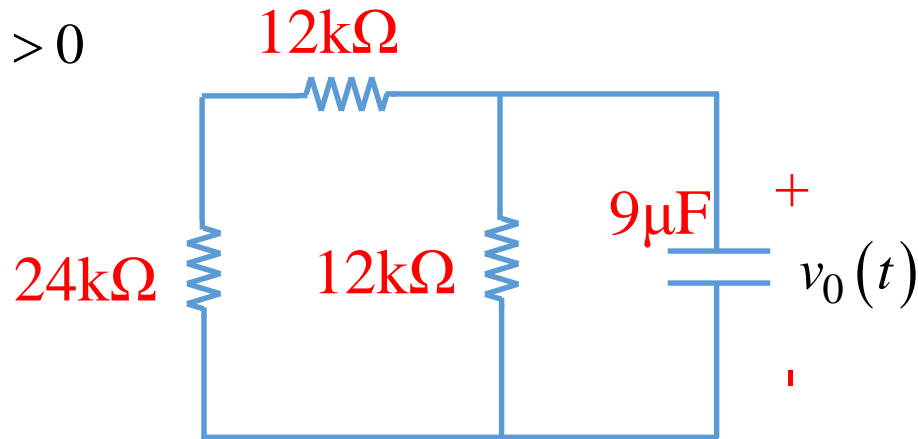
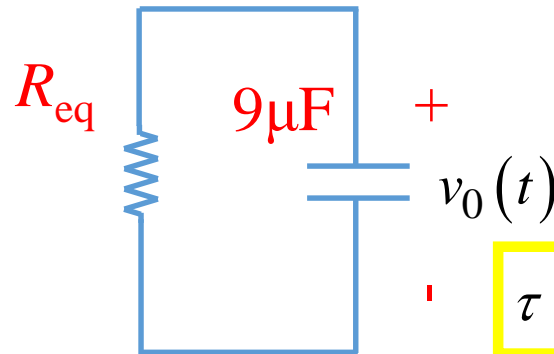
$$R_{\text{eq}} = (12\text{k}\Omega + 24\text{k}\Omega) \parallel 12\text{k}\Omega = 9\text{k}\Omega$$



The capacitors discharges in source free setup with the time constant

$$\tau = R_{\text{eq}} C = (9 \times 10^3 \Omega)(9 \times 10^{-6} \text{F}) = 81\text{ms}$$

$t \rightarrow \infty$  The current through capacitor vanishes, and the voltage decays towards zero  $v_0(\infty) = 0\text{V}$



$$\begin{aligned} v_0(t) &= v_0(\infty) + [v_0(0) - v_0(\infty)] e^{-t/\tau} \\ &= 12e^{-t/(81 \times 10^{-3})} \text{V} = 12e^{-12.35t} \text{V} \end{aligned} \quad t > 0$$

Problem 3: (RL circuit) Write the expressions for the current  $i_0$  and the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state current through the inductor. (35pts.)
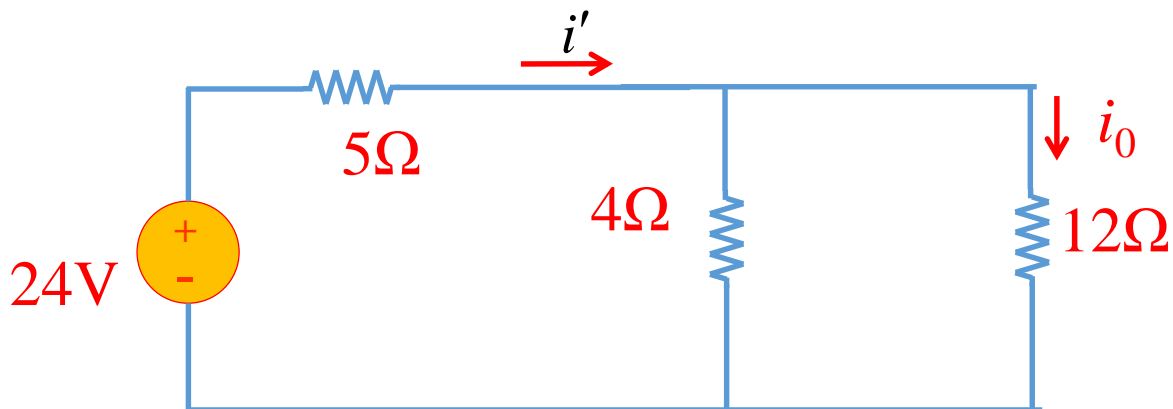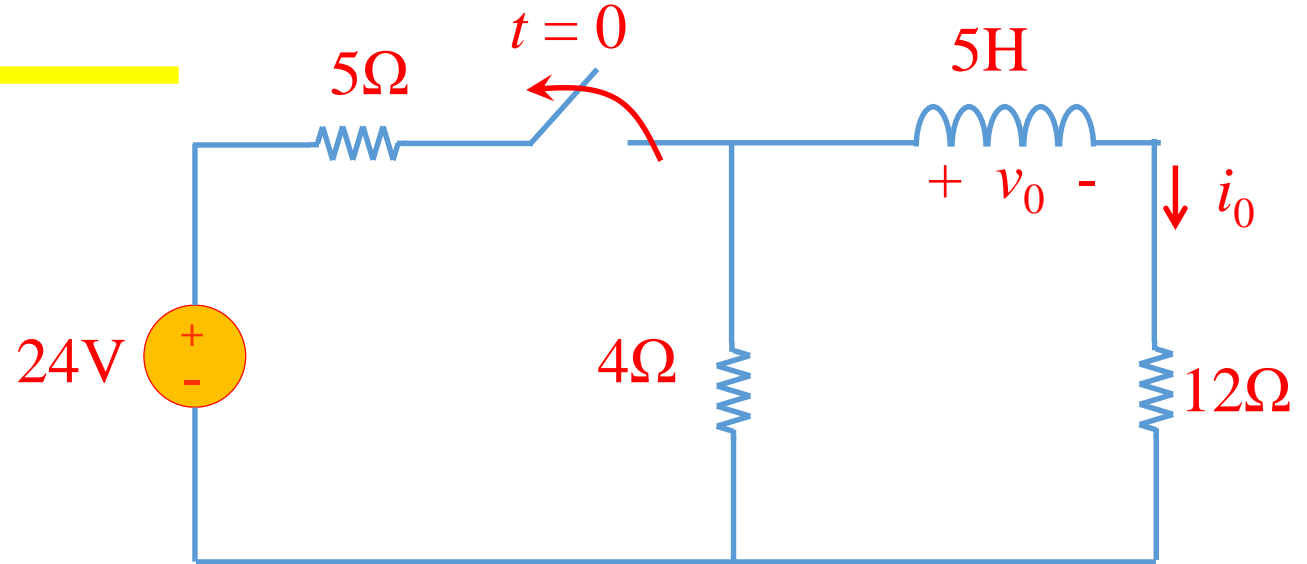
### Problem 3 Solution

@  $t = 0^-$  The inductor acts as short circuit since all the time derivatives are zero  $\frac{d}{dt}(\cdot) \rightarrow 0$

$$v_0(t) = L \frac{di_0(t)}{dt} \quad v_0(t = 0^-) = 0V$$



$$i' = \frac{24V}{(12\Omega \parallel 4\Omega) + 5\Omega} = \frac{24}{8} = 3A$$

$$i_0(t = 0^-) = i' \frac{(12\Omega \parallel 4\Omega)}{12\Omega} = i' \frac{3}{12} = \frac{3}{4} A$$



Problem 3: (RL circuit) Write the expressions for the current  $i_0$  and the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state current through the inductor. (35pts.)

### Problem 3 Solution (cont'd)

$t > 0$

5H
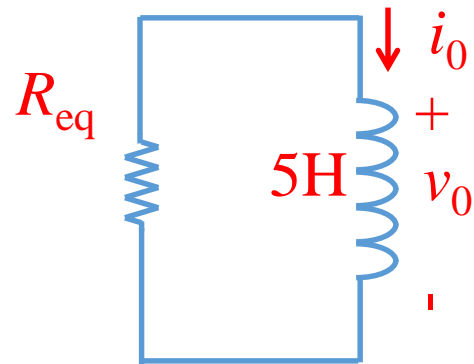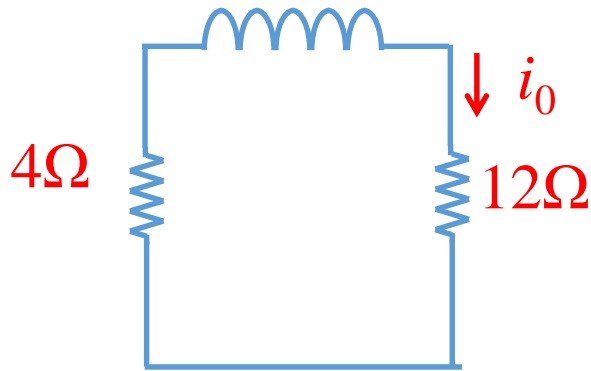
$$R_{eq} = 4\Omega + 12\Omega = 16\Omega$$



The stored energy in the inductor discharges through the resistor in absence of a source.

The time constant is

$$\tau = \frac{L}{R_{eq}} = \frac{5\text{H}}{16\Omega} = 0.3125\text{s}$$

$t \rightarrow \infty$  The voltage across the inductor vanishes, and the current decays towards zero  $i_0(\infty) = 0\text{A}$

$$\begin{aligned} i_0(t) &= i_0(\infty) + [i_0(0) - i_0(\infty)]e^{-t/\tau} \\ &= \frac{3}{4}e^{-t/0.3125}\text{A} = 0.75e^{-3.2t}\text{A} \quad t > 0 \end{aligned}$$

$$\begin{aligned} v_0(t) &= L \frac{di_0(t)}{dt} = -\frac{1}{\tau} Li_0(t) \\ &= -12e^{-t/0.3125}\text{A} = -12e^{-3.2t}\text{A} \quad t > 0 \end{aligned}$$