
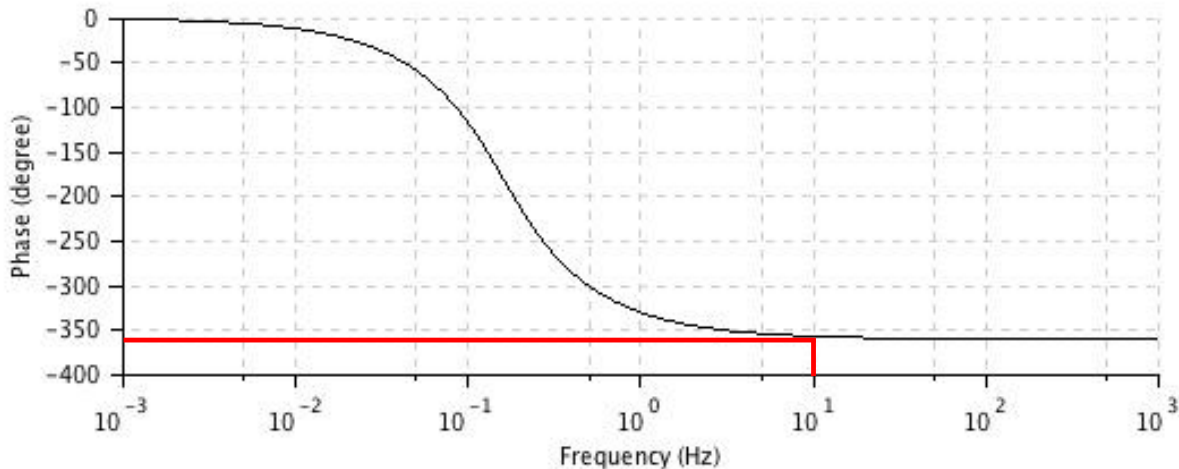


# EECS/CSE 70A Network Analysis I

## Homework #6 Solution Key
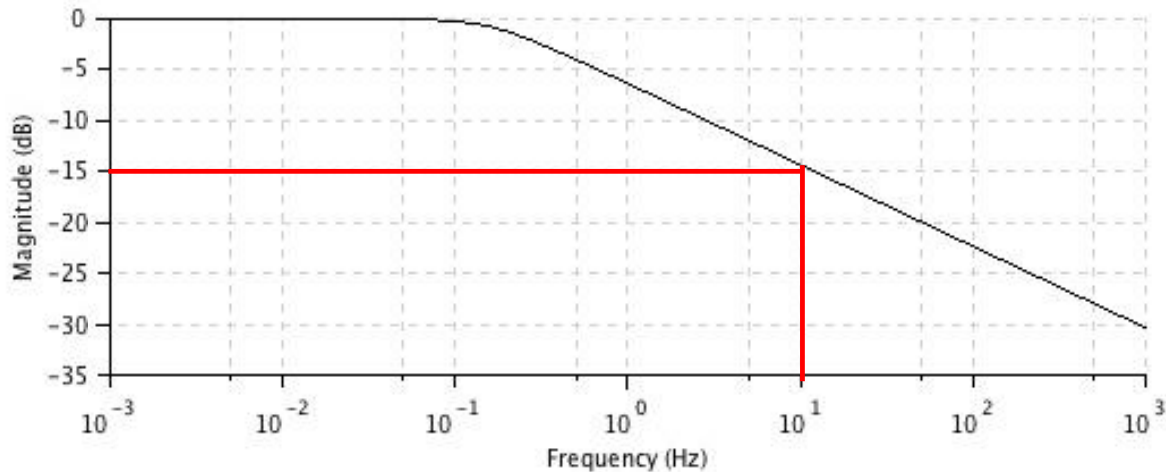
## Problem 1 (30pts.)

The Bode plots show the magnitude and phase of the transfer function of a circuit. The input voltage  $v_{in}(t) = 1 \text{ mV} \cos([2\pi \cdot 10\text{Hz}]t)$ . Find the output voltage  $v_{out}(t)$ .



$$v_{in} \Rightarrow V_{in} = 1 \text{ mV}$$

to phasor

$$V_{out} = H(\omega = 2\pi \cdot 10\text{Hz})V_{in}$$

From the graphs :

$$|H(\omega = 2\pi \cdot 10\text{Hz})|_{\text{dB}} = -15\text{dB},$$

$$|H(\omega = 2\pi \cdot 10\text{Hz})| = 10^{-15/20} \approx 0.18$$

$$\arg[H(\omega = 2\pi \cdot 10\text{Hz})] = -360^\circ = 0^\circ \equiv 0 \text{ rad}$$

$$H(\omega = 2\pi \cdot 10\text{Hz}) \approx 0.18e^{j0} = 0.18$$


$$V_{out} = 0.18 \text{ mV} \Rightarrow v_{out}(t) = \text{Re}\left\{V_{out}e^{j(2\pi \cdot 10)t}\right\}$$

$$v_{out}(t) = 0.18 \cos([2\pi \cdot 10\text{Hz}]t) \text{ mV}$$

## Problem 2 (35pts.)

Find the transfer function  $H(\omega)$  in terms of  $R_1$ ,  $R_2$ ,  $L_1$  and  $L_2$ . And simplify  $|H(\omega)|$  at  $\omega = 0$  and as  $\omega \rightarrow \infty$ .

$$H(\omega) = \frac{V_o}{V_s}$$

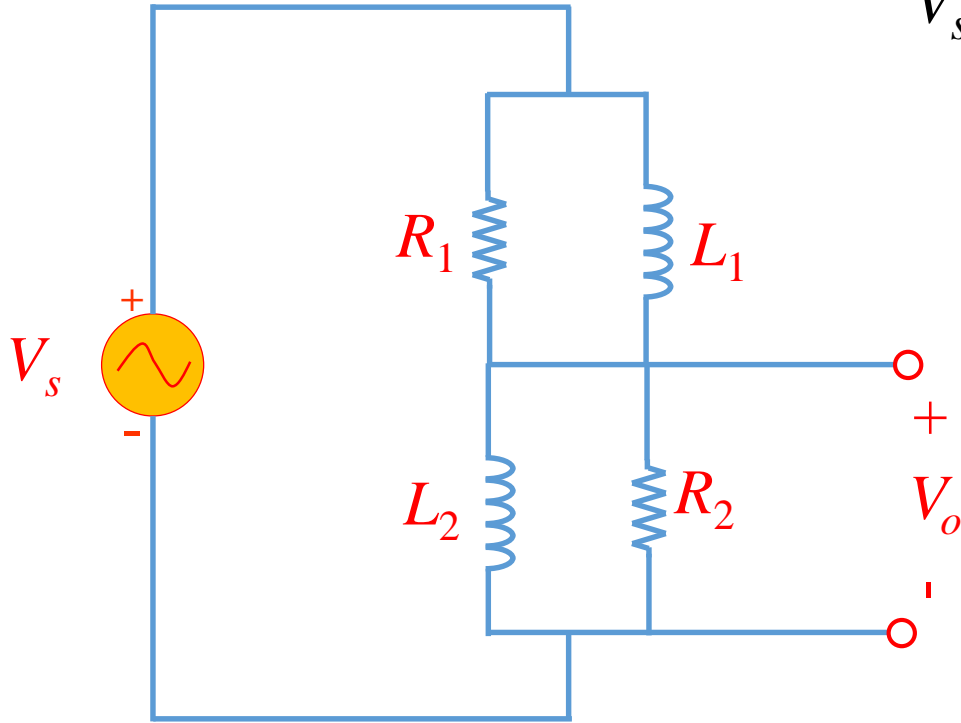

By voltage division

$$V_o = V_s \frac{R_2 \parallel j\omega L_2}{(R_1 \parallel j\omega L_1) + (R_2 \parallel j\omega L_2)}$$

$$\begin{aligned} H(\omega) &= \frac{R_2 \parallel j\omega L_2}{(R_1 \parallel j\omega L_1) + (R_2 \parallel j\omega L_2)} \\ &= \frac{\frac{j\omega L_2 R_2}{R_2 + j\omega L_2}}{\frac{j\omega L_1 R_1}{R_1 + j\omega L_1} + \frac{j\omega L_2 R_2}{R_2 + j\omega L_2}} = \frac{\frac{L_2 R_2}{R_2 + j\omega L_2}}{\frac{L_1 R_1}{R_1 + j\omega L_1} + \frac{L_2 R_2}{R_2 + j\omega L_2}} \end{aligned}$$

Problem 2 (35pts.) cont'd

$$|H(\omega = 0)| = \left| \frac{\frac{L_2 R_2}{R_2 + j0L_2}}{\frac{L_1 R_1}{R_1 + j0L_1} + \frac{L_2 R_2}{R_2 + j0L_2}} \right| = \left| \frac{\frac{L_2 R_2}{R_2}}{\frac{L_1 R_1}{R_1} + \frac{L_2 R_2}{R_2}} \right| = \boxed{\frac{L_2}{L_1 + L_2}}$$

Let us make an algebraic manipulation as

$$H(\omega) = \frac{\frac{\frac{1}{j\omega} L_2 R_2}{\frac{1}{j\omega} (R_2 + j\omega L_2)}}{\frac{\frac{1}{j\omega} L_1 R_1}{\frac{1}{j\omega} (R_1 + j\omega L_1)} + \frac{\frac{1}{j\omega} L_2 R_2}{\frac{1}{j\omega} (R_2 + j\omega L_2)}} = \frac{\frac{L_2 R_2}{\frac{R_2}{j\omega} + L_2}}{\frac{L_1 R_1}{\frac{R_1}{j\omega} + L_1} + \frac{L_2 R_2}{\frac{R_2}{j\omega} + L_2}}$$

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = \left| \frac{\frac{L_2 R_2}{0 + L_2}}{\frac{L_1 R_1}{0 + L_1} + \frac{L_2 R_2}{0 + L_2}} \right| = \boxed{\frac{R_2}{R_1 + R_2}}$$


The answers are expected since the inductors approach to: (i) short circuit, i.e. lowest impedance path, as the frequency decreases; and (ii) open circuit as frequency increases.

### Problem 3 (35pts.)

Find the transfer function  $H(\omega)$  in terms of  $R_1$ ,  $R_2$ ,  $C_1$  and  $C_2$ . And simplify  $|H(\omega)|$  at  $\omega = 0$  and as  $\omega \rightarrow \infty$ .

$$H(\omega) = \frac{V_o}{V_s}$$

Similarly as in Problem 2

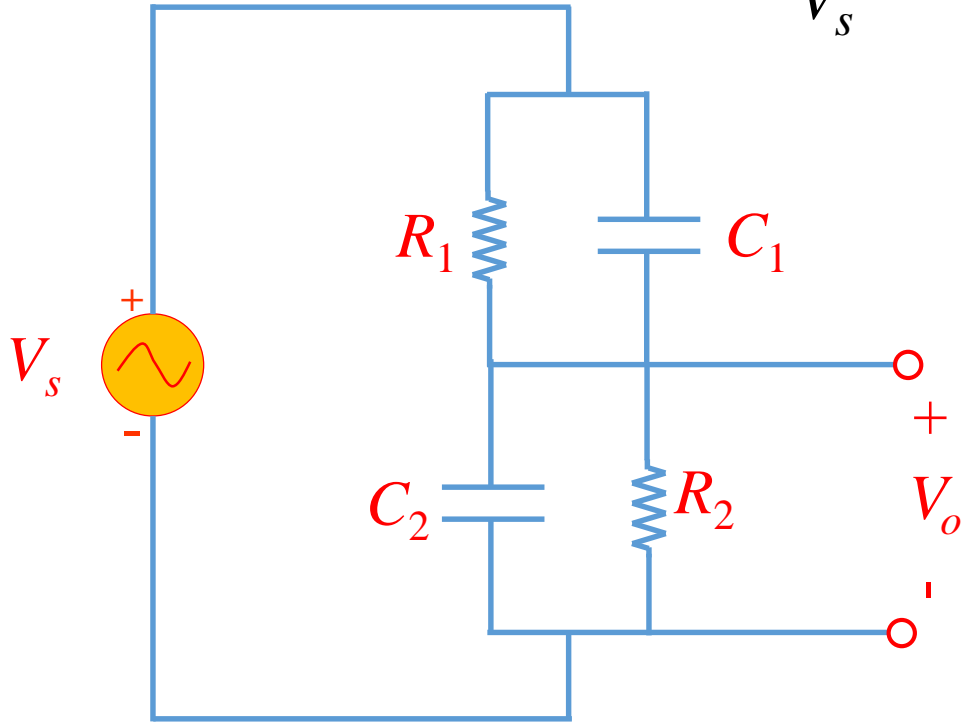

$$\begin{aligned}
 H(\omega) &= \frac{R_2 \parallel \frac{1}{j\omega C_2}}{\left( R_1 \parallel \frac{1}{j\omega C_1} \right) + \left( R_2 \parallel \frac{1}{j\omega C_2} \right)} \\
 &= \frac{\frac{R_2}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_2}{j\omega C_2} + \frac{R_1}{R_1 + \frac{1}{j\omega C_1}}} = \frac{R_2}{1 + j\omega C_2 R_2} \cdot \frac{R_1 + \frac{1}{j\omega C_1}}{R_2 + \frac{1}{j\omega C_2}} \\
 &= \frac{R_2}{1 + j\omega C_2 R_2} \cdot \frac{R_1 + \frac{1}{j\omega C_1}}{R_2 + \frac{1}{j\omega C_2}}
 \end{aligned}$$

Problem 3 (35pts.) cont'd

$$|H(\omega = 0)| = \left| \frac{\frac{R_2}{1 + j0C_2R_2}}{\frac{R_1}{1 + j0C_1R_1} + \frac{R_2}{1 + j0C_2R_2}} \right| = \frac{R_2}{R_1 + R_2}$$

Let us make an algebraic manipulation as

$$H(\omega) = \frac{\frac{\frac{1}{j\omega} R_2}{\frac{1}{j\omega} (1 + j\omega C_2 R_2)}}{\frac{\frac{1}{j\omega} R_1}{\frac{1}{j\omega} (1 + j\omega C_1 R_1)} + \frac{\frac{1}{j\omega} R_2}{\frac{1}{j\omega} (1 + j\omega C_2 R_2)}} = \frac{\frac{R_2}{\frac{1}{j\omega} + C_2 R_2}}{\frac{R_1}{\frac{1}{j\omega} + C_1 R_1} + \frac{R_2}{\frac{1}{j\omega} + C_2 R_2}}$$

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = \left| \frac{\frac{R_2}{0 + C_2 R_2}}{\frac{R_1}{0 + C_1 R_1} + \frac{R_2}{0 + C_2 R_2}} \right| = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

The answers are expected since the capacitors approach to: (i) open circuit as frequency decreases; and (ii) short circuit, i.e. lowest impedance path, as the frequency increases.