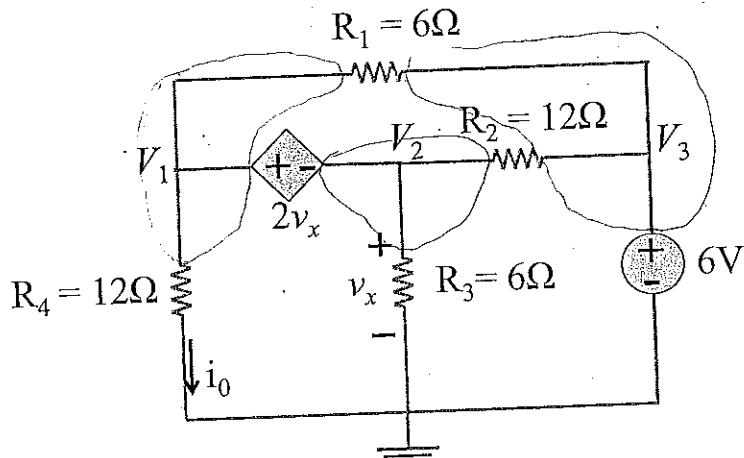


**PROBLEM 2: (20 points)**

Use nodal analysis, and solve for the node voltages and the current  $i_0$ .

use KCL



V <sub>1</sub>	1V
V <sub>2</sub>	3V
V <sub>3</sub>	6V
i <sub>0</sub>	1/2A

-17

$$\text{KCL @ node 1: } \frac{V_1 - 0V}{12\Omega} + \frac{V_1 - V_2}{2V_x} + \frac{V_1 - V_3}{6\Omega} = 0 \quad (1)$$

$$\text{KCL @ node 2: } \frac{V_2 - V_1}{2V_x} + \frac{V_2}{6\Omega} + \frac{V_2 - V_3}{12\Omega} = 0 \quad (2)$$

$$\text{KCL @ node 3: } V_3 = 6V \quad (3) \quad ; \quad V_x = \frac{V_2}{6\Omega} \quad * \quad i_0 = \frac{V_1}{12\Omega} = \frac{1V}{12\Omega}$$

Rearrange equations:

$$\frac{V_1}{12\Omega} + \frac{V_1}{2V_x} + \frac{V_1}{6\Omega} - \frac{V_2}{2V_x} - \frac{V_3}{6\Omega} = 0$$

$$\frac{V_1}{12\Omega} + \frac{V_1}{12\Omega} - \frac{V_2}{12\Omega} + \frac{V_1}{6\Omega} - \frac{V_3}{6\Omega} = 0$$

$$\frac{V_2}{2V_x} + \frac{V_2}{6\Omega} + \frac{V_2}{12\Omega} - \frac{V_3}{12\Omega} = 0$$

$$\frac{V_2}{2V_x} + \frac{3V_2}{12\Omega} - \frac{V_3}{12\Omega} = 0$$

$$\frac{V_2}{2(\frac{V_2}{6\Omega})} + \frac{3V_2}{12\Omega} = \frac{1}{2}A$$

$$\frac{V_2}{2V_x} + \frac{3V_2}{12\Omega} = \frac{1}{2}A$$

$$\frac{6\Omega V_2}{2V_x} + \frac{3V_2}{12\Omega} = \frac{1}{2}A$$

$$\frac{6\Omega}{V_2} + \frac{3V_2}{12\Omega} = \frac{1}{2}A$$


$$\frac{3V_2}{12\Omega} = \left( \frac{1}{2}A - \frac{6\Omega}{V_2} \right) \frac{12\Omega}{V_2}$$

$$3V_2 = 6V - \frac{72\Omega}{V_2}$$

Below average  
Score

~80  
~25

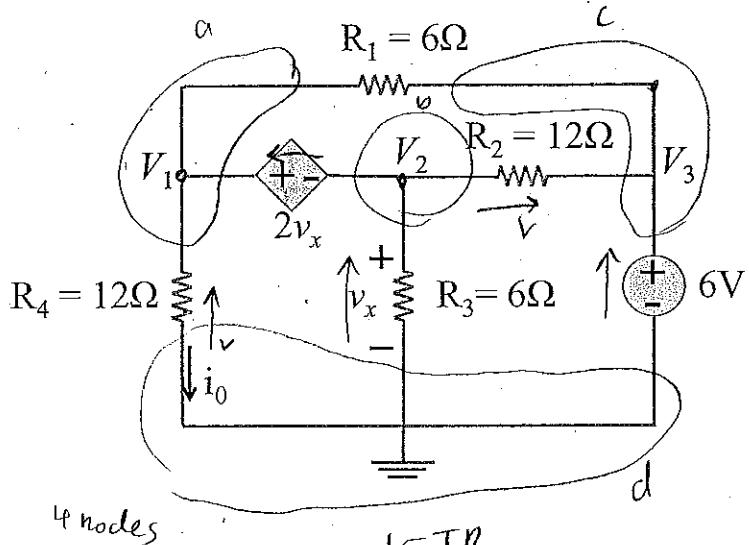Use nodal analysis, and solve for the node voltages and the current  $i_0$ .



$V_1$	66 V
$V_2$	$3 - 14V_x$
$V_3$	$-2V_x + 30$ V
$i_0$	5 Amp

4 nodes

$$V = IR$$

$$V_{in} = V_{out}$$

$$I_{in} = I_{out}$$

$$\text{node a: } \frac{V_1 - V_3}{R_1} = [2V_x] + \frac{(V_1 - 6V)}{R_4} \Rightarrow \frac{V_1 - V_3}{6\Omega} = 2V_x + \frac{(V_1 - 6V)}{12\Omega}$$

$$V_2 = V_3 - 12V_x$$

$$\text{node b: } \frac{V_2 - V_3}{R_2} + 2V_x = V_x \Rightarrow \frac{V_2 - V_3}{12\Omega} + 2V_x = V_x \Rightarrow \frac{V_2 - V_3}{12\Omega} = -V_x \Rightarrow V_2 - V_3 = -12V_x$$

$$\text{node c: } \frac{V_3 - V_1}{R_1} = \frac{V_3 - V_2}{R_2} + 6 \Rightarrow \frac{V_3 - V_1}{6} = \frac{V_3 - V_2}{12} + 6 \Rightarrow V_3 - V_1 = \frac{V_3 - V_2}{2} + 36$$

$$V_3 - V_1 = \frac{V_3}{2} - \frac{V_2}{2} + 36$$

$$2V_3 - 2V_1 = V_3 - V_2 + 72$$

$$V_1 - V_3 = 2V_x + \frac{(V_1 - 6V)}{2}$$

$$V_1 - V_3 = 2V_x + \frac{V_1}{2} + \frac{6V}{2}$$

$$\frac{V_1 - 6V}{12} = i_0$$

$$V_3 - 2(2V_x + 4V_x + 6) = -V_3 + 12V_x + 72$$

$$V_3 - 4V_3 + 8V_x + 12V_x = -V_3 + 12V_x + 72$$

$$V_2 - V_3 = 2V_x + 3$$

$$\frac{66 - 6}{12} = \frac{60}{12} = 5 \text{ Amp}$$

$$-2V_3 = 4V_x - 60$$

$$V_3 = -2V_x + 30$$

Below average sound  
≈ 20


$$V_1 = -4V_x + 60 + 4V_x + 6$$

$$V_1 = 66$$

$$V_1 = -2V_x + 3 - 12V_x$$

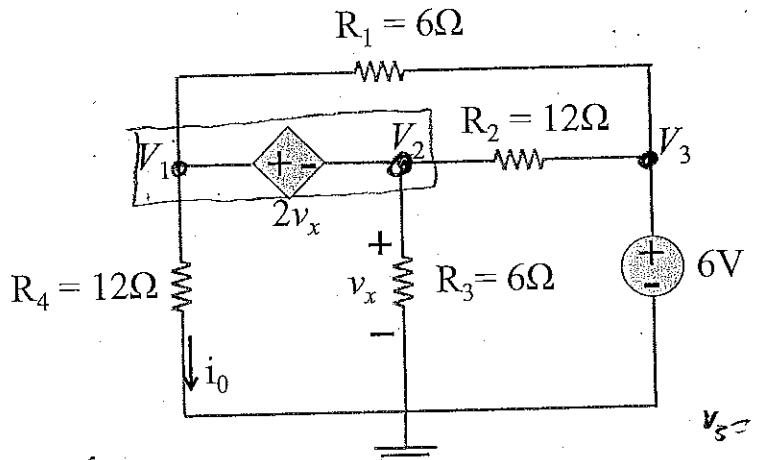1.2

Use nodal analysis, and solve for the node voltages and the current  $i_0$ .



V <sub>1</sub>	4V
V <sub>2</sub>	10V
V <sub>3</sub>	6V
i <sub>0</sub>	1A

$$\begin{array}{c} 6 \\ 1 \\ 3 \\ \hline 10 \\ 6 \end{array}$$

✓ + 2

KCL at N<sub>3</sub>:  $\frac{v_3 - v_2}{12} + \frac{v_3 - v_1}{6} = 0 \quad \text{Plug } v_3 = 6 \Rightarrow \frac{6 - v_2}{12} + \frac{6 - v_1}{6} = 0 \Rightarrow \frac{1}{2} - \frac{v_2}{12} + 1 - \frac{v_1}{6} = 0 \Rightarrow \frac{v_2}{12} + \frac{v_1}{6} = 1.5$

KCL at N<sub>1</sub>:  $\frac{v_1 - v_3}{6} + \frac{v_1}{12} + \frac{v_2 - v_3}{12} + \frac{v_2}{6} = 0 \Rightarrow v_2 + 2v_1 = 18$

Plug  $v_3 = 6 \Rightarrow \frac{v_1 - 6}{6} + \frac{v_1}{12} + \frac{v_2 - 6}{12} + \frac{v_2}{6} = 0$

$$\Rightarrow \frac{v_1}{6} - 1 + \frac{v_1}{12} + \frac{v_2}{12} - \frac{1}{2} + \frac{v_2}{6} = 0$$

$$\Rightarrow \frac{2v_1}{12} + \frac{v_1}{12} + \frac{v_2}{12} + \frac{2v_2}{12} = 1.5$$

$$\Rightarrow \frac{3v_1}{12} + \frac{3v_2}{12} = 1.5$$

$$\Rightarrow 3v_1 + 3v_2 = 18 \quad (+4)$$

$$\begin{cases} 3v_1 + 3v_2 = 18 \\ -v_1 + v_2 = 8 \\ -6v_1 - 3v_2 = -54 \end{cases}$$

$$-7v_1 = -36$$

$$v_1 = 4V, v_2 = 10V$$


$$V = IR + 2$$

$$I_0 = \frac{V_1}{R_4} = \frac{4V}{12\Omega} = \underline{\frac{1}{3}A}$$

Average since  $\times 55$

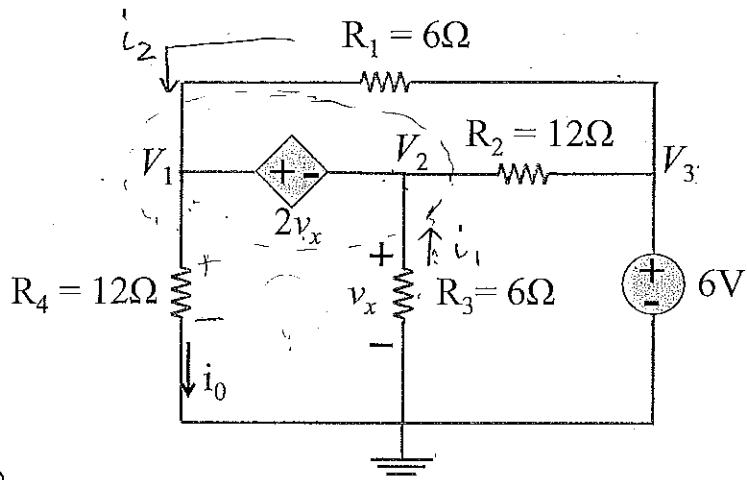**PROBLEM 2: (20 points)**

Use nodal analysis, and solve for the node voltages and the current  $i_0$ .



V <sub>1</sub>	4 V
V <sub>2</sub>	$\frac{4}{3}$ V
V <sub>3</sub>	6 V
i <sub>0</sub>	$\frac{1}{3}$ A

KCL @ Supernode +2  
 $i_0 = i_1 + i_2$

$$\frac{i_1}{2} = \left( \frac{v_x - v_2}{6} \right) + \left( \frac{v_3 - v_1}{6} \right) = 0 \quad \text{multiply by } 12$$

$v_3 = 6 \text{ V}$        $v_1 = 2v_x - 2v_2 + 2v_3 - 2v_1$

$$v_1 = 2\left(\frac{v_1}{3}\right) - 2\left(\frac{v_1}{3}\right) + 2(6) - 2v_1$$

$$v_1 = \cancel{\frac{2v_1}{3}} - \cancel{\frac{2v_1}{3}} + 12 - 2v_1$$

$$v_1 = 12 - 2v_1$$

$$3v_1 = 12$$

$$v_1 = 4$$

$$i = 2v_x - 2v_2 + 2v_3 - 2v_1$$


$$= 2\left(\frac{4}{3}\right) - 2v_2 + 12 - 8$$

$$= \frac{8}{3} - 2v_2 + 4$$

$$0 = \frac{8}{3} - 2v_2$$

$$-\frac{8}{3} = -2v_2$$

KVL Supernode

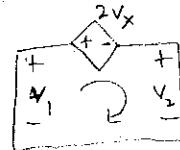

$$-V_1 + 2V_x + V_2 = 0 + 2$$

$$-(12i_0) + 2V_x + V_x = 0$$

$$-V_1 + 2V_x + V_x = 0$$

$$3V_x = V_1$$

$$V_x = \frac{V_1}{3}$$

$$-V_1 + 2\left(\frac{V_1}{3}\right) + V_2 = 0$$


$$-V_1 + \frac{2V_1}{3} + V_2 = 0$$

$$-\frac{V_1}{3} + V_2 = 0$$

$$V_2 = \frac{V_1}{3}$$

Average Score

255

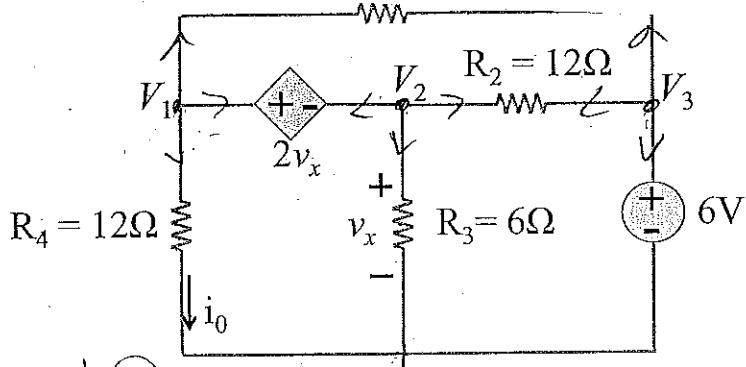

V <sub>1</sub>	
V <sub>2</sub>	
V <sub>3</sub>	
i <sub>0</sub>	

where  $\frac{V_1}{12\Omega} = 1 \text{ } \textcircled{2}$

②

① V<sub>1</sub>:  $i_0 + \frac{V_1 - V_3}{6\Omega} = 0$


② V<sub>2</sub>:  $\frac{V_2}{6\Omega} + \frac{V_2 - V_3}{12\Omega} = 0$

③ V<sub>3</sub>:  $\frac{V_3 - V_2}{12\Omega} + \frac{V_3 - V_1}{6\Omega} = 0$

19

V<sub>2</sub> = ?

Below average Score  
~ 30/100

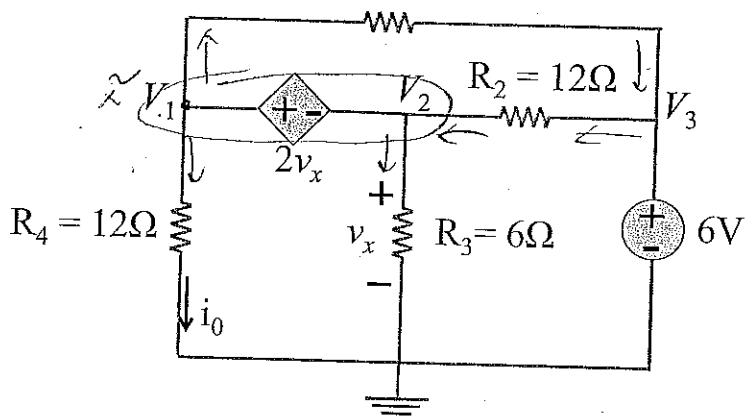

$V_1$	$\frac{24}{7} V$
$V_2$	$\frac{18}{7} V$
$V_3$	$6 V$
$i_0$	$\frac{2}{7} A$

12

$$\text{node 1 and 2: } \frac{V_1}{12} + \frac{V_1 - V_3}{6} + \frac{V_2}{6} = \frac{V_3 - V_2}{12}$$

$$V_1 + 2V_1 - 2V_3 + 2V_2 = V_3 - V_2$$

$$\text{node 3: } V_3 = 6 V$$

$$3V_1 + 3V_2 - 3V_3 = 0 \quad \times 3$$

$$V_1 + V_2 - V_3 = 0 \quad \checkmark$$

$$V_2 + 2V_x = V_1 \times 2$$

$$V_x = \frac{V_2}{6}$$

$$V_2 + \frac{V_2}{3} = V_1$$

$$\frac{4V_2}{3} = V_1$$

$$i_0 = \frac{V_1}{12} = \frac{24}{7} \times \frac{1}{12} A = \frac{2}{7} A$$

$$V_1 + V_2 - V_3 = 0$$

$$\frac{4}{3}V_2 + V_2 = 6$$

$$\frac{7}{3}V_2 = 6$$

$$V_2 = \frac{3 \times 6}{7} V = \frac{18}{7} V$$

$$V_1 = \frac{4}{3}V_2 = \frac{4}{3} \times \frac{18}{7} = \frac{24}{7} V$$

Well above average score.

~70/100