

Q1	Q2	Q3	Q4	Q5	Total
/20	/20	/20	/20	/20	/100

EECS / CSE 70A Midterm Exam #1

SOLUTION KEY


DO NOT BEGIN THE EXAM UNTIL YOU ARE TOLD TO DO SO.

Print your name on all pages.

Write your solutions in clear steps with concise explanations.

PROBLEM 1: (20 points)

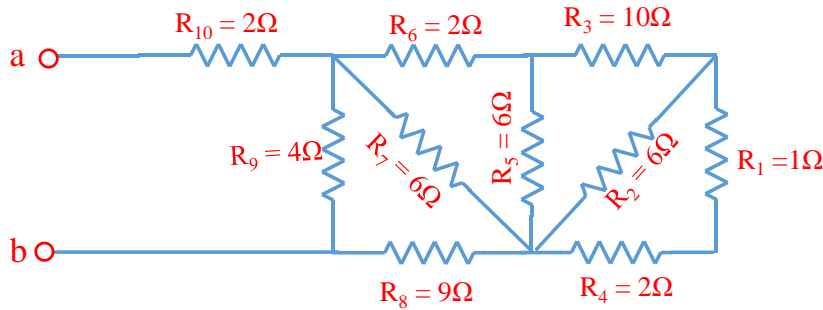
(a) Solve for the equivalent resistance, R_{eq} , across terminals a-b.



R_{eq}	5Ω
----------	-----------


$$\begin{aligned}
 R_{eq} &= \{([([(R_1 + R_4) \parallel R_2] + R_3) \parallel R_5] + R_6) \parallel R_7] + R_8) \parallel R_9\} + R_{10} \\
 &= \{([([(1\Omega + 2\Omega) \parallel 6\Omega] + 10\Omega) \parallel 6\Omega] + 2\Omega) \parallel 6\Omega] + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= \{([([(3\Omega \parallel 6\Omega] + 10\Omega) \parallel 6\Omega] + 2\Omega) \parallel 6\Omega] + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= \{([([(2\Omega + 10\Omega) \parallel 6\Omega] + 2\Omega) \parallel 6\Omega] + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= \{([([(12\Omega \parallel 6\Omega] + 2\Omega) \parallel 6\Omega] + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= \{([[(4\Omega + 2\Omega) \parallel 6\Omega] + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= \{(3\Omega + 9\Omega) \parallel 4\Omega\} + 2\Omega \\
 &= 5\Omega
 \end{aligned}$$

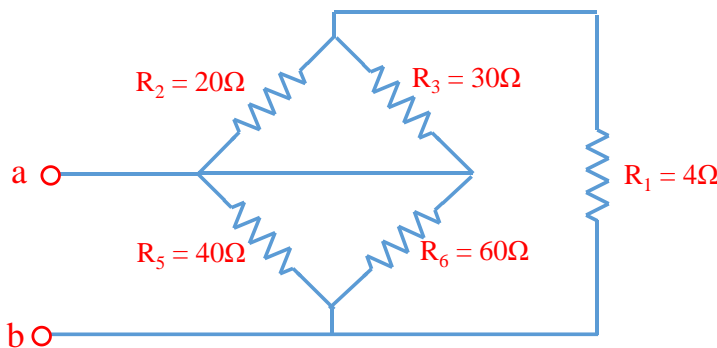(b) Solve for the equivalent resistance, R_{eq} , across terminals a-b.



R_{eq}	9.6Ω
----------	-------------

$$\begin{aligned}
 R_{eq} &= \{[(R_2 \parallel R_3) + R_1] \parallel (R_5 \parallel R_6)\} \\
 &= \{[(20\Omega \parallel 30\Omega) + 4\Omega] \parallel (40\Omega \parallel 60\Omega)\} \\
 &= \{[12\Omega + 4\Omega] \parallel 24\Omega\} \\
 &= 16\Omega \parallel 24\Omega \\
 &= 9.6\Omega
 \end{aligned}$$

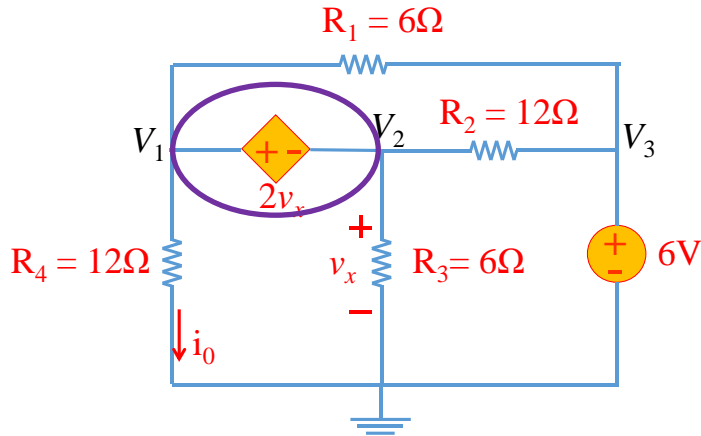PROBLEM 2: (20 points)Use nodal analysis, and solve for the node voltages and the current i_0 .

V_1	4.5V
V_2	1.5V
V_3	6V
i_0	0.375A

Due to the VSCV, KCL in nodes 1 and 2 can not be written in terms of node voltages. We need to use a supernode:

$$\text{KCL at supernode: } \frac{V_1 - 0\text{V}}{R_4} + \frac{V_1 - V_3}{R_1} + \frac{V_2 - 0\text{V}}{R_3} + \frac{V_2 - V_3}{R_2} = 0 \quad (1)$$

$$\text{Node 3 set by voltage source: } V_3 = 6\text{V} \quad (2)$$

Substitute (2) and (3) in (1):

$$\frac{V_1 - 0\text{V}}{12\Omega} + \frac{V_1 - 6\text{V}}{6\Omega} + \frac{V_2 - 0\text{V}}{6\Omega} + \frac{V_2 - 6\text{V}}{12\Omega} = 0 \rightarrow V_1 + V_2 = 6 \quad (3)$$

$$\text{Voltage source controlled by voltage: } V_1 - V_2 = 2v_x, \text{ also } V_2 = v_x, \text{ as a result } V_1 = 3V_2 \quad (4)$$


Substitute (4) in (3):

$$4V_2 = 6\text{V}, \text{ so } V_2 = 1.5\text{V} \text{ and } V_1 = 4.5\text{V}$$

$$\text{Also the current } i_0 = \frac{V_1 - 0\text{V}}{R_4} = \frac{4.5\text{V} - 0\text{V}}{12\Omega} = 0.375\text{A}$$

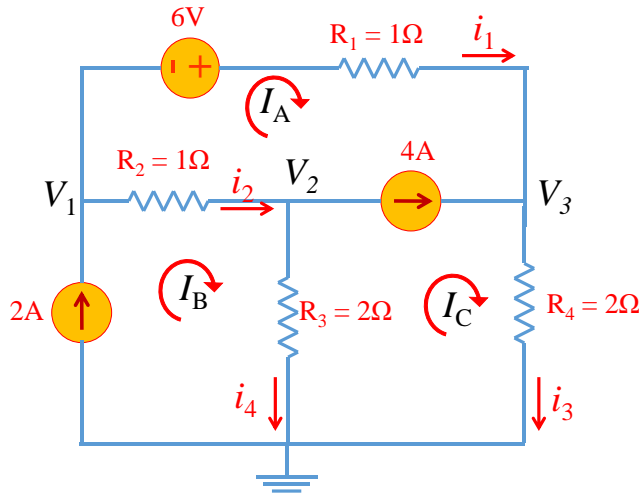PROBLEM 3: (20 points)

Use mesh analysis, and solve for the mesh currents and the labeled voltages.



I_A	-0.67 A
I_B	2 A
I_C	3.3 A
i_1	-0.67 A
i_2	2.67 A
i_3	3.3 A
i_4	-1.3 A
V_1	0 V
V_2	-2.6 V
V_3	6.6 V

The current of mesh B, I_B set by the current source: $I_B = 2\text{ A}$

Due to the 4A current source, KVL in meshes A and C can not be written in terms of mesh currents. We need to use a supermesh:

$$-6\text{ V} + R_1 \cdot I_A + R_4 \cdot I_C + R_3 \cdot (I_C - I_B) + R_2 \cdot (I_A - I_B) = 0$$

Substitute the resistors value and the I_B :

$$-6\text{ V} + 1\Omega \cdot I_A + 2\Omega \cdot I_C + 2\Omega \cdot (I_C - 2\text{ A}) + 1\Omega \cdot (I_A - 2\text{ A}) = 0$$

$$\text{So } 2I_A + 4I_C = 12 \quad (1)$$

$$\text{Also, based on the 4A current source: } I_C - I_A = 4 \quad (2)$$

$$\text{By solving (1) and (2), we reach: } I_A = \frac{-2}{3}\text{ A} = -0.67\text{ A} \text{ and } I_C = \frac{10}{3}\text{ A} = 3.3\text{ A}$$

$$\text{Also, } i_1 = I_A = -0.67\text{ A}, \quad i_2 = I_B - I_A = 2.67\text{ A}$$

$$i_3 = I_C = 3.3\text{ A}, \quad i_4 = I_B - I_C = -1.3\text{ A}$$


$$V_2 = R_3 \cdot i_4 = 2\Omega \cdot (-1.3\text{ A}) = -2.6\text{ V}$$

$$V_3 = R_4 \cdot i_3 = 2\Omega \cdot (3.3\text{ A}) = 6.6\text{ V}$$

$$V_1 - V_2 = R_2 \cdot i_2 = 1\Omega \cdot (2.67\text{ A}) \rightarrow V_1 = 0\text{ V}$$

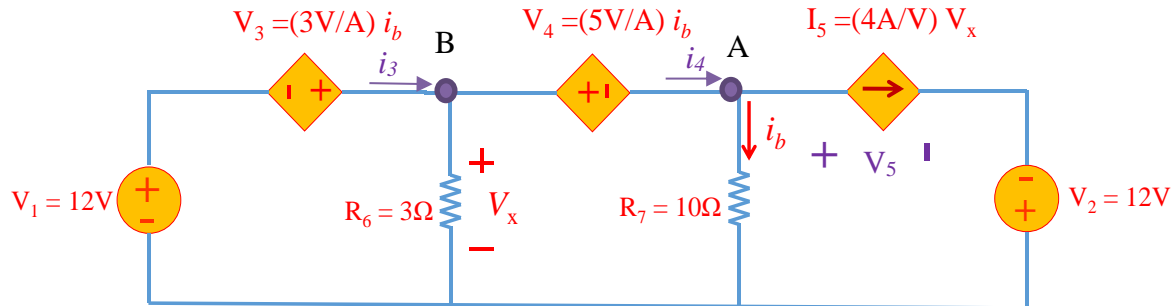PROBLEM 4: (20 points)

Find the absorbed or supplied power by each dependent source and indicate if it is source or sink.



$$\text{KVL in the left mesh: } -V_1 - V_3 + V_x = 0, \quad \text{So } V_x - 3i_b = 12 \quad (1)$$

$$\text{KVL in the middle mesh: } -V_x + V_4 + R_7 \cdot i_b = 0, \quad \text{So } -V_x + 15i_b = 0 \quad (2)$$

By solving (1) and (2), we reach $i_b = 1\text{ A}$ and $V_x = 15\text{ V}$

To find the powered absorbed/supplied by elements 3, 4 and 5, we need to calculate

i_3, V_3, i_4, V_4, I_5 and V_5 . To calculate the currents, we need to write the KCL at nodes A and B.

$$\text{KCL at node A: } i_4 = i_b + I_5 = 1\text{ A} + (4\text{ A/V}) \cdot 15\text{ V} = 61\text{ A}$$

$$\text{KCL at node B: } i_3 = \frac{V_x}{R_6} + i_4 = \frac{15\text{ V}}{3\Omega} + 61\text{ A} = 66\text{ A}$$

To calculate V_5 , we write the KVL in the right mesh: $V_5 - V_2 - R_7 \cdot i_b = 0$, so

$$V_5 = 12\text{ V} + 10\Omega \cdot 1\text{ A} = 22\text{ V}$$

Absorbed power by element 3: $P_3 = -i_3 \cdot V_3 = -66\text{ A} \cdot (3\text{ V/A})1\text{ A} = -198\text{ W}$, so element 3 is power source.


Absorbed power by element 4: $P_4 = i_4 \cdot V_4 = 61\text{ A} \cdot (5\text{ V/A})1\text{ A} = 305\text{ W}$, so element 4 is power sink.

Absorbed power by element 5: $P_5 = I_5 \cdot V_5 = (4\text{ A/V})15\text{ V} \cdot 22\text{ V} = 1320\text{ W}$, so element 5 is power sink.

element	Power	Type (sink/source)
3	-198W	source
4	305W	sink
5	1320W	sink

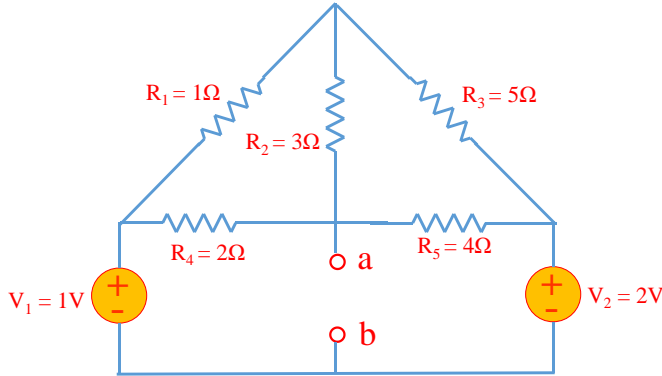PROBLEM 5: (20 points)


Obtain the Thévenin and Norton equivalent network representations as seen from the terminals a-b. (Please draw the equivalent network representations and annotate the source voltages or currents and resistances)



V_{Th}	1.29 V
R_{Th}	0.98Ω
i_{No}	1.3A
R_{No}	0.98Ω

One needs to solve two of the following, since the third can be found by the previous two parameters: V_{Th} , i_{No} , $R_{Th}=R_{No}$ where $V_{Th} = i_{No}R_{Th}$

Open-circuit voltage at a-b terminals:

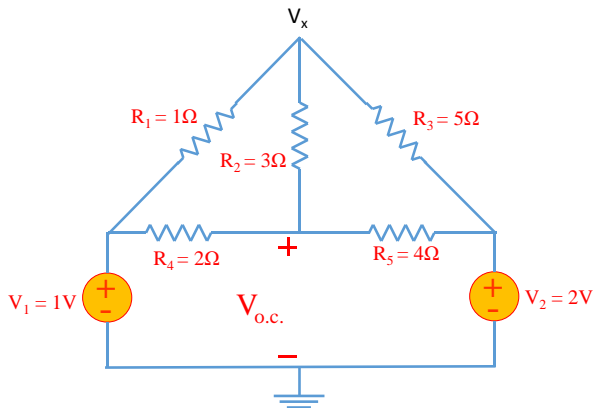

let us write KCL at the node "a" in terms of V_x

$$\frac{V_{o.c.} - V_x}{R_2} + \frac{V_{o.c.} - V_1}{R_4} + \frac{V_{o.c.} - V_2}{R_5} = 0$$

$$\text{So } \frac{V_{o.c.} - V_x}{3\Omega} + \frac{V_{o.c.} - 1V}{2\Omega} + \frac{V_{o.c.} - 2V}{4\Omega} = 0$$

As a result the first equation would be:

$$13V_{o.c.} - 4V_x = 12 \quad (1)$$

Also, KCL at the top node:


$$\frac{V_x - V_{o.c.}}{R_2} + \frac{V_x - V_1}{R_1} + \frac{V_x - V_2}{R_3} = 0$$

$$\text{So } \frac{V_x - V_{o.c.}}{3\Omega} + \frac{V_x - 1V}{1\Omega} + \frac{V_x - 2V}{5\Omega} = 0, \text{ as a result the second equation would be:}$$

$$-5V_{o.c.} + 23V_x = 21 \quad (2)$$

By solving (1) and (2), we reach $V_x = 1.193V$ and $V_{o.c.} = 1.29 V$. So $V_{Th} = V_{o.c.} = 1.29 V$

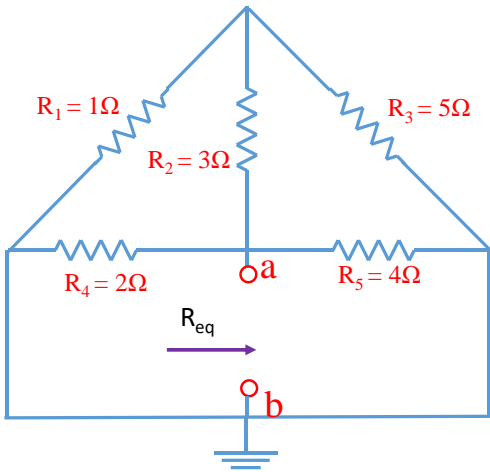To calculate the R_{Th} , we kill the independent voltage sources and find the equivalent resistance from a-b terminal:



$$\begin{aligned}
 R_{Th} = R_{eq} &= [(R_1 \parallel R_3) + R_2] \parallel (R_4 \parallel R_5) \\
 &= [(1\Omega \parallel 5\Omega) + 3\Omega] \parallel (2\Omega \parallel 4\Omega) \\
 &= \left[\frac{5}{6}\Omega + 3\Omega\right] \parallel \left(\frac{8}{6}\Omega\right) = \frac{92}{93}\Omega = 0.98\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{No} = R_{Th} &= \frac{92}{93}\Omega = 0.98\Omega \\
 i_{No} &= V_{Th}/R_{Th} = 1.3A
 \end{aligned}$$

Finally we have:

