

## EECS / CSE 70A MIDTERM #1

### GRADING RUBRIC

#### Problem 1.

a.

| Step   | Points    |
|--|-----------|
| Recognizing series combination $R_1+R_4 = 3 \Omega$                  | 1         |
| Recognizing parallel combination $3\Omega \parallel R_2 = 2 \Omega$  | 1         |
| Recognizing series combination $R_3+2 \Omega = 12 \Omega$            | 1         |
| Recognizing parallel combination $12\Omega \parallel R_5 = 4 \Omega$ | 1         |
| Recognizing series combination $R_6+4 \Omega = 6 \Omega$             | 1         |
| Recognizing parallel combination $6\Omega \parallel R_7 = 3 \Omega$  | 1         |
| Recognizing series combination $3\Omega + R_8 = 12\Omega$            | 1         |
| Recognizing parallel combination $12\Omega \parallel R_9=3\Omega$    | 1         |
| Recognizing series combination $3\Omega + R_{10} = 5\Omega$          | 1         |
| Final answer = $5\Omega$   | 1         |
| <b>Total</b>   | <b>10</b> |

b.

| Step  | Points    |
|---|-----------|
| Recognizing parallel combinations $R_2 \parallel R_3$   | 2         |
| Application of the parallel resistors formula in step 1<br>$(20\Omega \parallel 30\Omega) = 12\Omega$ | 1         |
| Recognizing series combination of $R_1+12\Omega = 16\Omega$   | 1         |
| Recognizing parallel combination of $R_5 \parallel R_6$   | 2         |
| Application of the parallel resistors formula in step 3<br>$(40\Omega \parallel 60\Omega) = 24\Omega$ | 1         |
| Recognizing parallel combination of $16\Omega \parallel 24\Omega$                                     | 2         |
| Final answer = $9.6\Omega$  | 1         |
| <b>Total</b>  | <b>10</b> |

**Problem 2.**

| Step   | Points    |
|--|-----------|
| Recognizing using supernode for Node 1 and Node 2              | 2         |
| Recognizing that Node 3 voltage is set by the voltage source   | 1         |
| Writing the expressions for KCL at supernode ( $V_1+V_2 = 6$ ) | 4         |
| Writing the expression for dependent voltage source            | 2         |
| Writing the expression for $V_2$ versus $V_x$                  | 1         |
| Finding the second equation for $V_1$ and $V_2$                | 2         |
| Writing the expression for $i_0$                               | 2         |
| Final Answers (Should be filled in the table)                  |           |
| $V_1 = 4.5V$   | 2         |
| $V_2 = 1.5V$   | 2         |
| $V_3 = 6V$   | 1         |
| $i_0 = 0.375A$   | 1         |
| <b>Total</b>   | <b>20</b> |

**Problem 3.**

| Step   | Points    |
|--|-----------|
| Recognizing the current $I_B$ is set by the current source         | 1         |
| Recognizing using supermesh for A&C                                | 1         |
| KVL Loop equation for Supermesh                                    | 4         |
| Writing the expression for $I_A$ and $I_C$ based on current source | 2         |
| Final Answers  |           |
| $I_A = -2/3 A$   | 2         |
| $I_B = 2 A$  | 1         |
| $I_C = 10/3A$  | 2         |
| $i_1 = I_A = -2/3A$  | 1         |
| $i_2 = I_B - I_A = 8/3A$   | 1         |
| $i_3 = I_C = 10/3A$  | 1         |
| $i_4 = I_B - I_C = -4/3A$  | 1         |
| $V_1 = V_2 + R_2 i_2 = 0 V$  | 1         |
| $V_2 = R_3 i_4 = -2.6V$  | 1         |
| $V_3 = R_4 i_3 = 6.6V$   | 1         |
| <b>Total</b>   | <b>20</b> |

**Problem 4.****Method 1:**

| Step   | Points    |
|--|-----------|
| Writing the KVL in the left mesh                       | 2         |
| Writing the KVL in the middle mesh                     | 2         |
| Finding the values of $i_b$ and $V_x$                  | 2         |
| Calculating $i_4$ by writing the KCL at node A         | 2         |
| Calculating $i_3$ by writing the KCL at node B         | 2         |
| Calculating $V_5$ by writing the KVL in the right mesh | 1         |
| Finding the value of $P_3$ & the type                  | 2&1       |
| Finding the value of $P_4$ & the type                  | 2&1       |
| Finding the value of $P_5$ & the type                  | 2&1       |
| <b>Total</b>   | <b>20</b> |

OR

**Method 2:**

| Step   | Points    |
|--|-----------|
| Writing the KVL in the left mesh                       | 2         |
| Writing the KVL in the middle mesh                     | 2         |
| Finding the values of $i_b$ and $V_x$                  | 2         |
| Calculating the current of the left mesh               | 2         |
| Calculating the current of the middle mesh             | 2         |
| Calculating $V_5$ by writing the KVL in the right mesh | 1         |
| Finding the value of $P_3$ & the type                  | 2&1       |
| Finding the value of $P_4$ & the type                  | 2&1       |
| Finding the value of $P_5$ & the type                  | 2&1       |
| <b>Total</b>   | <b>20</b> |

**Problem 5.**

| Step  | Points    |
|---|-----------|
| Solving the open circuit voltage for Thevenin voltage source                    | -         |
| Writing the KCL at node a   | 2         |
| Writing the KCL at the top node   | 2         |
| Finding the Values of $V_{oc}$ and $V_x$  | 4         |
| Finding the $R_{th}$  | -         |
| Recognizing parallel combination of $R_1    R_3 = 5/6\Omega$                    | 1         |
| Recognizing series combination of $R_2 + 5/6\Omega = 23/6\Omega$                | 1         |
| Recognizing the parallel combination of $R_4    R_5 = 8/6\Omega$                | 1         |
| Recognizing the parallel combination of $8/6\Omega    23/6\Omega = 92/93\Omega$ | 1         |
| Finding the $I_{No}$  | 2         |
| Finding the $R_{No}$  | 2         |
| Drawing the correct Thevenin equivalent network                                 | 2         |
| Drawing the correct Norton equivalent network                                   | 2         |
| <b>Total</b>  | <b>20</b> |

