

Q1	Q2	Q3	Q4	Total
/20	/30	/30	/20	/100

EECS / CSE 70A Midterm Exam #2

SOLUTION KEY


DO NOT BEGIN THE EXAM UNTIL YOU ARE TOLD TO DO SO.

Print your name on all pages.

Write your solutions in clear steps with concise explanations.

PROBLEM 1: (20 points)

Assuming ideal op-amp:

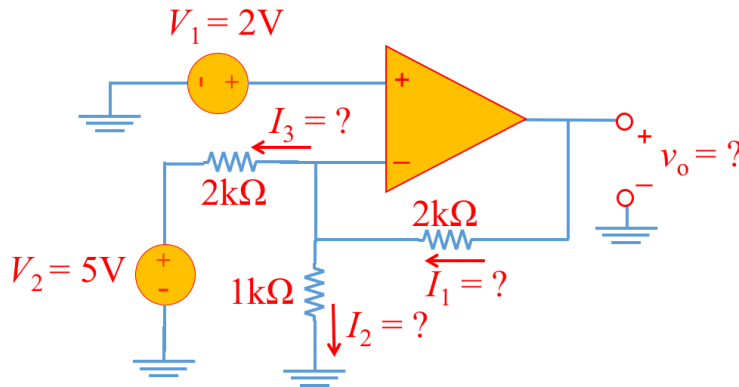(a) Calculate currents I_1 , I_2 and I_3 .(b) Find the output voltage v_o .

I_1	0.5mA
I_2	2mA
I_3	-1.5mA
v_o	3V

SOLUTION:

Opamp is ideal so voltage at its positive and negative inputs are equal: $V_+ = V_- = 2V$ and there is no current flowing in to the opamp input pins.

$$I_3 = \frac{V_- - V_2}{2k\Omega} = -1.5mA$$

$$I_2 = \frac{V_-}{1k\Omega} = 2mA$$


KCL at V_- : $I_1 = I_2 + I_3 = 0.5mA$

KVL: $v_o = V_- + 2k\Omega \cdot I_1 = 2 + 1 = 3V$

PROBLEM 2: (30 points)

The switch in the circuit in the figure below has been closed for a long time (from $t = -\infty$ till $t = 0$) and is opened at $t = 0$.

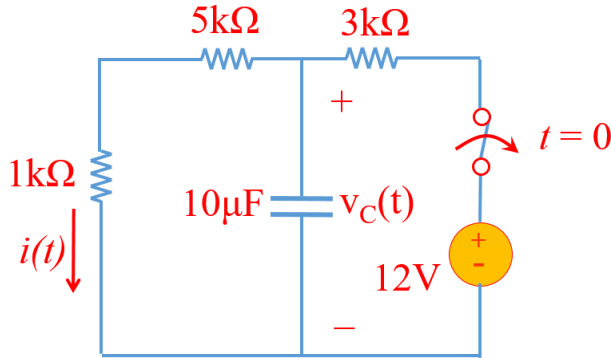- (a) Find the voltage across the capacitor, $v_C(t)$ for $t > 0$.
- (b) Find the current passing through the $1k\Omega$ resistor for $t > 0$.



$v_C(t)$	$v_C(t) = 8e^{\frac{-t}{0.06}} \text{ (V)}$
$i(t)$	$i(t) = 1.33e^{\frac{-t}{0.06}} \text{ (mA)}$

SOLUTION:

Capacitor is open-circuit at DC, which is the state the circuit is in for $t < 0$ and $t = \infty$.

For $t < 0$: $v_C(t) = \frac{5k\Omega + 1k\Omega}{5k\Omega + 1k\Omega + 3k\Omega} \times 12V = 8V$ and $i(t) = \frac{12V}{5k\Omega + 1k\Omega + 3k\Omega} = 1.33mA$

For $t = \infty$: notice the switch is open so the voltage source and $3k\Omega$ resistors are out of the circuit. Capacitor is also open-circuit so no current passes through it $\rightarrow v_C(t = \infty) = 0$ and $i(t = \infty) = 0$.

After the switch opens, capacitor sees $1k\Omega$ and $5k\Omega$ series resistances \rightarrow circuit time constant $= \tau = RC = 6k\Omega \times 10\mu F = 6 \times 10^{-2} s$

Solving for first order differential equation, we know for $t > 0$:

$$v_C(t) = v_C(t=\infty) + [v_C(t=0^+) - v_C(t=\infty)]e^{\frac{-t}{\tau}} \text{ and } i(t) = i(t=\infty) + [i(t=0^+) - i(t=\infty)]e^{\frac{-t}{\tau}}$$


$$\rightarrow v_C(t) = 8e^{\frac{-t}{0.06}} \text{ (V)} \text{ and } i(t) = 1.33e^{\frac{-t}{0.06}} \text{ (mA)}$$

PROBLEM 3: (30 points)

The switch in the circuit in the figure below was closed for a long time and is opened at $t = 0$.

(a) Find the expression of the $i_L(t)$ for $t > 0$.

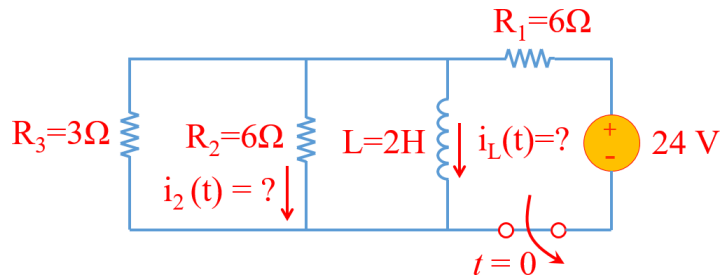(b) Find the expression of the current passing R_2 , $i_2(t)$ for $t > 0$.



$i_L(t)$	$4e^{-\frac{t}{1}} \text{ (A)}$
$i_2(t)$	$-\frac{4}{3}e^{-\frac{t}{1}} \text{ (A)}$

SOLUTION:

inductor is short-circuit at DC, which is the state the circuit is in for $t < 0$ and $t = \infty$.

$$\text{For } t < 0 : i_L(t) = \frac{24V}{6\Omega} = 4A \text{ and } i_2(t < 0) = 0$$

For $t = \infty$: notice the switch is open so the voltage source and $6k\Omega$ resistor are out of the circuit. Inductor is also short-circuit and since there is no independent source $\rightarrow i_L(t = \infty) = 0$.

From KCL we see after the switch is open $i_2(t) = -i_L(t)/3$ and the current passing R_3 $i_1(t) = -2i_L(t)/3$.

The equivalent resistance seen from the inductor is $R_2 \parallel R_1 = 2\Omega \rightarrow$ circuit time constant $= \tau = L/R = 2H/2\Omega = 1s$

Solving for first order differential equation, we know for $t > 0$:


$$i_L(t) = i_L(t=\infty) + [i_L(t=0^+) - i_L(t=\infty)]e^{-\frac{t}{\tau}} \text{ and } i_L(t) = -3i_2(t)$$

$$\rightarrow i_L(t) = 0 + [4 - 0]e^{-\frac{t}{1}} \text{ (mA)} = 4e^{-\frac{t}{1}} \text{ (mA)} \text{ and } i_2(t) = -\frac{4}{3}e^{-\frac{t}{1}} \text{ (A)}$$

PROBLEM 4: (20 points)

The switch in the circuit in the figure below was open for a long time (from $t = -\infty$ till $t = 0$) and is closed at $t = 0$. Assume the capacitor is completely discharged before $t = 0$. Opamp is ideal.

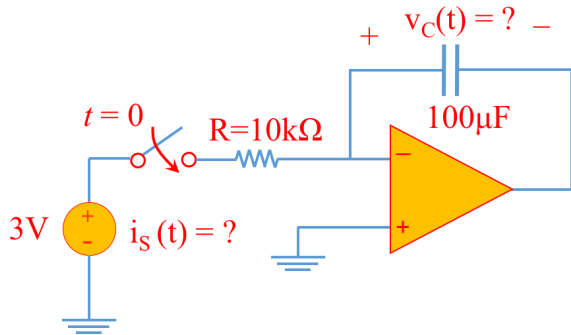
- (a) Find the current supplied by the voltage source, $i_s(t)$ for $t > 0$.
- (b) Find the voltage across the capacitor, $v_C(t)$ at $t = 2s$.



$i_s(t)$	0.3mA
$v_C(t)$	6V

SOLUTION:

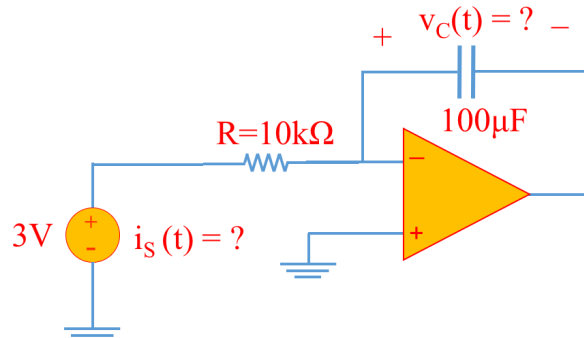for $t < 0$ capacitor is fully discharged so $v_C(t < 0) = 0$. After the switch closes, we will have the circuit below :



Opamp is ideal \rightarrow negative and positive opamp input pins have the same voltage: $V_- = V_+ = 0V \rightarrow i_s(t) = 3V / 10k\Omega = 0.3mA$.

Since no current enters the opamp input pins, $i_s(t)$ has nowhere to go but through the capacitor: $i_C(t) = i_s(t) = 0.3mA$.

For capacitor we know: $i_C(t) = C \frac{dv_C(t)}{dt}$ or $v_C(t) = \int \frac{1}{C} i_C(t) dt \rightarrow$

To find the voltage at $t = 2$ we do the integration fro $t = 0$ to $t = 2$:

$$v_C(t) = \int_0^2 10^4 \times 0.3mA dt = \int_0^2 3 dt = 6V$$