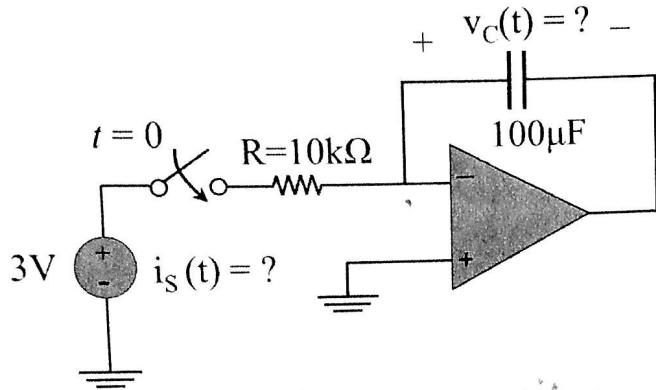


**PROBLEM 4: (20 points)**

The switch in the circuit in the figure below was open for a long time (from  $t = -\infty$  till  $t = 0$ ) and is closed at  $t = 0$ . Assume the capacitor is completely discharged before  $t = 0$ . Opamp is ideal.

- (a) Find the current supplied by the voltage source,  $i_s(t)$  for  $t > 0$ .
- (b) Find the voltage across the capacitor,  $v_C(t)$  at  $t = 2s$ .



$i_s(t)$	0
$v_C(t)$	

At  $t=0$ , capacitor is removed,  $v_+ = v_- = 0$   
 (4)  $\downarrow$  ground


At  $t > 0$  source is connected  
 $v_- = -3V$   
 $\frac{0 - 3V}{10k\Omega} = i_s(t)$   
 $\frac{0 - 3V}{10k\Omega} = i_s(t) = -\frac{3V}{10k\Omega}$   
 (2)

\*  $\frac{78}{100}$

**PROBLEM 2: (30 points)**

The switch in the circuit in the figure below has been closed for a long time (from  $t = -\infty$  till  $t = 0$ ) and is opened at  $t = 0$ .

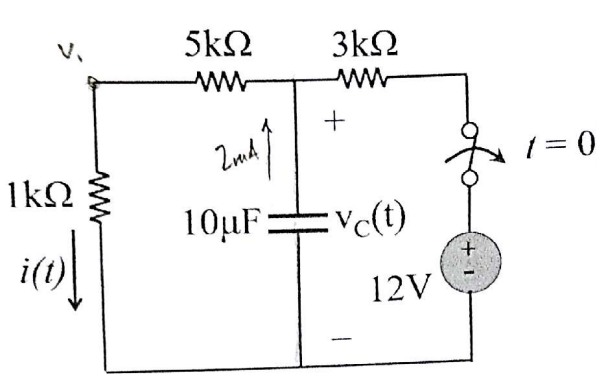
- (a) Find the voltage across the capacitor,  $v_C(t)$  for  $t > 0$ .
- (b) Find the current passing through the  $1k\Omega$  resistor for  $t > 0$ .



$v_C(t)$	<del>12V</del>
$i(t)$	<del>2mA</del>


$R_{eq} = (5 + 1) \parallel 3 \Rightarrow 2k\Omega$

for  $t = 0^-$ :

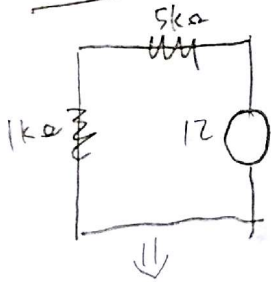

$\tau = RC$   
 $V_C(t) = V_0 e^{-t/\tau}$

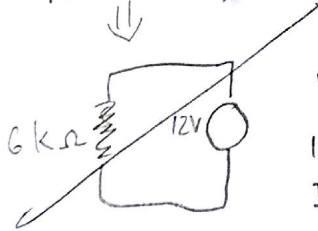
$\tau = RC = (2 \times 10^3)(10 \times 10^{-6}) = 20 \times 10^{-3} = 0.02s$



$V = IR$   
 $12 = I(6k)$   
 $I = 2mA$



for  $t < 0^-$ :

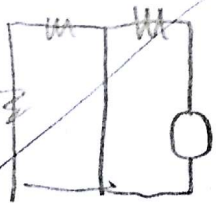


$\frac{V - V_0}{6} = 0$

$\frac{V - 12}{6} = 0$

$V - 12 = 0$

$V = 12$

~~8/10~~ ~~A~~

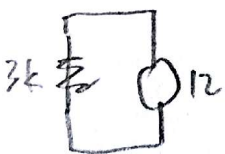

$V = IR$   
 $12 = I(3k)$   
 $I = 4mA$


4/30

**PROBLEM 3: (30 points)**

The switch in the circuit in the figure below was closed for a long time and is opened at  $t = 0$ .

(a) Find the expression of the  $i_L(t)$  for  $t > 0$ .

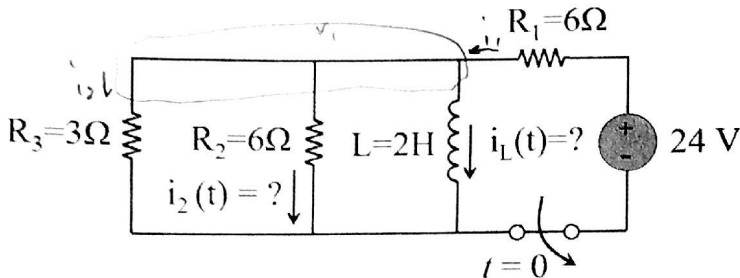(b) Find the expression of the current passing  $R_2$ ,  $i_2(t)$  for  $t > 0$ .



$i_L(t)$	$i_L(t > 0) = 24 e^{-t/2.5}$
$i_2(t)$	$i_2(t > 0) = (V_1 - 24) e^{-t/2.5}$

$$i_L(t) = V_0 e^{-t/\tau}$$

$$R_{eq} =$$



$$(3 || 6) + 6$$


$$\left(\frac{1}{3} + \frac{1}{6}\right) + 6 = 8 \Omega$$

$$\tau = \frac{L}{R} = \frac{2}{8} = \frac{1}{4}$$

$$i_1 = i_L + i_2 + i_3$$

$$\frac{V_1 - 24}{6} = i_2$$

For  $t > 0$

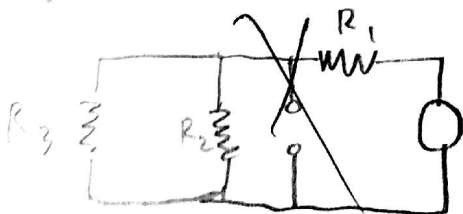


$$\frac{18}{100} *$$

**PROBLEM 4: (20 points)**

The switch in the circuit in the figure below was open for a long time (from  $t = -\infty$  till  $t = 0$ ) and is closed at  $t = 0$ . Assume the capacitor is completely discharged before  $t = 0$ . Opamp is ideal.

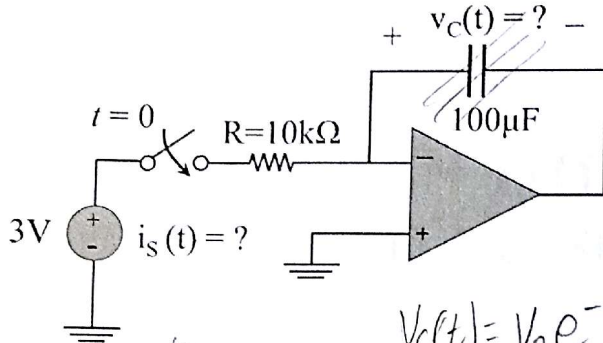- (a) Find the current supplied by the voltage source,  $i_s(t)$  for  $t > 0$ .  
 (b) Find the voltage across the capacitor,  $v_c(t)$  at  $t = 2s$ .



$i_s(t)$	$\frac{3-3e^{-t}}{10} \text{ A}$
$v_c(t)$	$3e^{-2} \text{ V}$ or $\frac{3}{e^2} \text{ V}$

$v_c(t) = V_0 e^{-t/\tau}$   $\tau = RC$   $i_s(t) = \frac{V_0}{R} e^{-t/\tau}$

$$i_s(t) = \frac{3V}{10k\Omega} - \frac{3e^{-t}}{10k\Omega}$$

①  $\frac{V^- - 3V}{10k} = 0$

$V^- = 3V$

$V^- = V^+ = V_0 = 3V$

$v_c(t) = 3e^{\frac{-t}{(10,000)(0.0001)}}$


$v_c(t) = 3e^{-t}$   
 $v_c(2) = 3e^{-2}$

\*\*\*  
6/100


**PROBLEM 4: (20 points)**

The switch in the circuit in the figure below was open for a long time (from  $t = -\infty$  till  $t = 0$ ) and is closed at  $t = 0$ . Assume the capacitor is completely discharged before  $t = 0$ . Opamp is ideal.

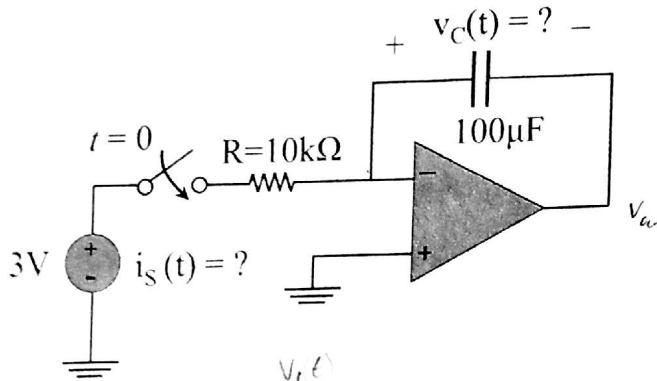- (a) Find the current supplied by the voltage source,  $i_s(t)$  for  $t > 0$ .
- (b) Find the voltage across the capacitor,  $v_c(t)$  at  $t = 2s$ .



$i_s(t)$	.0003A
$v_c(t)$	$\left(\frac{.0003}{100}\right) \cdot 2$ V·sec (-2)

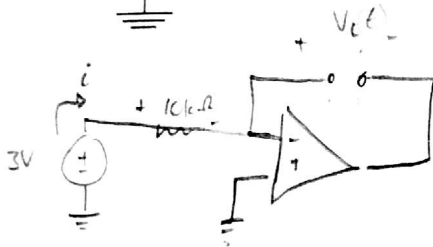

$V_+ = 0 = V_-$

\*  $\frac{60}{100}$

$\frac{3V - 0}{10k\Omega} = i_s = \frac{3V}{10k\Omega} = \frac{3}{10000} A = .0003A$

$V_- - V_{out} = v_c$

$v_c(t) = -V_{out}$

~~$v_c(t) = \frac{1}{C} \int i dt$~~

$= \frac{(.0003A)}{100\mu F} (2)$

W/out a calculator its hard for me to do division like this in my head. It would be unfair if you mark off students' answers even if math is wrong b/c we weren't able to use a calculator.

How difficult is this?!


$\frac{3V}{10k\Omega} = 0.3mA$

if a student cannot do this division he should provide another answer by the end

**PROBLEM 2: (30 points)**

The switch in the circuit in the figure below has been closed for a long time (from  $t = -\infty$  till  $t = 0$ ) and is opened at  $t = 0$ .

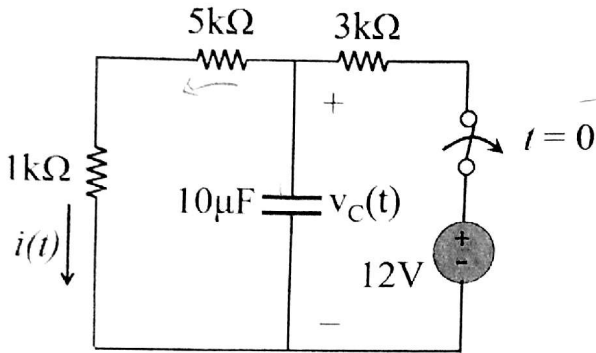
- (a) Find the voltage across the capacitor,  $v_C(t)$  for  $t > 0$ .
- (b) Find the current passing through the  $1k\Omega$  resistor for  $t > 0$ .



$v_C(t)$	$12e^{-t/0.06}$
$i(t)$	$C \frac{dv}{dt} = 10\mu F \frac{dv}{dt}$

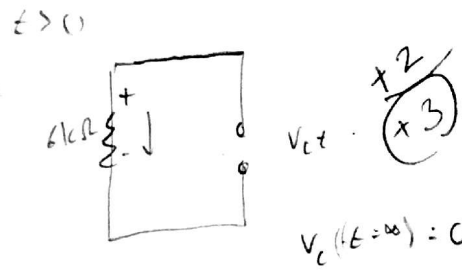0.000010  
x 8000.  
0.000060000  
8000  
x 80000

b/c switch opens Volt. source is gone  
∴ as  $t \rightarrow \infty$   
 $v_C$  &  $i_C = 0$  but  
①  $t > 0$  the capacitor will be discharged



$x(t) = x(t=0) + [x(t=0) - x(t=-\infty)]e^{-t/\tau}$

$i(t)$  also = 0 b/c voltage source as  $t \rightarrow \infty$   
but  $i(t) = C \frac{dv}{dt}$



$\tau @ t > 0$   
 $R_{eq} = 6k\Omega$

$\tau = (6k\Omega) 10\mu F = 6000 \cdot 10^{-6} = 0.06$   
I need a calculator but I think its 0.

Voltage decays to 0 b/c the voltage source is eliminated.

$V_L = iL$   
 $V_C = \frac{1}{C} i$   
 $i = C \frac{dv}{dt}$   
 $i = C \frac{dv}{dt} = 10\mu F$

x  
60/100

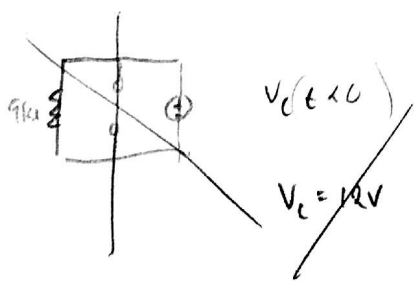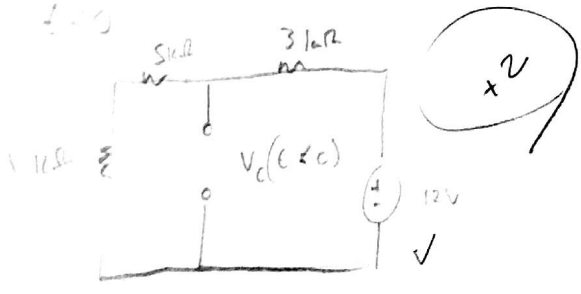


$v_C(t) = v(t=\infty) + (v(t=0) - v(t=\infty))e^{-t/\tau}$   
 $= 12e^{-t/0.06}$

16/30

**PROBLEM 2: (30 points)**

The switch in the circuit in the figure below has been closed for a long time (from  $t = -\infty$  till  $t = 0$ ) and is opened at  $t = 0$ .

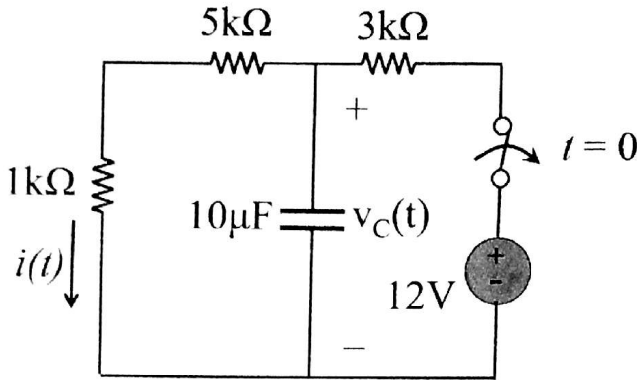- (a) Find the voltage across the capacitor,  $v_C(t)$  for  $t > 0$ .
- (b) Find the current passing through the  $1k\Omega$  resistor for  $t > 0$ .



$v_C(t)$	$8e^{-t/0.06} \text{ V}$	-1
$i(t)$	<del><math>-4.8 \times 10^{-6} e^{-t/0.06} \text{ A}</math></del>	

$i(t) = i_{\text{initial}} + [i_{\text{final}} - i_{\text{initial}}] e^{-t/\tau}$

$t < 0$



$V_{(t=0^-)} = 12V \left(\frac{6}{9}\right) = 8V \checkmark$

$t > 0$



$V_{(t>0)} = 0$

$\tau = R_{\text{eq}} C = 6 \times 10^3 \cdot 10 \times 10^{-6} = 60 \times 10^{-3} \text{ s} = 0.06 \text{ s}$

$v_C(t) = 8e^{-t/0.06} \text{ V}$

$i(t) = C \frac{dv}{dt} = 10\mu\text{F} \left( -8 \times (6 \times 10^{-2})^{-1} e^{-t/0.06} \right) = 10\mu\text{F} (-0.48 e^{-t/0.06}) = -4.8 \times 10^{-6} e^{-t/0.06} \text{ A}$

$i(t) = -i_C(t)$

-5

24  
30

$\frac{6}{100} \quad \times \times$




**PROBLEM 3: (30 points)**

The switch in the circuit in the figure below was closed for a long time and is opened at  $t = 0$ .


(a) Find the expression of the  $i_L(t)$  for  $t > 0$ .

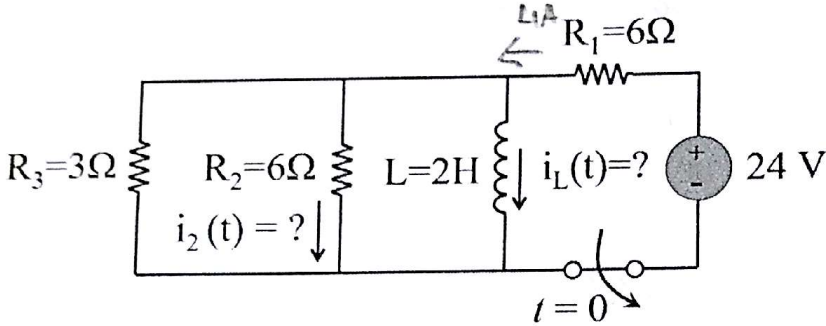(b) Find the expression of the current passing  $R_2$ ,  $i_2(t)$  for  $t > 0$ .



$i_L(t)$	0
$i_2(t)$	$\frac{4}{3} e^{-3/4 t}$

$t < 0$

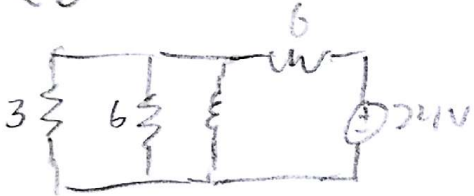

~~$i_L(t) = 0$~~

$t > 0$



②

②  $i_2(t) = 4 \left( \frac{3}{9} \right) e^{-t/4/35}$   
 $= \frac{12}{9} e^{-\frac{3}{4} t}$

~~②  $\tau = \frac{L}{R_{eq}} = \frac{2H}{\frac{3}{2}\Omega} = \frac{4}{3} s$~~

~~$R_{eq} = \frac{3}{2} \Omega$~~

$\frac{61}{100}$

\*




**PROBLEM 2: (30 points)**

The switch in the circuit in the figure below has been closed for a long time (from  $t = -\infty$  till  $t = 0$ ) and is opened at  $t = 0$ .

(a) Find the voltage across the capacitor,  $v_C(t)$  for  $t > 0$ .

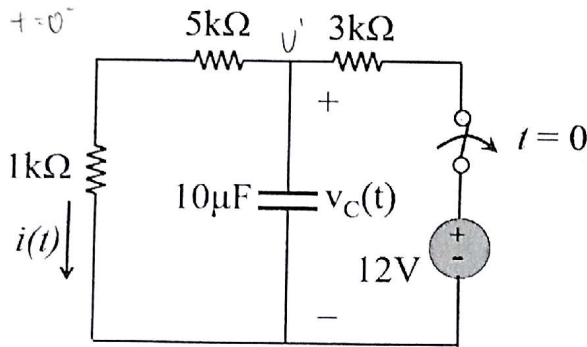(b) Find the current passing through the  $1k\Omega$  resistor for  $t > 0$ .




$v_C(t)$	$12e^{-6 \times 10^5 t} + V$
$i(t)$	$-72e^{-6 \times 10^5 t} A$

$\frac{V'}{6} + \frac{V' - 12}{3} = 0$   
 $V' + 2V' - 24 = 0$   
 $3V' = 24$   
 $V' = 12V$   
 $V' = 8V$

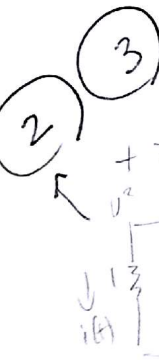(2) (2)

$\tau = RC = 6(10^{-5}) \rightarrow 6 \times 10^{-2}$   
 $V_C = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau} = 12e^{-6 \times 10^5 t}$   
 $V_C = i(t)R_{eq} = i(t)6$



$i(t) = \frac{V_2}{1}$   
 $\frac{V_2}{1} = \frac{V_2 - V_C}{5}$

$i(t) = C(\frac{1}{\tau})V_C$   
 $= 10^{-5}(-6 \times 10^5)(12e^{-6 \times 10^5 t})$

(11/30)

X 38/100