

EECS/CSE 70A Network Analysis I


Homework #3

Due on or before


5/2/2017, Tuesday 6pm

(online on the designated EEE dropbox)


Problem 1: (KCL, KVL, Ohm's Law) Find currents i_1, i_2, i_3 . (10pts.)

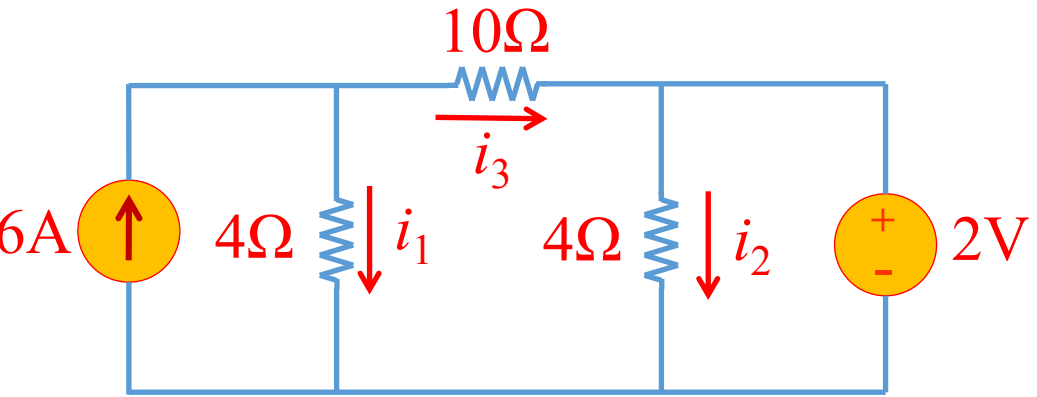


Problem 2: Use nodal analysis and find i_3 . (10pts.)

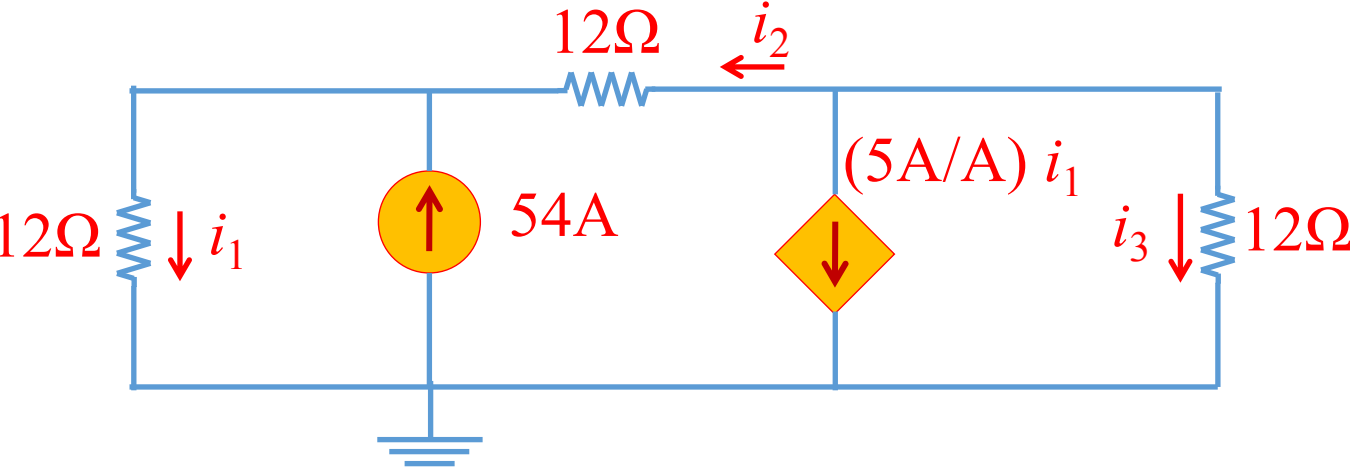


Problem 3: Use nodal analysis and find V_0 . (10pts.)

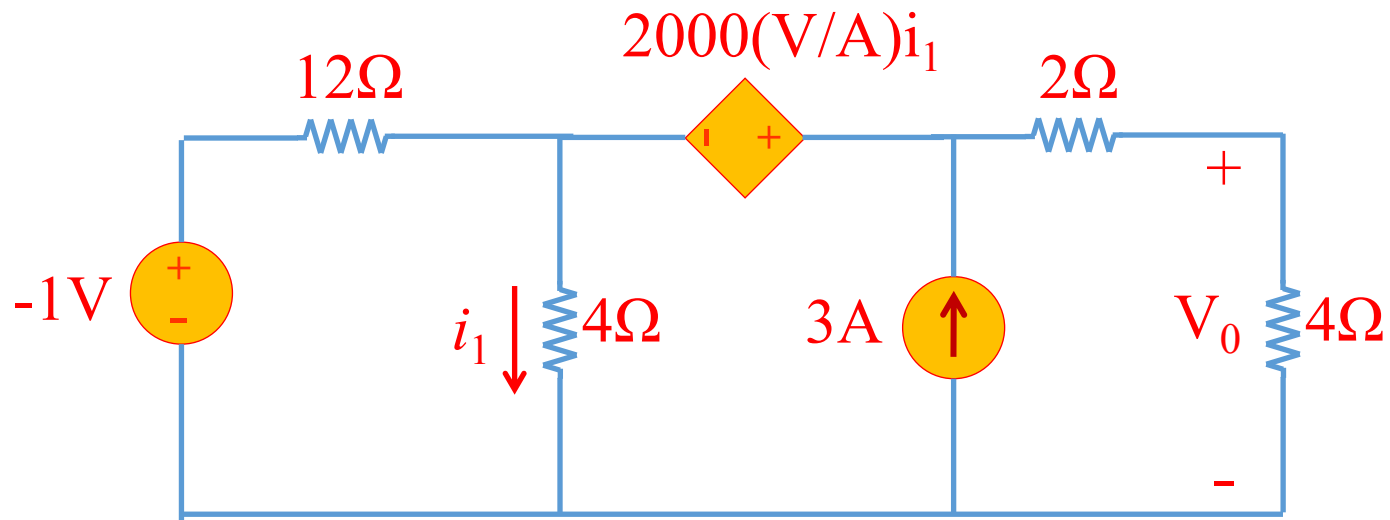


Problem 4: Write all nodal voltage equations and put them in the matrix form. (You do not need to solve.) (10pts.)

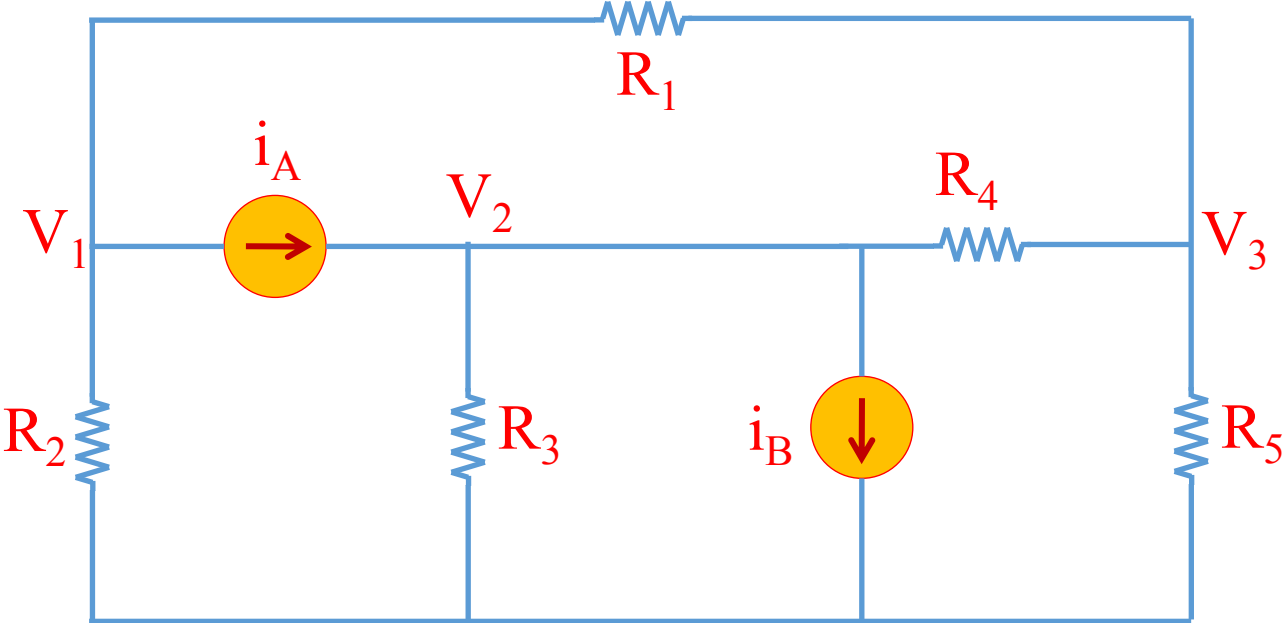


Problem 5: Write all mesh current equations and put them in the matrix form. (You do not need to solve.) (10pts.)

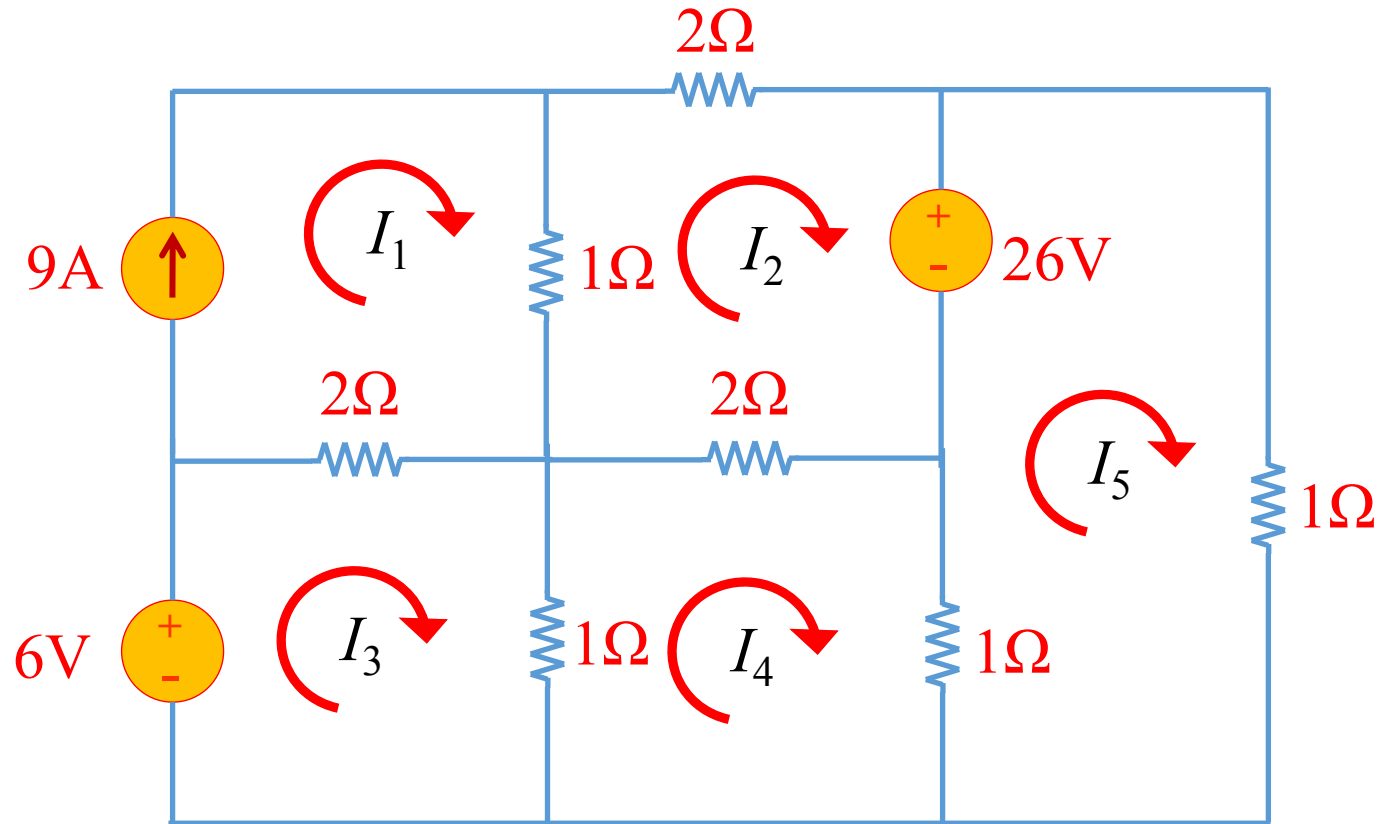


Problem 6: Use mesh analysis to find the power delivered/consumed by the CCVS (10pts.)

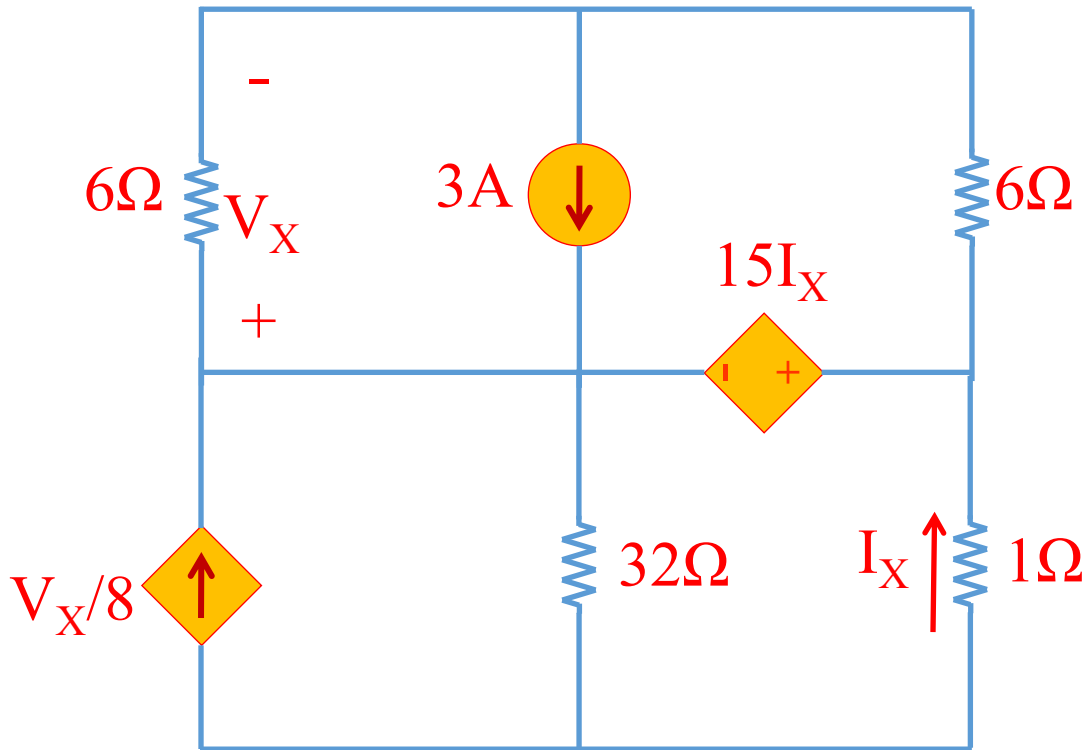


Problem 5: Use mesh analysis to find I_0 (10pts.)

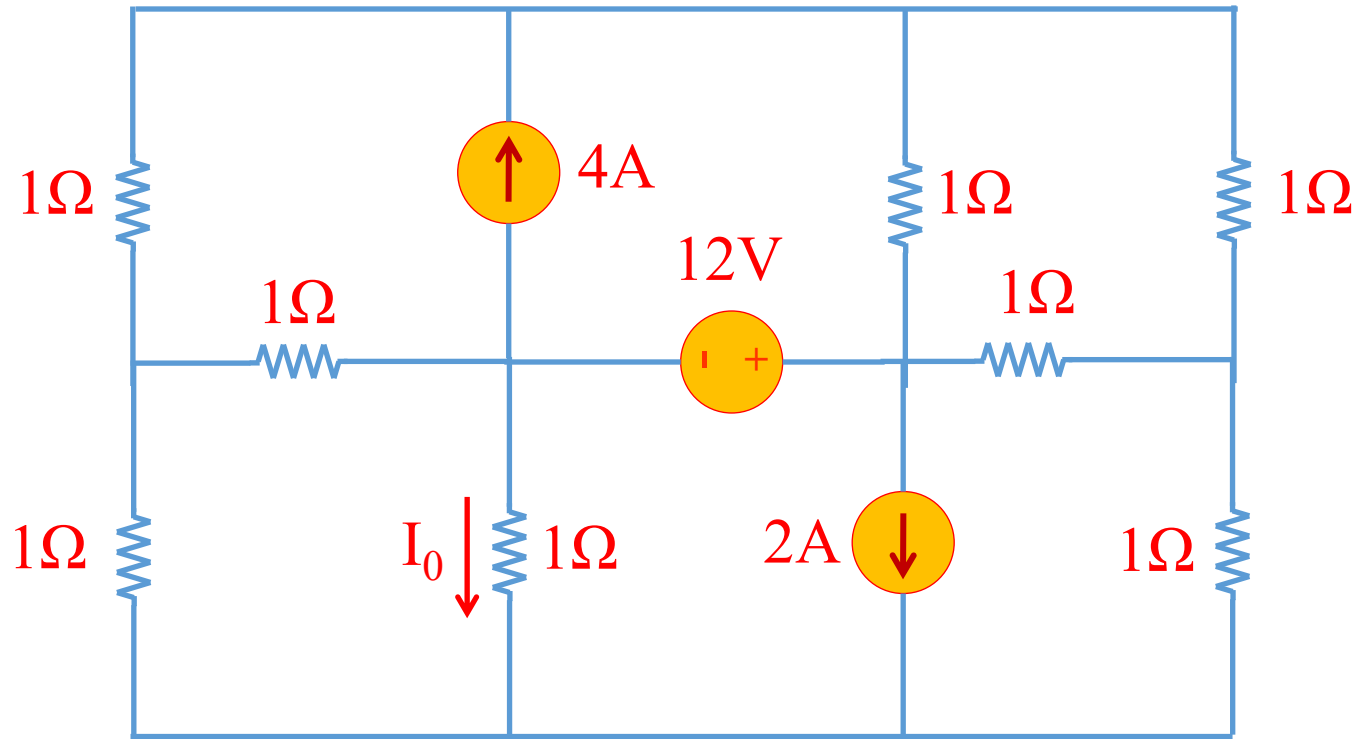


Problem 8: Use both nodal and mesh analyses to find I_o (10pts.)

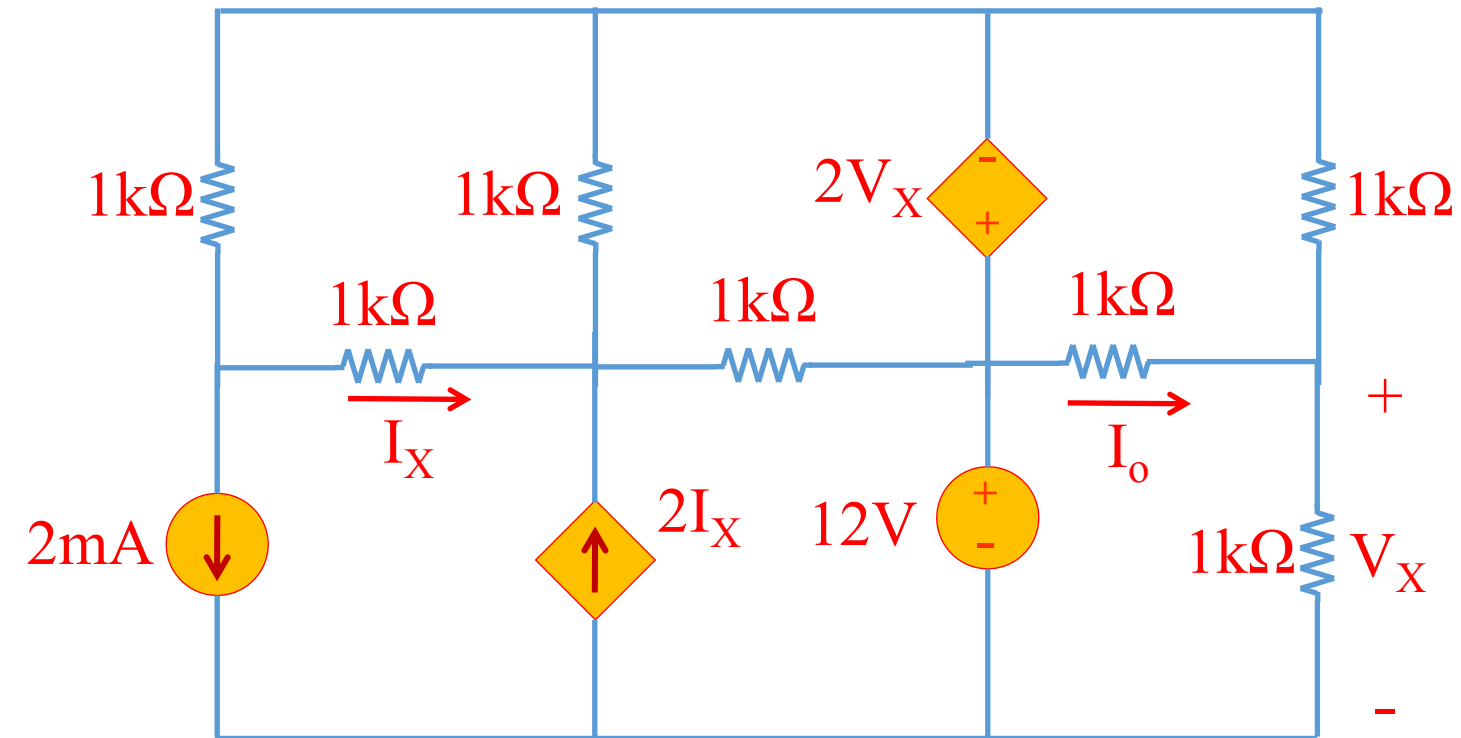

Problem 9: Find V_o using Thévenin theorem. (10pts.)

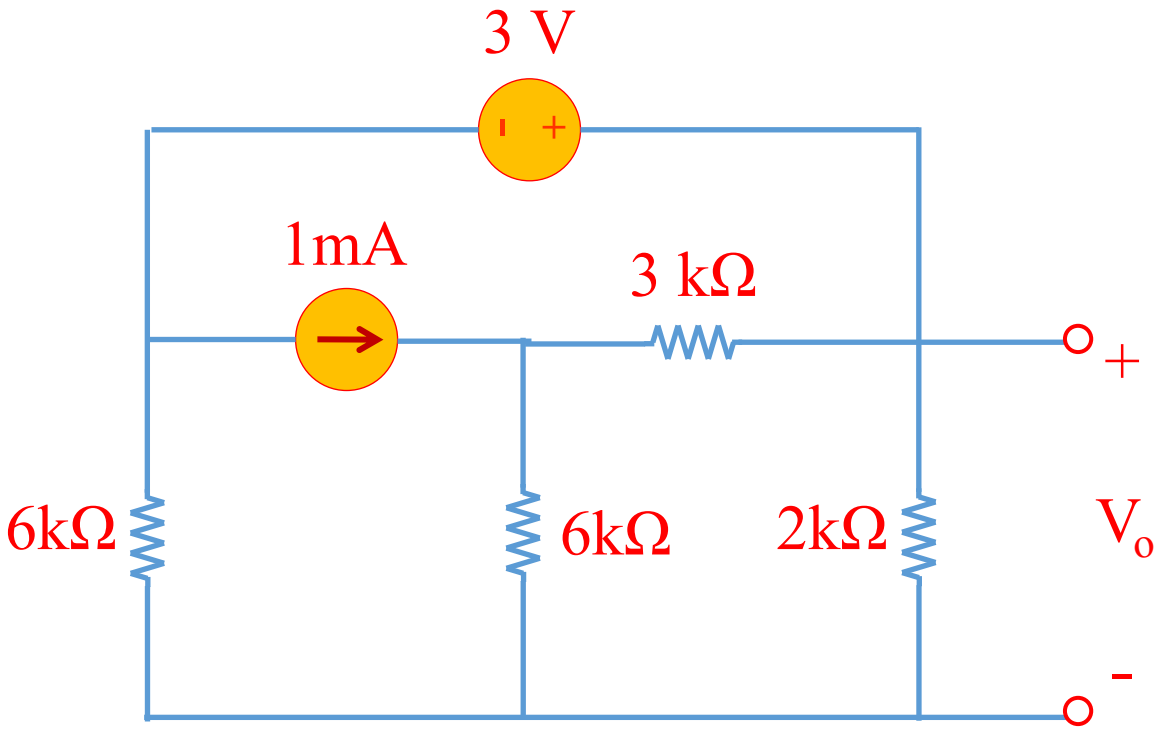

Problem 9: Find I_o using Norton theorem. (10pts.)

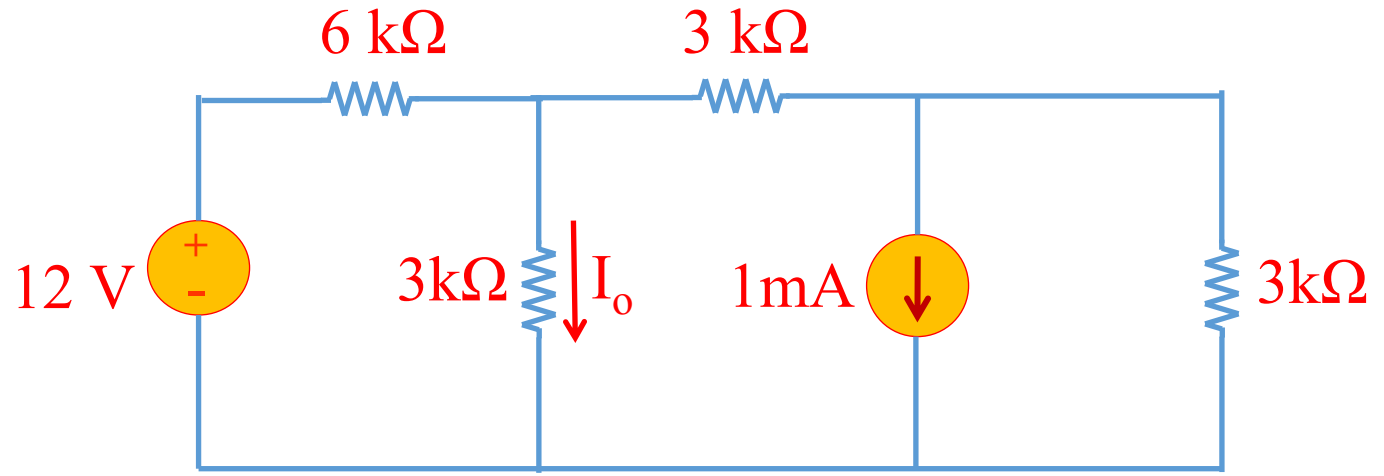

Problem 10: Obtain the Thévenin and Norton equivalent network representations as seen from the terminals a-b. (10pts.)

