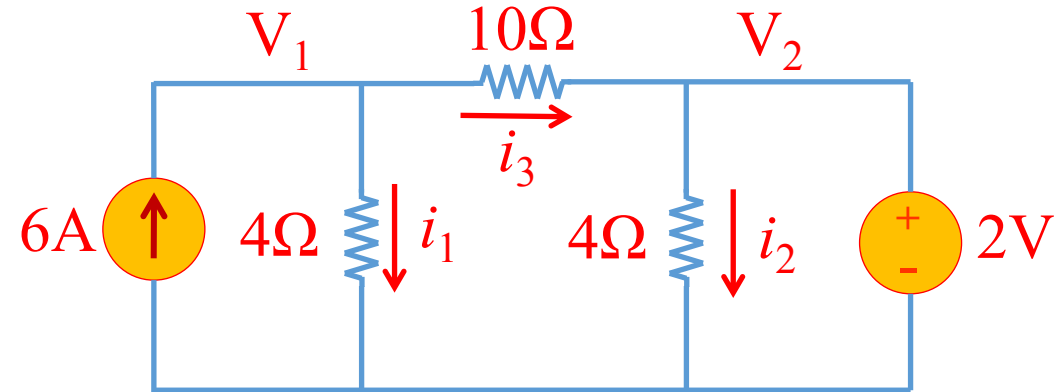


# EECS/CSE 70A Network Analysis I

## Homework #3

## Solution Key

Problem 1: (KCL, KVL, Ohm's Law) Find currents  $i_1$ ,  $i_2$ ,  $i_3$ . (10pts.)



Solution:

KCL @ node 1:  $6 \text{ A} = i_1 + i_3$


$i_1 = V_1/4 \ \Omega$ ,  $i_3 = (V_1 - V_2)/10 \ \Omega = (V_1 - 2)/10 \ \Omega$

$\rightarrow 6 \text{ A} = V_1/4 + (V_1 - 2)/10 \ \Omega \rightarrow V_1 = 17.71 \text{ V}$

$\rightarrow i_1 = 4.42 \text{ A}$ ,  $i_3 = 1.57 \text{ A}$

$i_2 = 2 \text{ V}/4 \ \Omega = 0.5 \text{ A}$

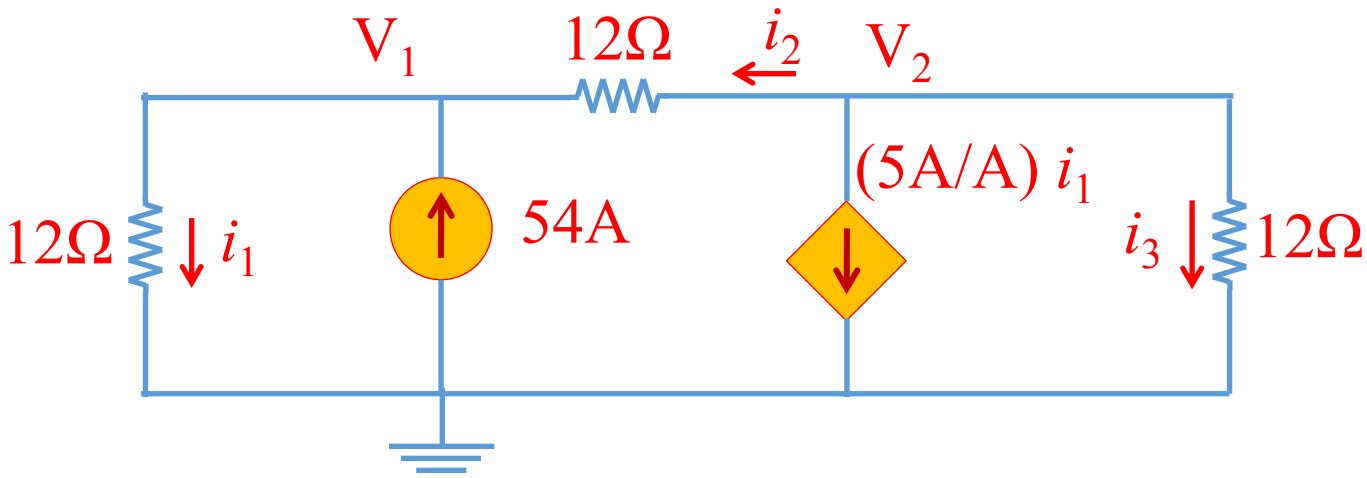Problem 2: Use nodal analysis and find  $i_3$ . (10pts.)



Solution:

$$i_1 = V_1/12 \Omega, i_3 = V_2/12 \Omega, i_2 = (V_2 - V_1)/12 \Omega$$


$$\text{KCL @ node 1: } 54 \text{ A} + i_2 = i_1 \rightarrow 54 + (V_2 - V_1)/12 \Omega = V_1/12 \Omega$$

$$\text{KCL @ node 2: } 5i_1 + i_2 + i_3 = 0 \rightarrow 5V_1/12 \Omega + (V_2 - V_1)/12 \Omega + V_2/12 \Omega = 0$$

→ Solving the system of two equations and two unknowns:

$$\rightarrow V_1 = 162\text{V and } V_2 = -324\text{V} \rightarrow i_3 = -27\text{A}$$

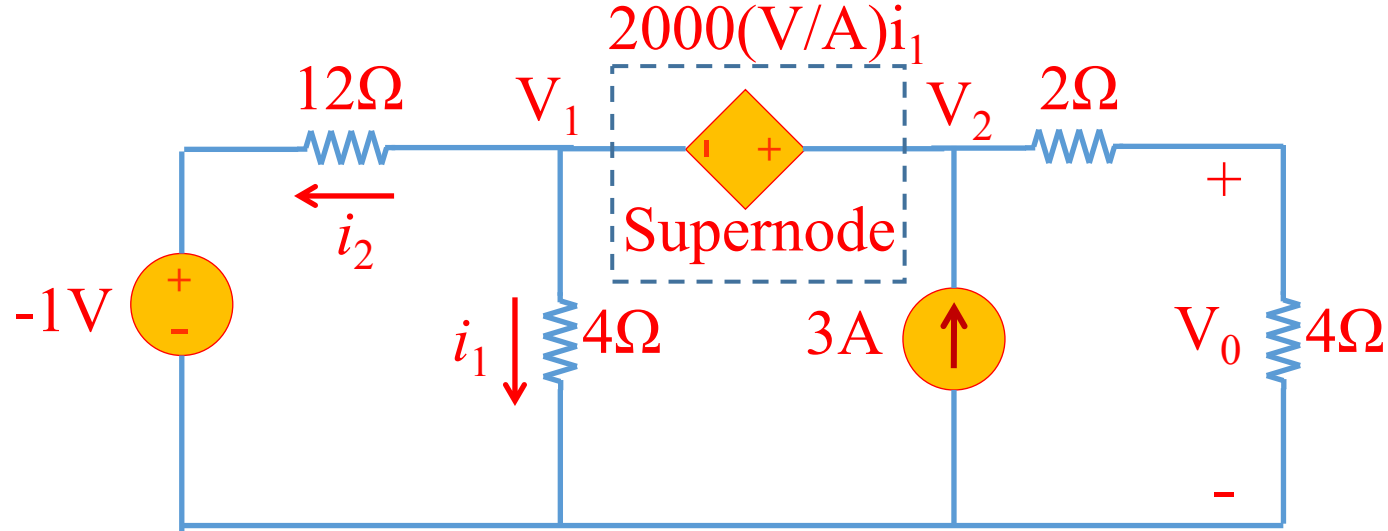Problem 3: Use nodal analysis and find  $V_0$ . (10pts.)



Solution:


$$i_1 = V_1/4 \text{ } \Omega, \quad i_2 = (V_1 + 1)/12 \text{ } \Omega, \quad V_2 = V_1 + 2000i_1 = V_1 + 500V_1 = 501V_1$$

$$\text{KCL @ supernode: } i_2 + i_1 = 3\text{A} - V_2/6 \rightarrow V_1/4 + (V_1 + 1)/12 \text{ } \Omega = 3\text{A} - V_2/6 = 3\text{A} - 501V_1/6$$

$$\rightarrow V_2 = 17.43\text{V}$$

$$V_0 = 4V_2/(4+2) = 11.62\text{V}$$

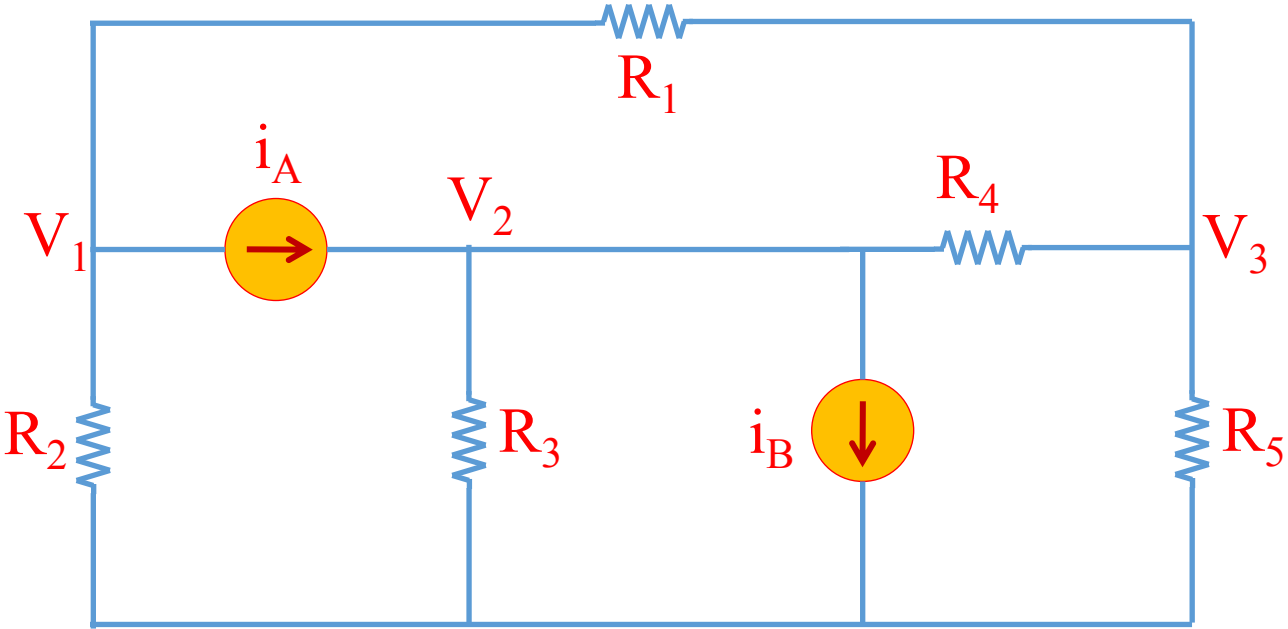Problem 4: Write all nodal voltage equations and put them in the matrix form. (You do not need to solve.) (10pts.)



Solution. Write KCL for all three nodes of the circuit:

$$(V_1 - V_3)/R_1 + V_1/R_2 + i_A = 0, \quad V_2/R_3 + i_B + (V_2 - V_3)/R_4 = 0,$$

$$(V_3 - V_1)/R_1 + (V_3 - V_2)/R_4 + V_3/R_5 = 0$$

Rearranging the equations in the matrix form:


$$V_1(1/R_1 + 1/R_2) - V_2 \times 0 - V_3/R_1 = -i_A$$

$$-V_1 \times 0 + V_2(1/R_3 + 1/R_4) - V_3/R_4 = i_A - i_B$$

$$-V_1(1/R_1) - V_2(1/R_4) + V_3(1/R_1 + 1/R_4 + 1/R_5) = 0$$

$$\rightarrow \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & 0 & -\frac{1}{R_1} \\ 0 & \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_1} & -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -i_A \\ i_A - i_B \\ 0 \end{bmatrix}$$

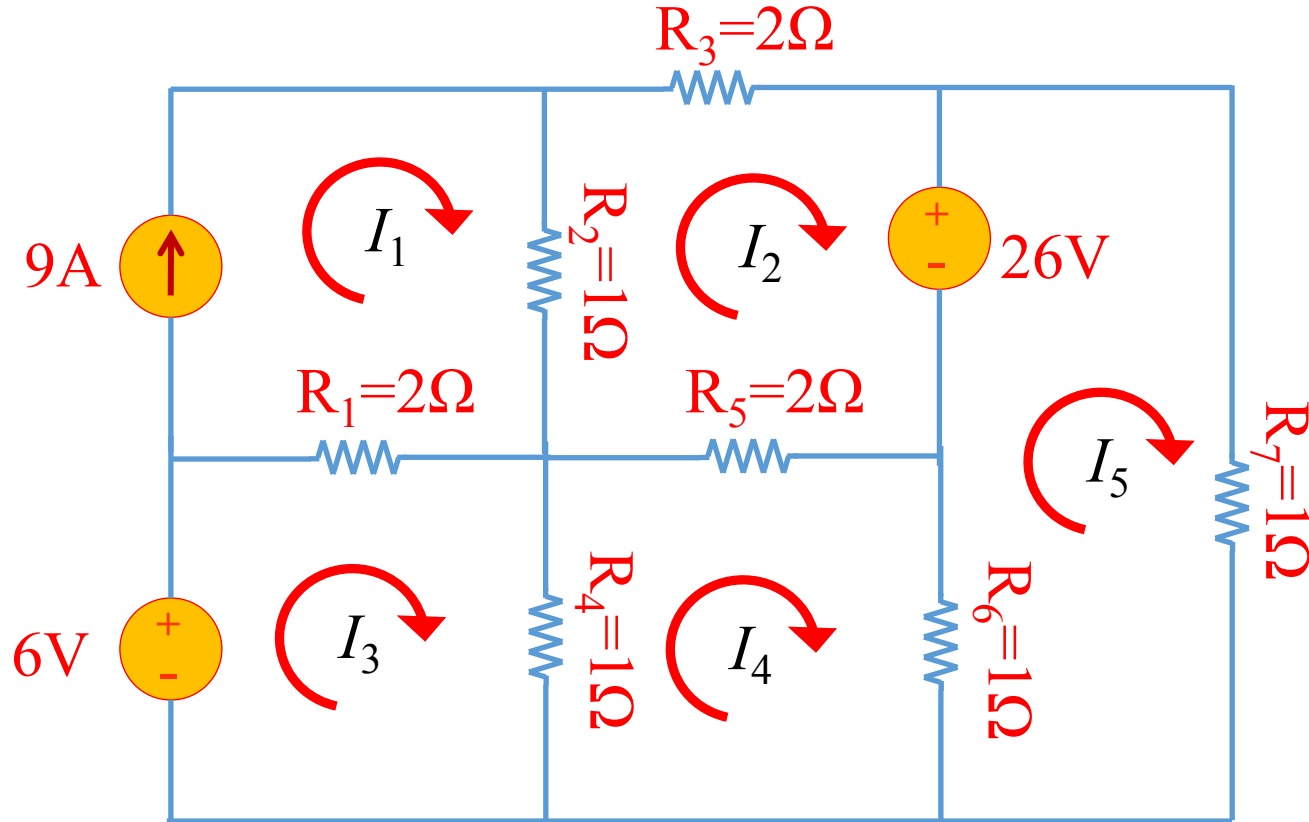Problem 5: Write all mesh current equations and put them in the matrix form. (You do not need to solve.) (10pts.)



Solution. Write KVL for loops  $I_2$  through  $I_5$ :

$$\text{Loop } I_2: (I_2 - I_1)R_2 + I_2R_3 + 26 + (I_2 - I_4)R_5 = 0$$

$$\text{Loop } I_3: -6 + (I_3 - I_1)R_1 + (I_3 - I_4)R_4 = 0$$

$$\text{Loop } I_4: (I_4 - I_3)R_4 + (I_4 - I_2)R_5 + (I_4 - I_5)R_6 = 0$$

$$\text{Loop } I_5: -26 + I_5R_7 + (I_5 - I_4)R_6 = 0$$

Rearranging the equations in the matrix form:

$$\text{Loop } I_2: -I_1 + 5I_2 - 2I_4 = -26$$

$$\text{Loop } I_3: -2I_1 + 3I_3 - I_4 = 6$$


$$\text{Loop } I_4: -2I_2 - I_3 + 4I_4 - I_5 = 0$$

$$\text{Loop } I_5: -I_4 + 2I_5 = 26$$

So in the matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ -1 & 5 & 0 & -2 & 0 \\ -2 & 0 & 3 & -1 & 0 \\ 0 & -2 & -1 & 4 & -1 \\ 0 & 0 & 0 & -1 & 2 \end{bmatrix} \times \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 9 \\ -26 \\ 6 \\ 0 \\ 26 \end{bmatrix}$$

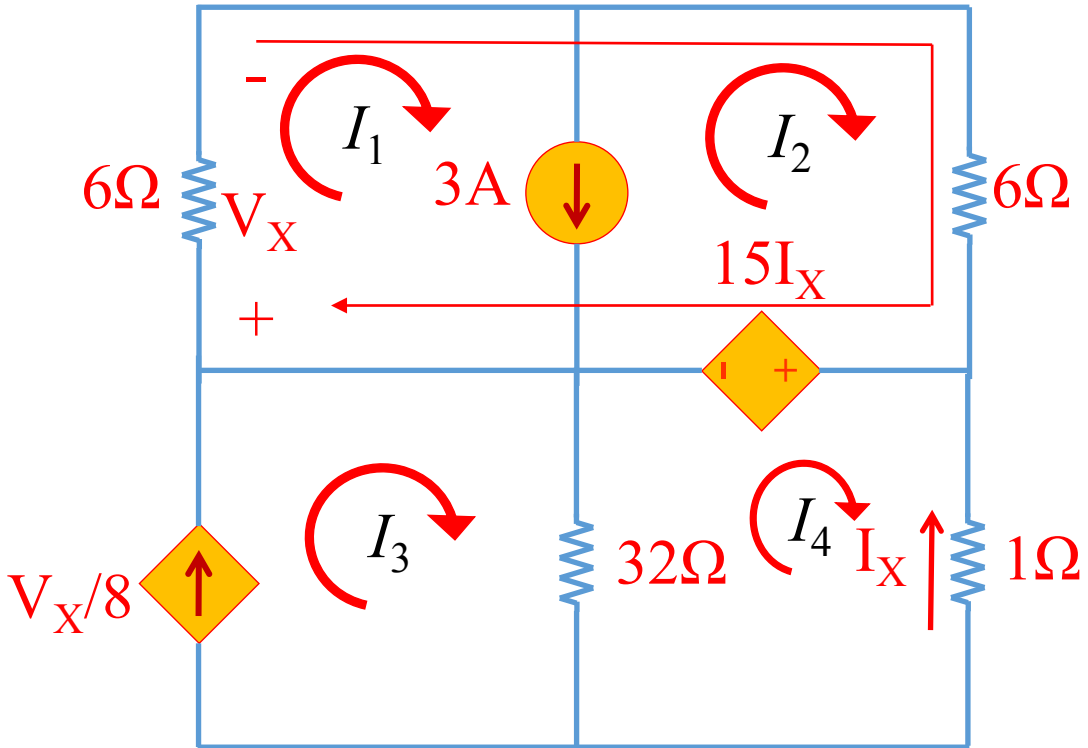Problem 6: Use mesh analysis to find the power delivered/consumed by the CCVS (10pts.)



Solution: Note we have a current source in the loop 1, we have a “supermesh” in this circuit, reducing the number of the equations.

$$I_1 - I_2 = 3A, V_X = 6I_1, I_X = -I_4, I_3 = V_X/8 = 3I_1/4$$

Write KVL for the loops:

$$\text{Loop } I_4: -32(I_4 - I_3) + 15I_X - I_4 = 0$$

$$\rightarrow -48I_4 + 32I_3 = 0 \text{ and since } I_3 = 3I_1/4 \rightarrow$$

$$\rightarrow -48I_4 + 24I_1 = 0 \text{ or } I_1 = 2I_4 \text{ (*)}$$

$$\text{KVL @ supermesh: } -V_X - 6I_2 - 15I_X = 0 \rightarrow$$


$$-6I_1 - 6I_2 + 15I_4 = 0 \text{ and since } I_1 - I_2 = 3A \rightarrow$$

$$-12I_1 + 15I_4 = 18A \text{ (**)}$$

$$\rightarrow \text{From (*) and (**): } I_1 = 4A, I_4 = 2A, I_2 = 1A$$

$\rightarrow$  The current passing through CCVS (with a voltage of  $15I_X = -30V$ ) from its positive polarity to its negative polarity is  $I_2 - I_4 = -1A$  so it is consuming  $+30W$

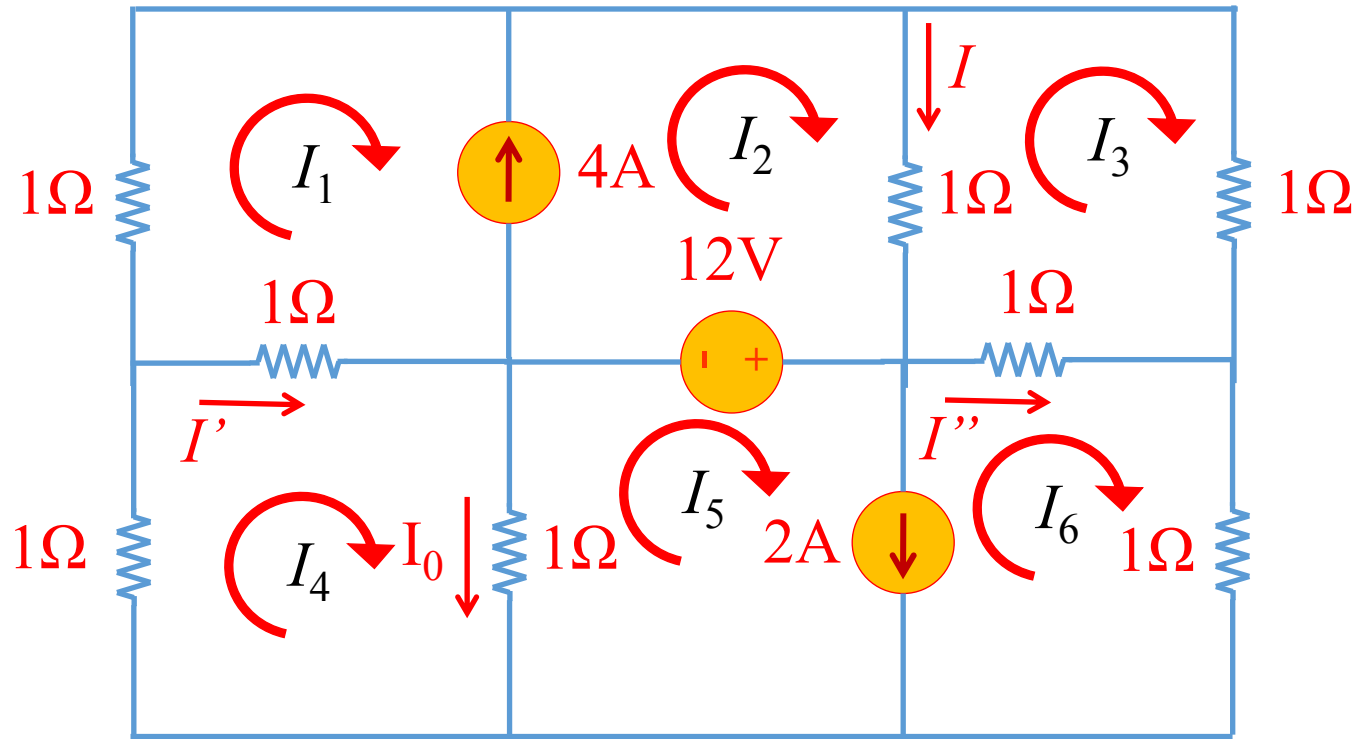Problem 7: Use mesh analysis to find  $I_0$  (10pts.)



*Solution in the next page*



$$\text{KCL: } I_2 = I_1 + I_3 \rightarrow I_1 = I_2 - I_3$$

$$\text{KCL: } I_3 + I'' = I_6 \rightarrow I'' = I_6 - I_3$$

$$\text{KCL: } I_4 = I_1 + I' \rightarrow I' = I_4 - I_1$$

$$\text{KCL: } I_0 + I_5 = I_4 \rightarrow I_0 = I_4 - I_5$$

$$\text{KVL: } 12 = 1 \times I'' + 1 \times I_6 - 1 \times I_0 \rightarrow \text{replacing for } I_0 \text{ and } I'' \text{ from}$$

$$\text{KCL's above} \rightarrow \boxed{-I_3 - I_4 + I_5 + 2I_6 = 12}$$

$$\text{KVL: } 1 \times I' + 1 \times I_0 + 1 \times I_4 = \phi \rightarrow 1 \times (I_4 - I_1) + 1 \times (I_4 - I_5) + 1 \times I_4 = \phi$$

$$\rightarrow \boxed{-I_1 + 3I_4 - I_5 = \phi}$$

$$\text{KCL: } I_6 - I_5 = -2A, \quad I_2 - I_1 = 4A$$

$$\text{KVL: } 1 \times I_1 + 1 \times I_3 - 1 \times I'' + 12 + 1 \times (-I') = \phi$$

$$\rightarrow 1 \times I_1 + 1 \times I_3 - 1 \times (I_6 - I_3) - 1 \times (I_4 - I_1) = \phi$$

$$\rightarrow \boxed{2I_1 + 2I_3 - I_4 - I_6 = -12}$$

$$\text{KVL: } 1 \times I_3 + 1 \times (-I'') + 1 \times (-I) = \phi$$

$$\rightarrow I_3 - (I_6 - I_3) - (I_2 - I_3) = \phi \rightarrow \boxed{-I_2 + 3I_3 - I_6 = \phi}$$

Arrange in matrix form and solve:

$$0I_1 + 0I_2 - I_4 + I_5 + 2I_6 = 12$$

$$-I_1 + 0I_2 + 0I_3 + 3I_4 - I_5 + 0I_6 = \phi$$

$$0I_1 + 0I_2 + 0I_3 + 0I_4 - I_5 + I_6 = -2$$

$$I_1 - I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 = -4$$

$$2I_1 + 0I_2 + 2I_3 - I_4 + 0I_5 - 1I_6 = -12$$

$$0I_1 - I_2 + 3I_3 + 0I_4 + 0I_5 - I_6 = \phi$$

$$I_1 = -4.93A$$

$$I_2 = -0.933A$$

$$I_3 = 0.933A$$


$$I_4 = 0.267A$$

$$I_5 = 5.73A$$

$$I_6 = 3.73A$$

$$I_0 = I_4 - I_5 = -5.46A$$

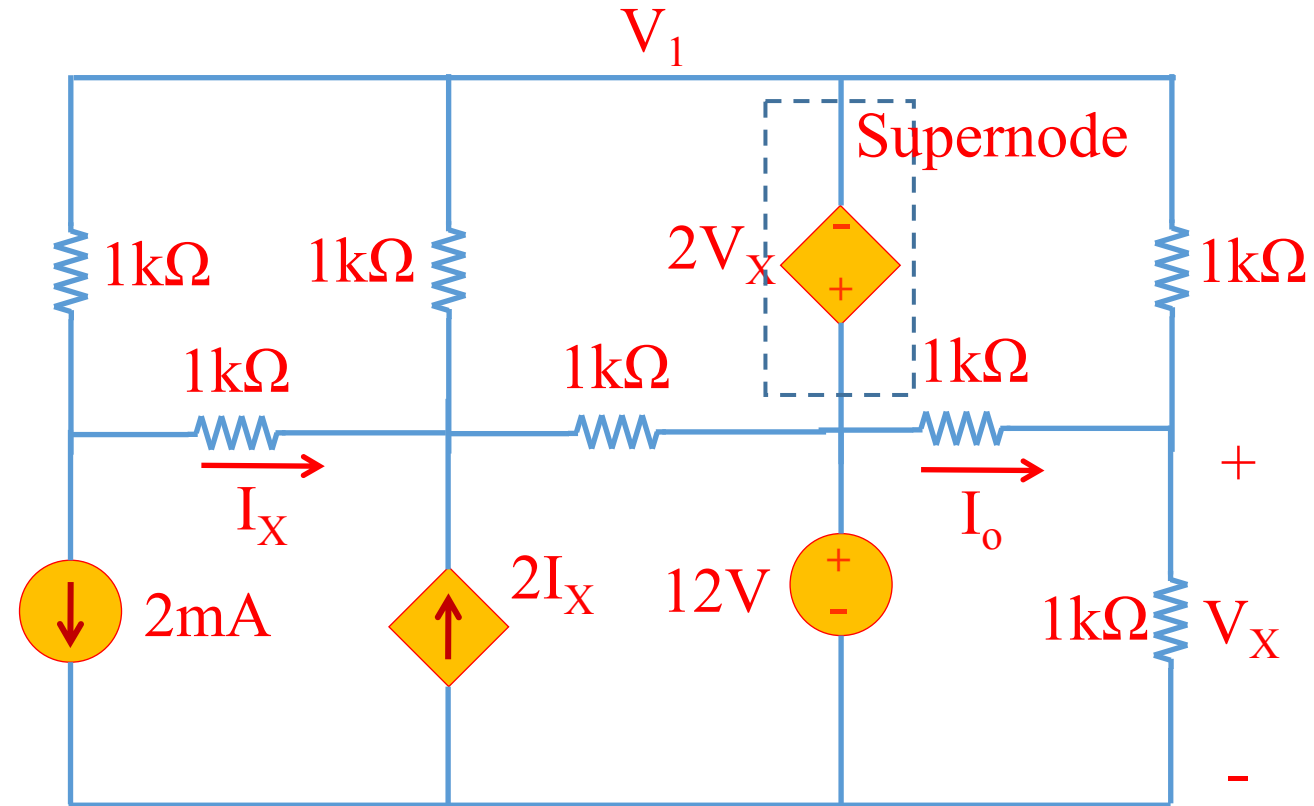Problem 8: Use both nodal and mesh analyses to find  $I_o$  (10pts.)



KCL @  $v_x$ :  $\frac{v_1 - v_x}{1k\Omega} + I_o = \frac{v_x}{1k\Omega}$

$I_o = \frac{12V - v_x}{1k\Omega} \rightarrow \frac{v_1}{1k\Omega} = \frac{3v_x - 12V}{1k\Omega}$


$\rightarrow \boxed{v_1 = 3v_x - 12V} \text{ (*)}$

KVL @ supernode:  $\boxed{v_1 + 2v_x = 12} \text{ (**)}$


$\rightarrow$  from the two equations above:

$v_x = \frac{24}{5} V = 4.8V \rightarrow I_o = \frac{12 - 4.8V}{1k\Omega} = 7.2mA$

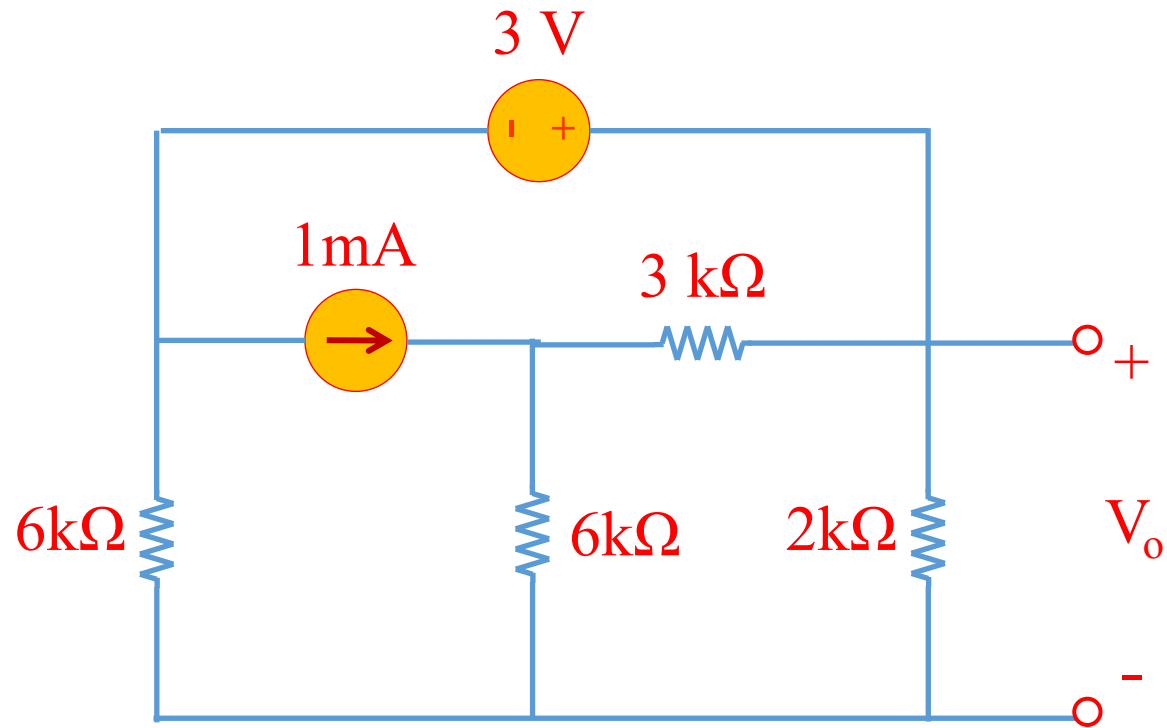Problem 9: Find  $V_o$  using Thévenin theorem. (10pts.)




Equivalent thevenin resistance:

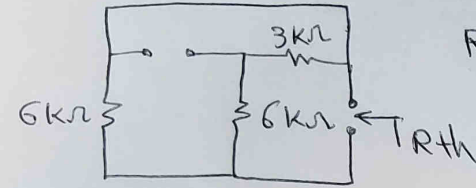


$$R_{th} = (6k\Omega + 3k\Omega) \parallel 6k\Omega = 3.6k\Omega$$

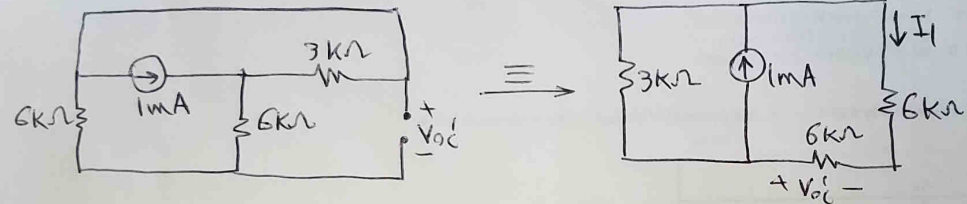Effect of the current source only on the output voltage:



$$I_1 = \left( \frac{3k\Omega}{3k\Omega + 6k\Omega} \right) \times 1mA = 0.2mA \rightarrow V_{oc}' = -0.2mA \times 6k\Omega = -1.2V$$

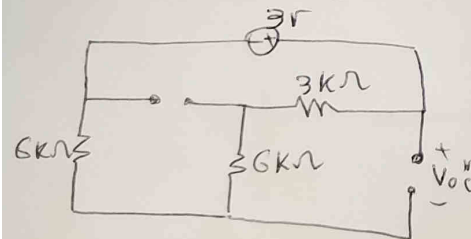
Effect of voltage source only on the output:



$$V_{oc}'' = \frac{9k\Omega}{9k\Omega + 6k\Omega} \times 3V = 1.8V$$


$$\rightarrow V_{oc} = V_{oc}' + V_{oc}'' = 0.6V \text{ (superposition)}$$

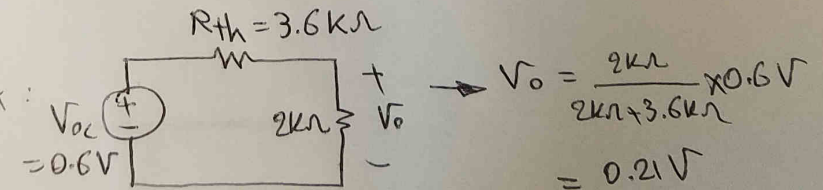$\rightarrow$  Thevenin equivalent circuit:




$$\rightarrow V_o = \frac{2k\Omega}{2k\Omega + 3.6k\Omega} \times 0.6V = 0.21V$$

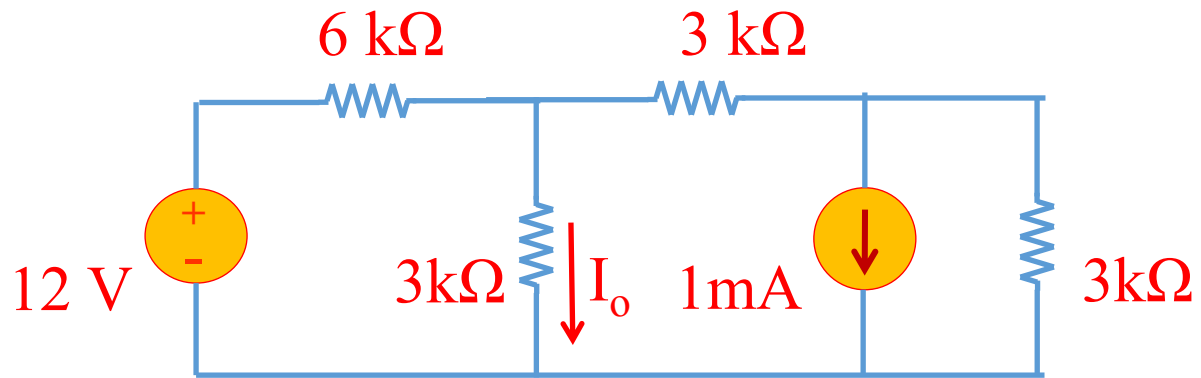
Problem 10: Find  $I_o$  using Norton theorem. (10pts.)



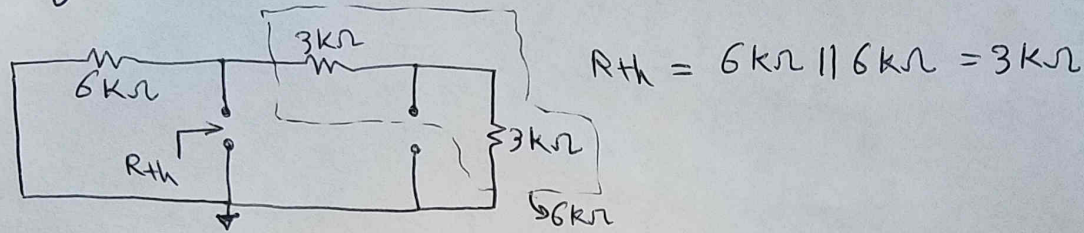Solving for equivalent Norton/Thvenin resistance:




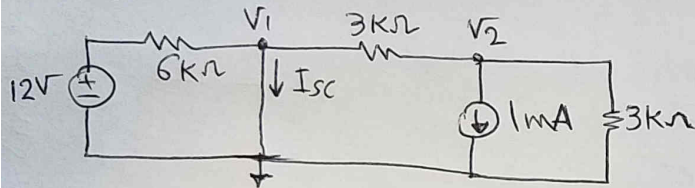Finding the short circuit current ( $I_{sc}$ ):




$$\left. \begin{aligned} V_1 &= \phi \\ \text{KCL @ } V_1: \frac{12 - V_1}{6k\Omega} &= \frac{V_1 - V_2}{3k\Omega} + I_{sc} \\ \text{KCL @ } V_2: \frac{V_2 - V_1}{3k\Omega} + 1\text{mA} + \frac{V_2}{3k\Omega} &= \phi \end{aligned} \right\} \begin{aligned} V_2 &= -1.5\text{V} \\ I_{sc} &= 1.5\text{mA} \end{aligned}$$

→ Equivalent Norton circuit:

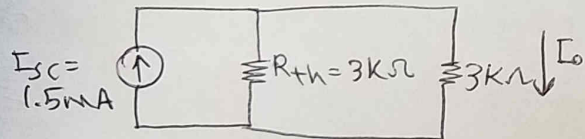

$$I_o = \frac{3k\Omega}{3k\Omega + 3k\Omega} \times I_{sc} = 0.75\text{mA}$$

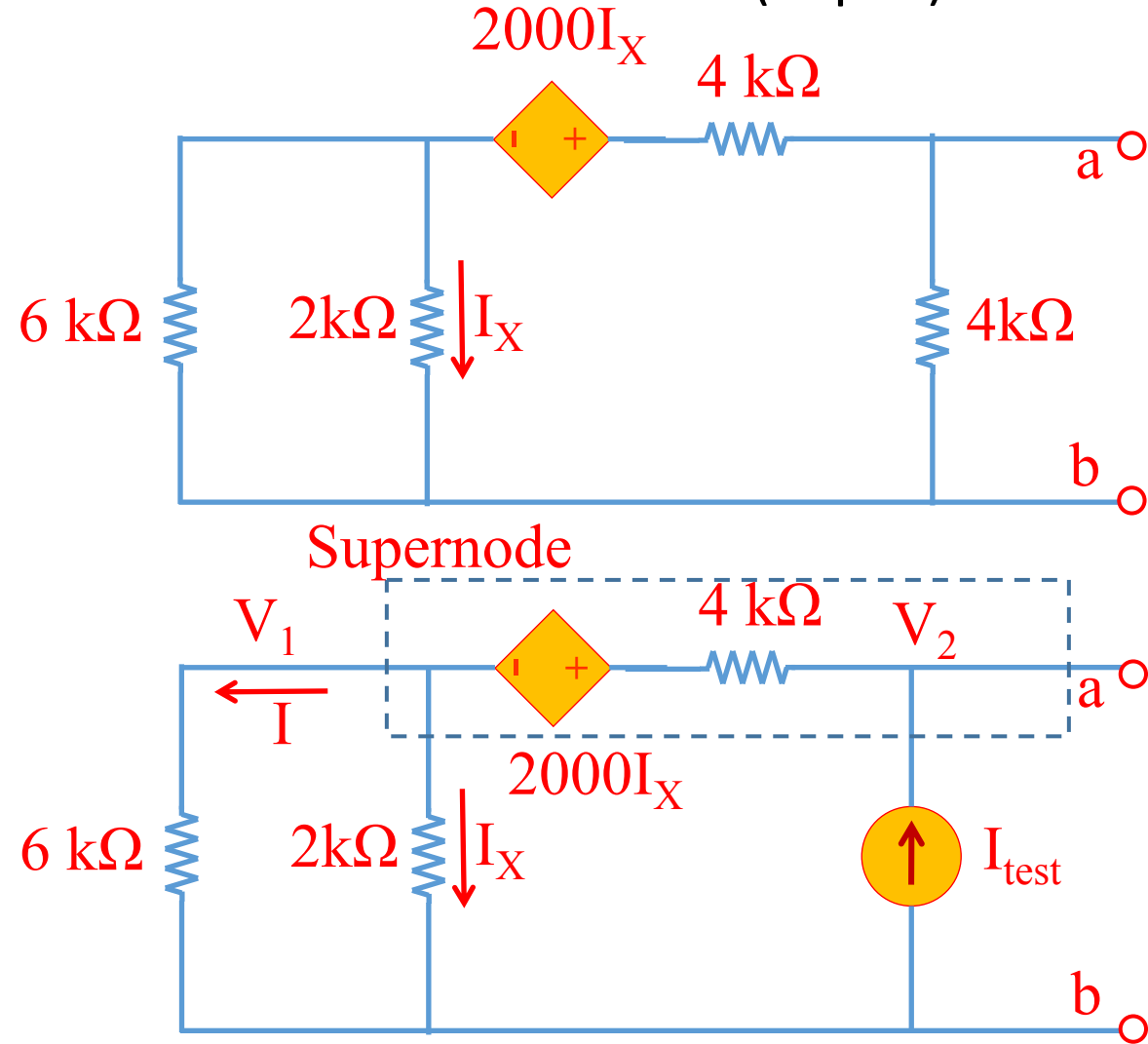Problem 11: Obtain the Thévenin and Norton equivalent network representations as seen from the terminals a-b. (10pts.)



Solution: Note we do not have any independent source, so  $V_{th} = 0$ . We only need to find the Thevenin resistor seen from terminal a-b. To do so, we apply a test current at the port and find the voltage appearing across it ( $V_2$ ). The ratio of this voltage ( $V_2$ ) and the applied current results in resistor  $R$ . We have a resistor parallel to the port ( $4k\Omega$ ). Finally  $R_{th}$  will be  $R \parallel 4k\Omega$ .

KCL at supernode:  $V_1/6k\Omega + V_1/2k\Omega = I_{test}$

$$\rightarrow 2V_1/3k\Omega = I_{test} \rightarrow V_1 = 3k \times I_{test}/2$$

$$V_2 - V_1 = 2000I_X + 4k\Omega \times I_{test} = 2000(V_1/2k\Omega) + 8V_1/3$$

$$\rightarrow V_2 = 14V_1/3 = 7k \times I_{test} \rightarrow V_2/I_{test} = R = 7k\Omega$$

$$\rightarrow R_{th} = 4k\Omega \parallel 7k\Omega = 2.54k\Omega$$