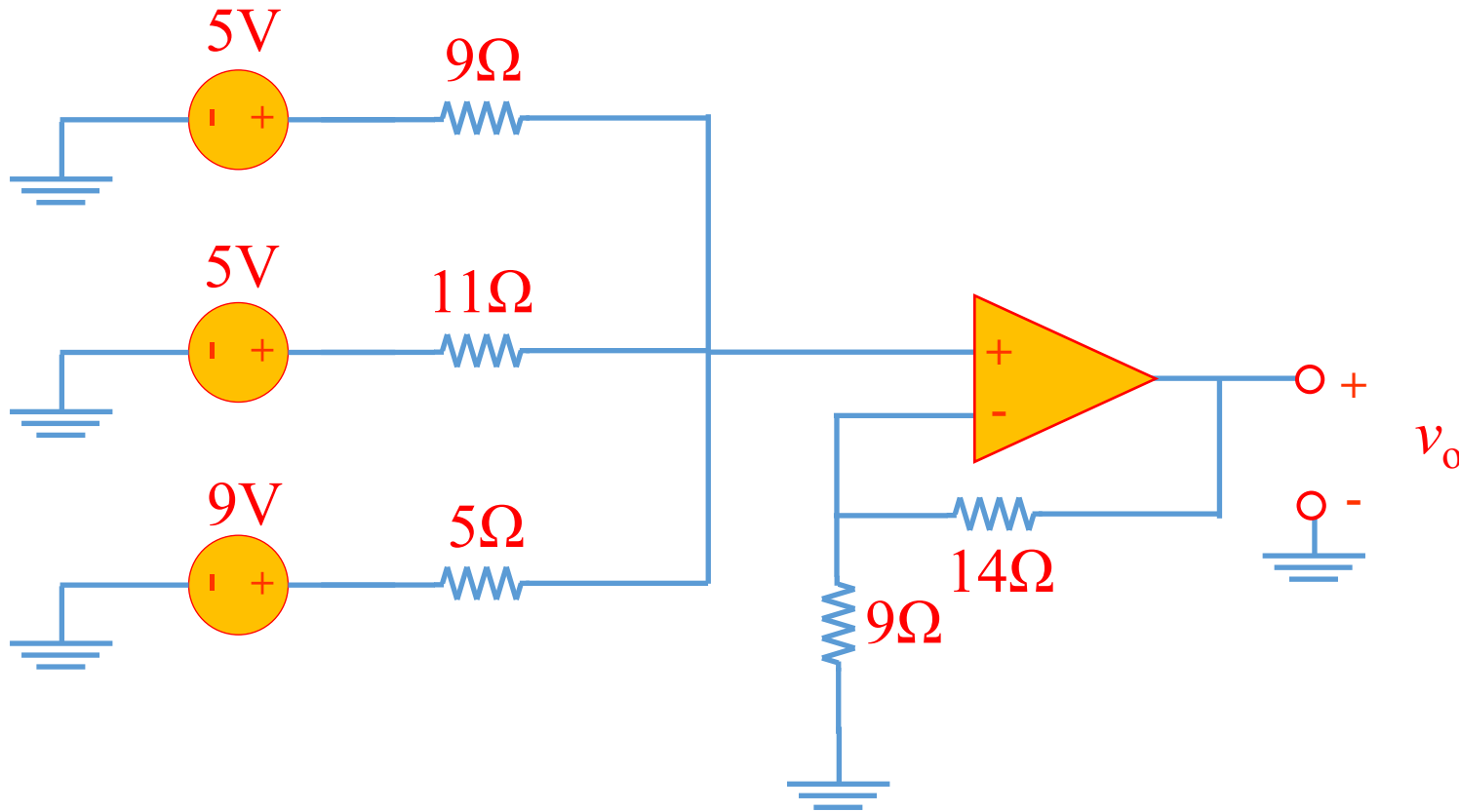


EECS/CSE 70A Network Analysis I

Homework #4

Solution Key

Problem 1: (Ideal Opamp) Find the output voltage v_o (20pts.)



Solution:

Ideal opamp $\rightarrow A = \infty$, opamp input resistance $R_{in} = \infty$ and opamp output resistance $R_o = 0$.

$$\text{KCL at } V_+ : \frac{5-V_+}{9} + \frac{5-V_+}{11} + \frac{9-V_+}{5} = 0 \rightarrow$$


$$V_+ = 7V$$

$A = \infty \rightarrow V_+ = V_- = 7V$ (Virtual ground at the input)

$$\text{KCL at } V_- : \frac{V_-}{9} = \frac{v_o - V_-}{14} \rightarrow v_o = 17.9V$$


Note that since R_{in} is infinity, no current is entering either of the opamp inputs.

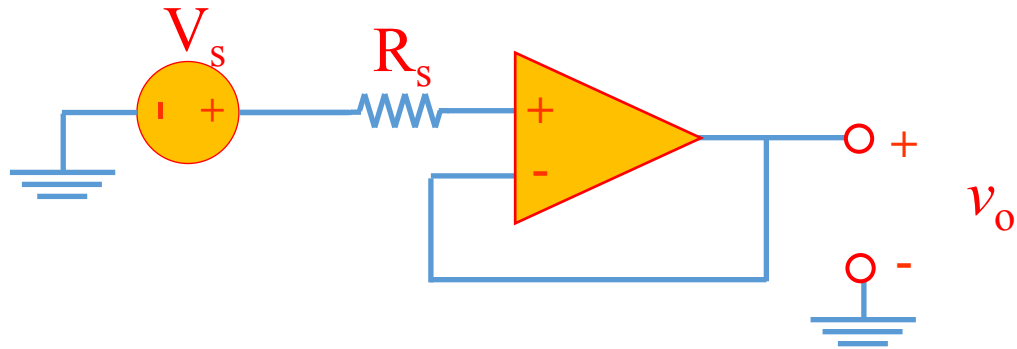Problem 2: Find the equivalent Thevenin output resistance if the opamp is modeled as the circuit in the green box in terms of R_i , R_o and A (10pts.)



Solution:


First we nullify the independent sources. Second we apply a test voltage source at the output and determine how much current is drawn from it. The ratio of the test voltage and the drawn current is the Thevenin resistance.

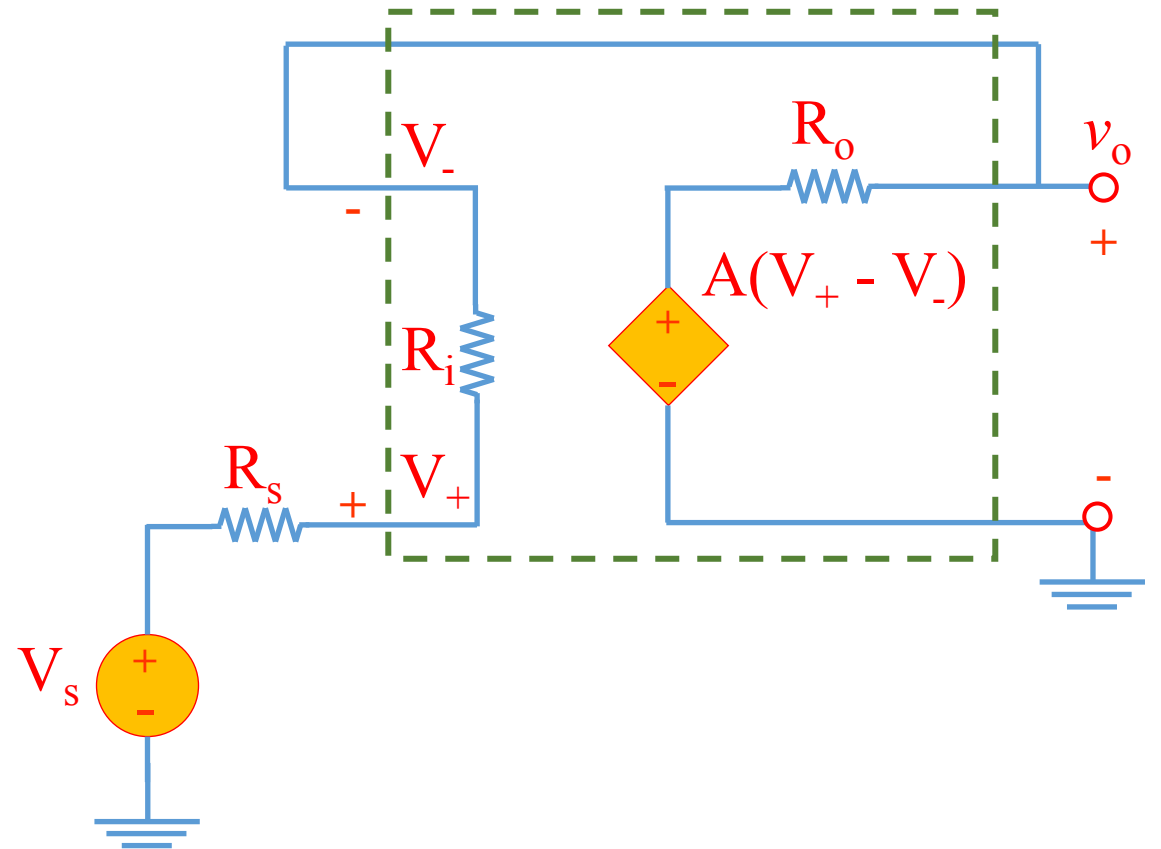

Problem 2: Find the equivalent Thevenin output resistance if the opamp is modeled as the circuit in the green box in terms of R_i , R_o and A (10pts.)

Solution Continued:

The equivalent circuit is shown below:

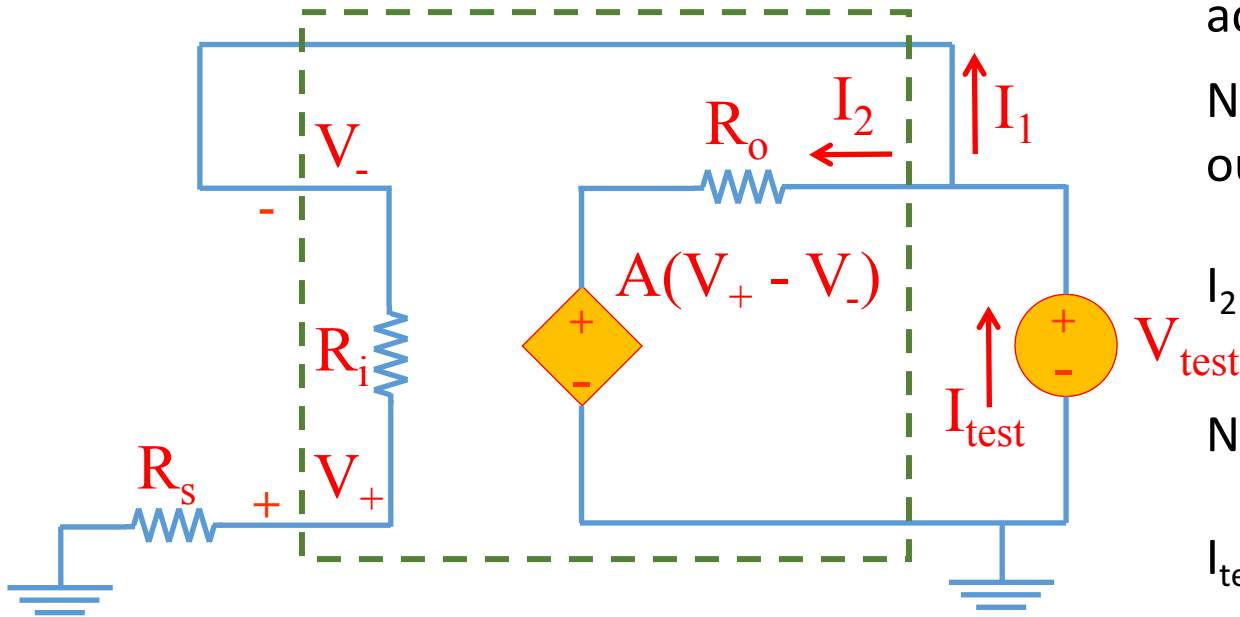

The current passing R_i is $I_1 = V_{test}/(R_i + R_s)$. Therefore, voltage across the R_i is: $V_+ - V_- = \frac{-R_i}{R_i + R_s} V_{test}$

Now we can calculate I_2 (the current flowing into the opamp output):


$$I_2 = [V_{test} - A(V_+ - V_-)]/R_o = \frac{(V_{test} - \frac{-AR_i}{R_i + R_s} V_{test})}{R_o} = \frac{V_{test}(1 + \frac{AR_i}{R_i + R_s})}{R_o}$$

Now from KCL we have:

$$I_{test} = I_1 + I_2 = V_{test} \left[\frac{\left(1 + \frac{AR_i}{R_i + R_s}\right)}{R_o} + \frac{1}{R_i + R_s} \right]$$


$$\rightarrow R_{th} = \frac{V_{test}}{I_{test}} = 1 / \left[\frac{\left(1 + \frac{AR_i}{R_i + R_s}\right)}{R_o} + \frac{1}{R_i + R_s} \right]$$

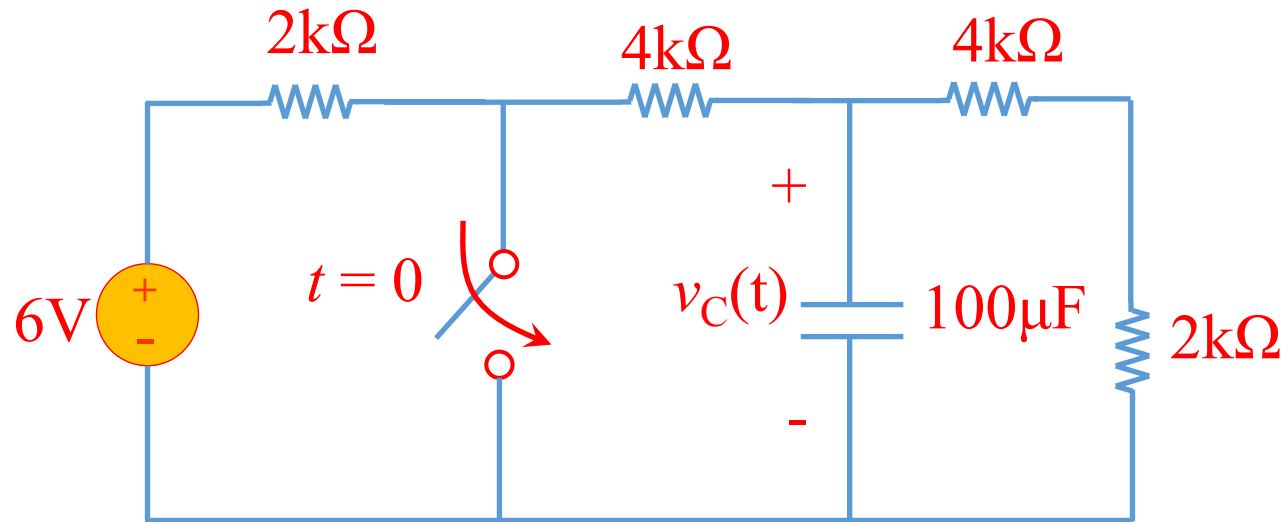Problem 2: (RC circuit) Find the expression of $v_C(t)$ for $t > 0$. What is the circuit time constant after switch is closed? Plot the $v_C(t)$ for $-\infty < t < \infty$ (35pts.)




Solution:

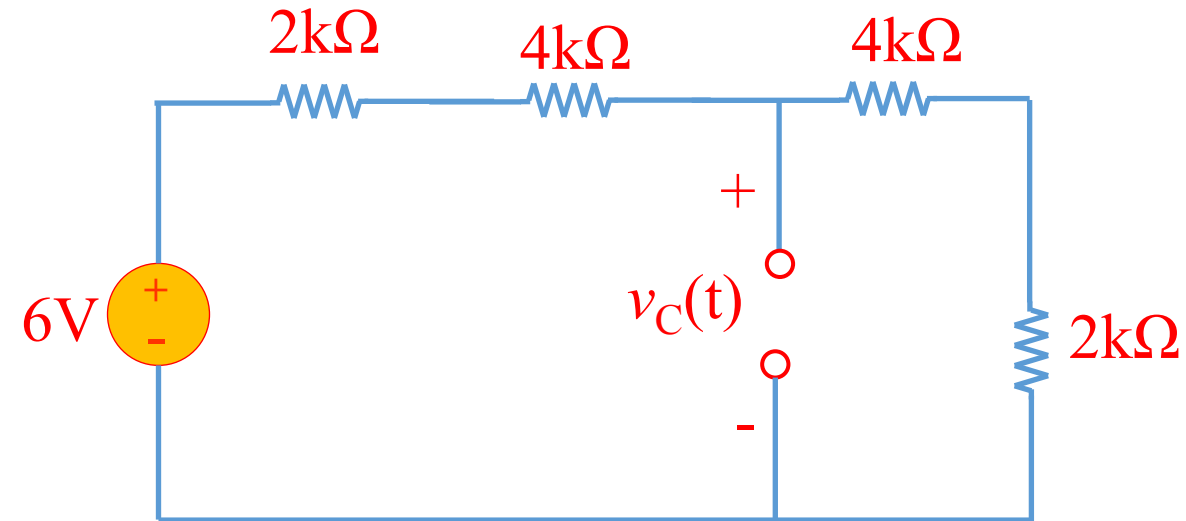At $t < 0$, switch is open and the capacitor is open circuit. The voltage across the capacitor at $t < 0$ can be derived using the equivalent circuit below:




$$\rightarrow v_C(t < 0) = 3V$$

for $t > 0$, switch is closed and the capacitor is getting discharged. The equivalent circuit after switch is closed:

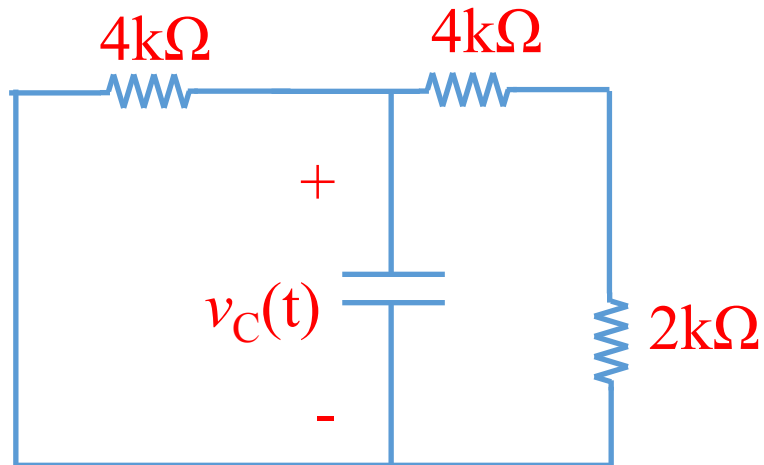

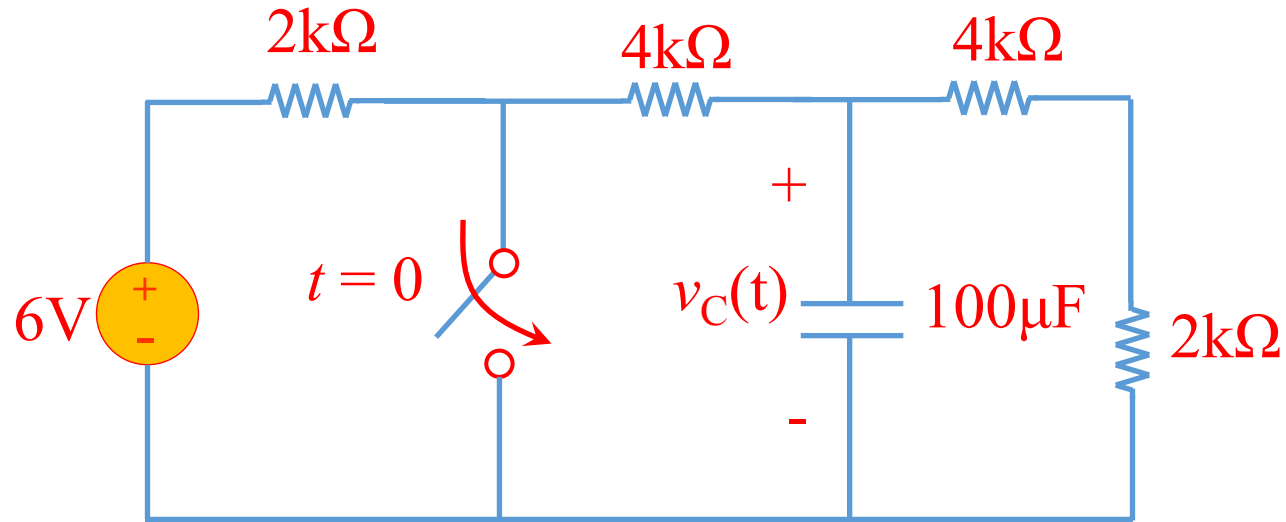Problem 2: (RC circuit) Find the expression of $v_C(t)$ for $t > 0$. What is the circuit time constant after switch is closed? Plot the $v_C(t)$ for $-\infty < t < \infty$ (35pts.)



Solution Continued:

Circuit time constant T is $R_{eq}C$, where R_{eq} is the total resistance seen by the capacitor:

$$R_{eq} = 4 \text{ k}\Omega \parallel (4 \text{ k}\Omega + 2 \text{ k}\Omega) = 2.4 \text{ k}\Omega$$


$$\rightarrow T = 0.24$$

The current through capacitor vanishes, and the voltage decays towards zero at $t = \infty \rightarrow$


$$v_C(t = \infty) = 0$$

$$v_C(t) = v_C(t = \infty) + [v_C(t = 0) - v_C(t = \infty)] e^{\frac{-t}{T}}$$

$$v_C(t) = 3e^{\frac{-t}{0.24}}$$

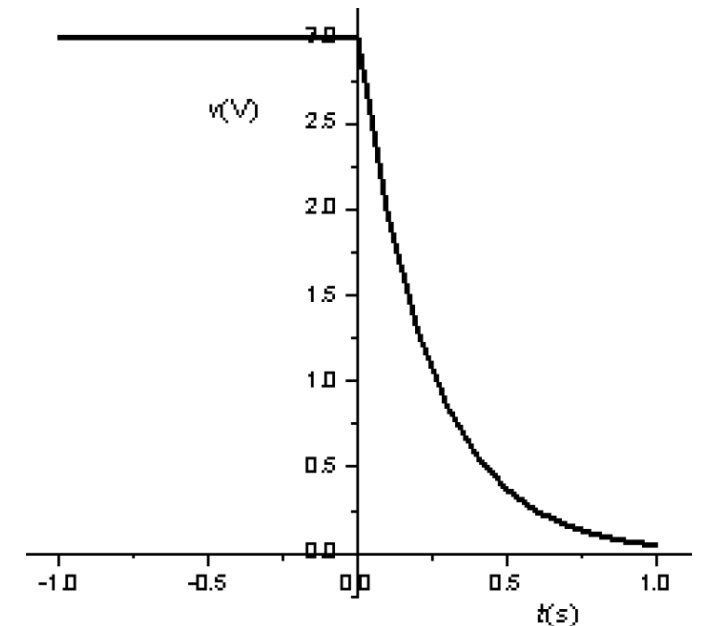

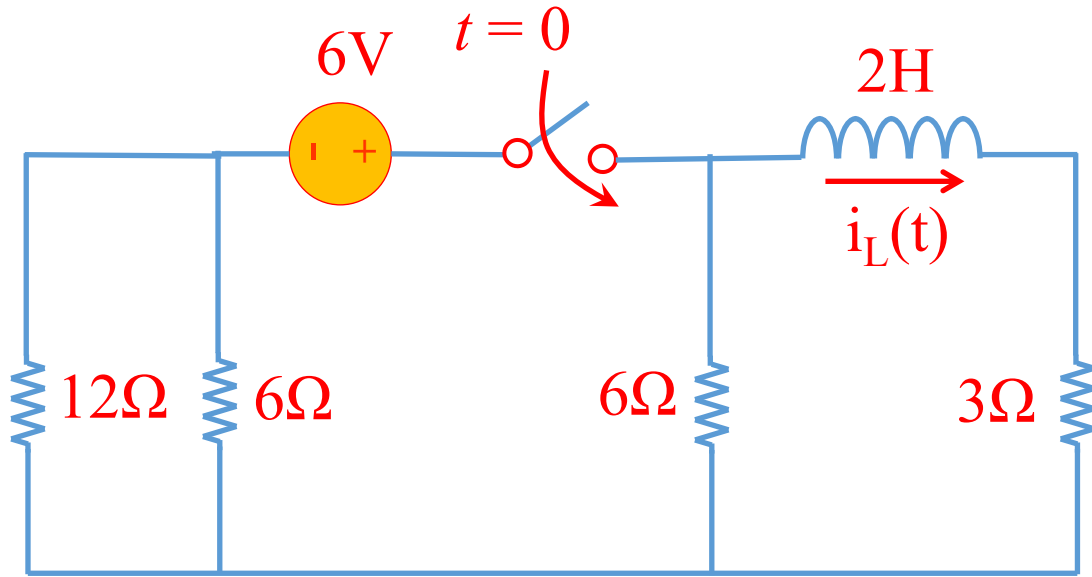
Problem 3: (RL circuit) Find the expression of $i_L(t)$ for $t > 0$. What is the circuit time constant after switch is closed? Plot the $i_L(t)$ for $-\infty < t < \infty$ (35pts.)



Solution:


At $t < 0$, switch is open and the inductor has is discharged so $i_L(t < 0) = 0$.

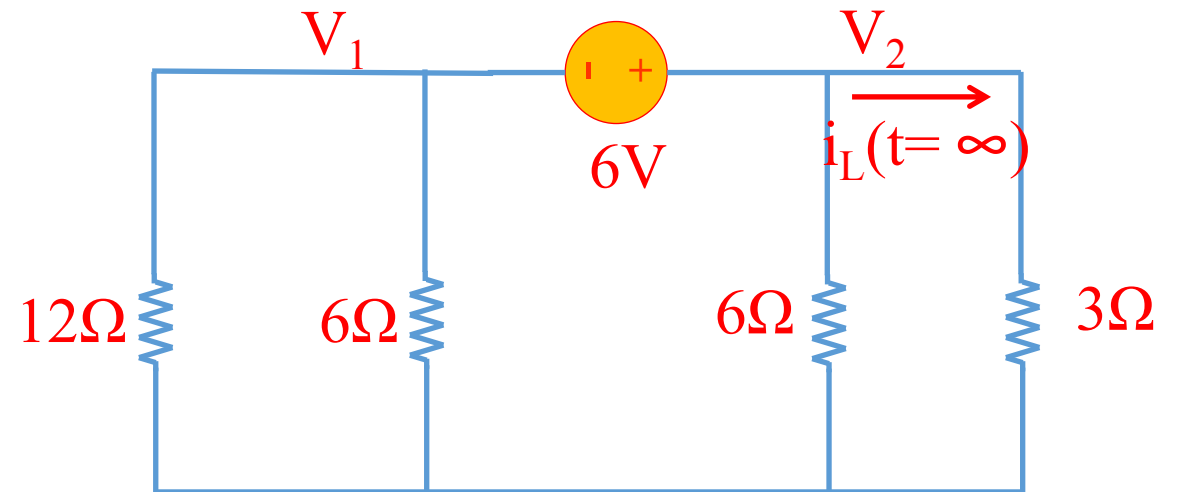After switch closes and at $t = \infty$, the inductor will become short circuit and the equivalent circuit below results:



Using nodal analysis we can find $i_L(t = \infty)$:
 $V_1(1/6 + 1/12) = -V_2(1/6 + 1/3)$, $V_2 = V_1 + 6$
 $\rightarrow V_1 = 4\text{V}$, $V_2 = 2\text{V} \rightarrow i_L(t = \infty) = V_2/3 = 2/3\text{A}$

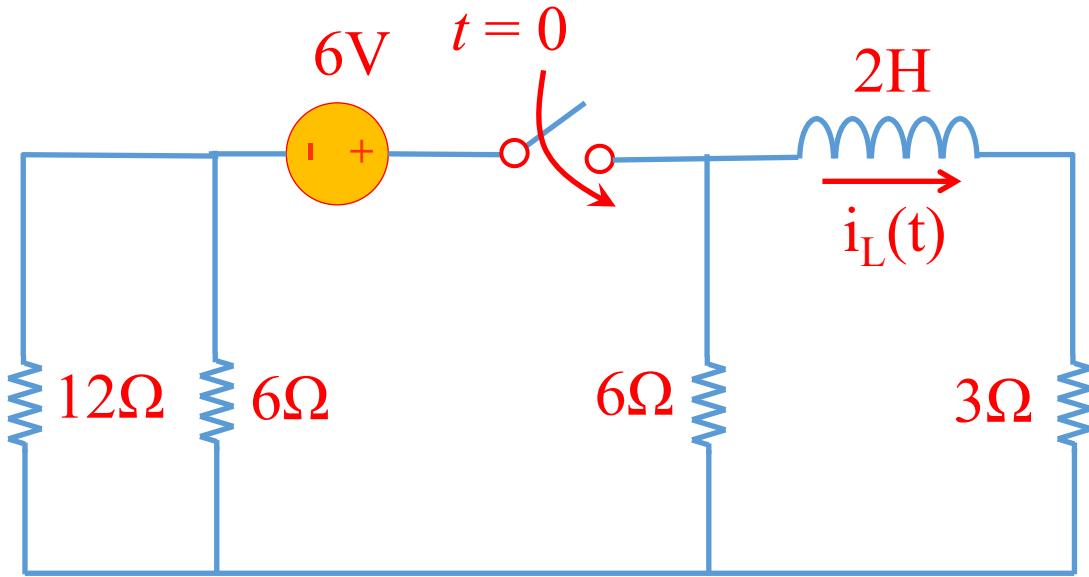Problem 3: (RL circuit) Find the expression of $i_L(t)$ for $t > 0$. What is the circuit time constant after switch is closed? Plot the $i_L(t)$ for $-\infty < t < \infty$ (35pts.)



Solution Continued:

The circuit time constant is $T = L/R_{eq}$ where R_{eq} is the total resistance as seen from the inductor:

$$R_{eq} = 12\Omega \parallel 6\Omega \parallel 6\Omega + 3\Omega = 5.4\Omega$$

$$\rightarrow T = 0.37s$$

$$i_L(t) = i_L(t = \infty) + [i_L(t = 0) - i_L(t = \infty)] e^{-\frac{t}{T}}$$

$$i_L(t) = 2/3 + (-2/3)e^{-\frac{t}{0.37}}$$