

EECS/CSE 70A Network Analysis I

Homework #5


Due on or before

5/23/2017, Tuesday 6.00pm ONLINE ONLY

Problem 1: (Phasor) (40pts)

- a) Given $v(t) = 5\cos(\omega t - \pi/3)$. Find the phasor \mathbf{V} that represents $v(t)$. Express \mathbf{V} as $x+jy$ and as $re^{j\varphi}$
- b) Given $i(t) = 10\sin(3t + \pi/4)$. Find the phasor \mathbf{I} that represents $i(t)$. Express \mathbf{I} as $x+jy$ and as $re^{j\varphi}$
- c) Convert the phasor $\mathbf{V} = 3+7j$ to time domain expression $v(t)$.
- d) Convert the phasor $\mathbf{I} = 16-9j$ to time domain expression $i(t)$.

Problem 2: Find $V_C(t)$. Hint: convert the voltage source into a phasor, then find the voltage phasor for the capacitor, then convert back to the time dependent $V_C(t)$ (30pts)

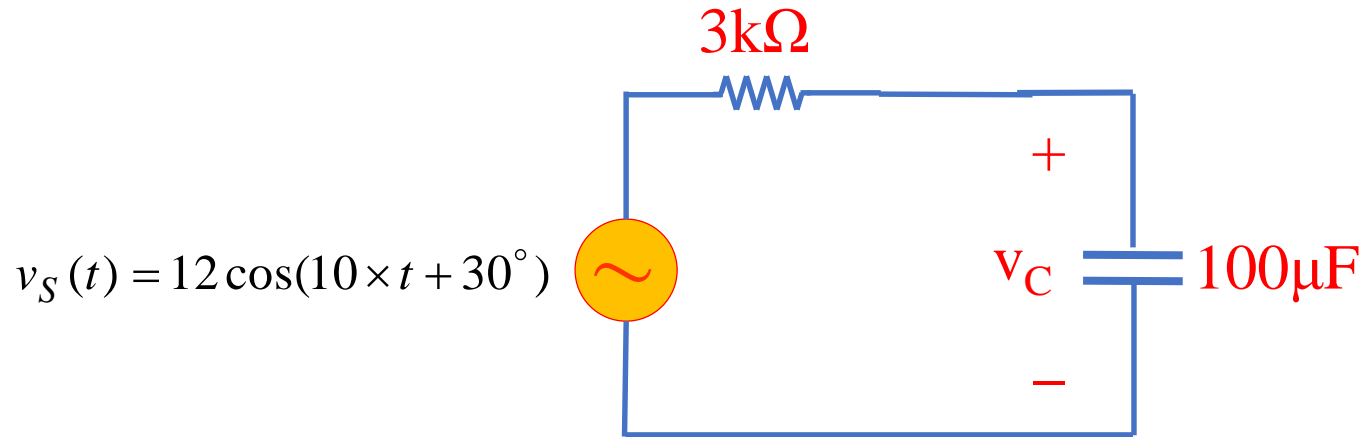

Problem 3: $Z_{eq}(\omega)$ is the equivalent impedance between terminals a-b. (30pts)

Find the parametric expression for $Z_{eq}(\omega)$ as a function of the angular frequency ω and circuit elements (R_1 , R_2 , C and L). You do not need to simplify the expression.

