

EECS/CSE 70A Network Analysis I

Homework #5

Solution Key

Problem 1: (Phasor) (40pts)

- a) Given $v(t) = 5\cos(\omega t - \pi/3)$. Find the phasor \mathbf{V} that represents $v(t)$. Express \mathbf{V} as $x+jy$ and as $re^{j\varphi}$

Phasor: $\mathbf{V} = x + jy = re^{j\varphi} ; x = r \cos \varphi, y = r \sin \varphi$

$$r = 5, \varphi = -\frac{\pi}{3} \Rightarrow \mathbf{V} = 5e^{-j\frac{\pi}{3}}$$

$$\left. \begin{array}{l} x = 5 \cos(-\frac{\pi}{3}) = 2.5 \\ y = 5 \sin(-\frac{\pi}{3}) = -4.33 \end{array} \right\} \Rightarrow \mathbf{V} = 2.5 - j4.33$$

- b) Given $i(t) = 10\sin(3t + \pi/4)$. Find the phasor \mathbf{I} that represents $i(t)$. Express \mathbf{I} as $x+jy$ and as $re^{j\varphi}$

Phasor: $i(t) = 10\sin(3t + \frac{\pi}{4}) = 10\cos(3t + \frac{\pi}{4} - \frac{\pi}{2}) = 10\cos(3t - \frac{\pi}{4})$

$$\mathbf{I} = x + jy = re^{j\varphi} ; x = r \cos \varphi, y = r \sin \varphi$$

$$r = 10, \varphi = -\frac{\pi}{4} \Rightarrow \mathbf{I} = 10e^{-j\frac{\pi}{4}}$$

$$\left. \begin{array}{l} x = 10 \cos(-\frac{\pi}{4}) = 7.07 \\ y = 10 \sin(-\frac{\pi}{4}) = -7.07 \end{array} \right\} \Rightarrow \mathbf{I} = 7.07 - j7.07$$

c) Convert the phasor $\mathbf{V} = 3+7j$ to time domain expression $v(t)$.

$$\left. \begin{array}{l} |\mathbf{V}| = |3 + j7| = \sqrt{9 + 49} = 7.6158 \\ \angle \mathbf{V} = \arctan\left(\frac{7}{3}\right) = 1.16 \text{ rad} \end{array} \right\} \Rightarrow \mathbf{V} = 7.6158e^{j1.16}$$


$$v(t) = \operatorname{Re}\{\mathbf{V}e^{j\omega t}\} = 7.6158 \cos(\omega t + 1.16)$$

d) Convert the phasor $\mathbf{I} = 16-9j$ to time domain expression $i(t)$.

$$\left. \begin{array}{l} |\mathbf{I}| = |16 - j9| = \sqrt{256 + 81} = 18.35 \\ \angle \mathbf{I} = \arctan\left(\frac{-9}{16}\right) = -0.51 \text{ rad} \end{array} \right\} \Rightarrow \mathbf{I} = 18.35e^{-j0.51}$$

$$i(t) = \operatorname{Re}\{\mathbf{I}e^{j\omega t}\} = 18.35 \cos(\omega t - 0.51)$$

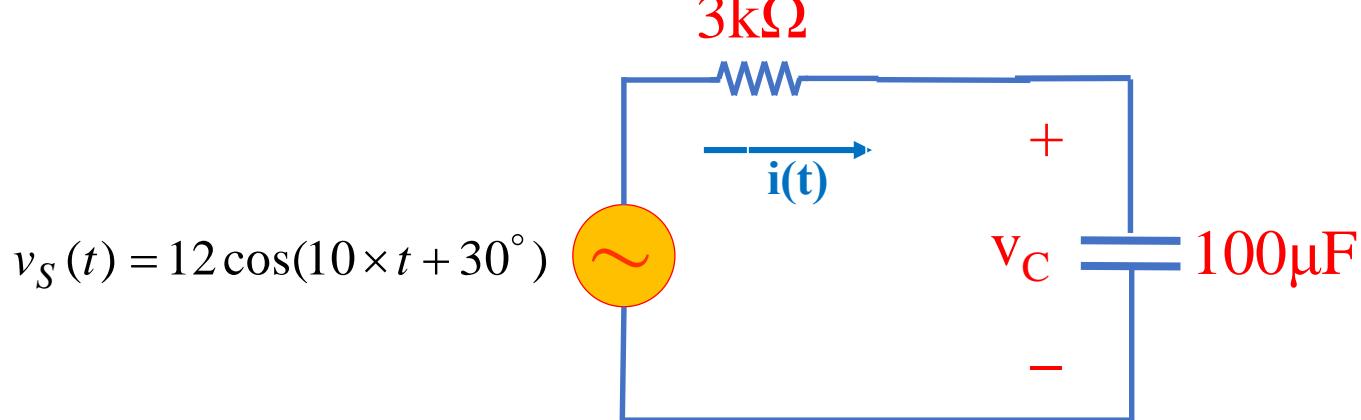Problem 2: Find $V_C(t)$. Hint: convert the voltage source into a phasor, then find the voltage phasor for the capacitor, then convert back to the time dependent $V_C(t)$ (30pts)




Convert to the Phasor domain:

$$Z_c = \frac{1}{j\omega c} = \frac{1}{j10 \times 100 \times 10^{-6}} = -j1000\Omega$$

$$Z_{eq} = 3000 - j1000 \quad (\Omega)$$

$$v_s(t) = 12 \cos(10t + 30^\circ) \Rightarrow \mathbf{V}_s = 12e^{j\frac{\pi}{6}} \quad \omega = 10(\text{rad/s})$$

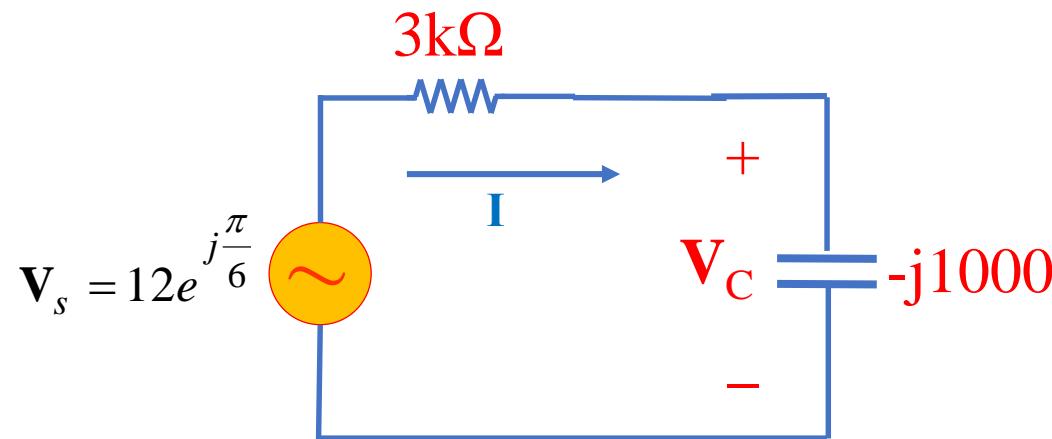
$$\mathbf{I} = \frac{\mathbf{V}_s}{Z_{eq}} \rightarrow \mathbf{V}_c = \mathbf{I} \times Z_c = \frac{Z_c}{Z_{eq}} \mathbf{V}_s = \frac{-j1000}{3000 - j1000} 12e^{-j\frac{\pi}{6}} = 3.7949e^{-j0.7254} \text{ V}$$




$$v_c(t) = \text{Re}\{\mathbf{V}_c e^{j\omega t}\} = \text{Re}\{3.7949e^{-j0.7254} e^{j10t}\} \\ = 3.7949 \cos(10t - 0.7254)$$

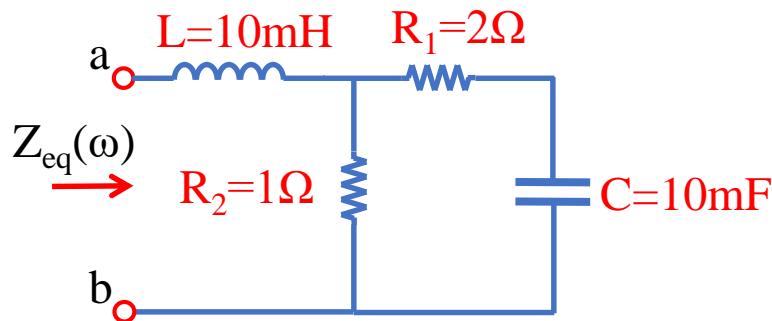Problem 3: $Z_{eq}(\omega)$ is the equivalent impedance between terminals a-b. (30pts)

Find the parametric expression for $Z_{eq}(\omega)$ as a function of the angular frequency ω and circuit elements (R_1 , R_2 , C and L). You do not need to simplify the expression.



Phasor Domain:

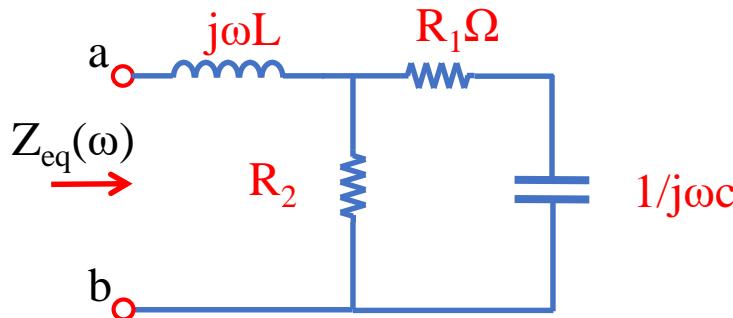

$$\begin{aligned}
 Z_{eq} &= j\omega L + [R_2 \parallel (R_1 + \frac{1}{j\omega C})] \\
 &= j\omega L + R_2 \parallel \frac{1 + j\omega C R_1}{j\omega C} \\
 &= j\omega L + \frac{R_2 + j\omega C R_1 R_2}{1 + j\omega C (R_1 + R_2)}
 \end{aligned}$$