

Q1	Q2	Q3	Q4	Q5	Q6	Total
/15	/30	/15	/15	/10	/15	/100

EECS / CSE 70A Final Exam

DO NOT BEGIN THE EXAM UNTIL YOU ARE TOLD TO DO SO.

Print your name on all pages.

Write your solutions in clear steps with concise explanations.

radians :	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$	π
sin	$\frac{\sqrt{0}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{4}}{2}$	0
cos	$\frac{\sqrt{4}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{0}}{2}$	-1
tan	$\frac{\sqrt{0}}{\sqrt{4}}$	$\frac{\sqrt{1}}{\sqrt{3}}$	$\frac{\sqrt{2}}{\sqrt{2}}$	$\frac{\sqrt{3}}{\sqrt{1}}$	DNE	0


where $\sqrt{\cdot}$ always denotes the positive square root, and DNE means does not exist.

PROBLEM 1: (20 points)

Find phasor of I_1 , I_2 and V_C and $V_C(t)$. Assume $\omega=10^7$ rad/s.

(express your answers for phasor of I_1 , I_2 and V_C in polar form $re^{j\theta}$)

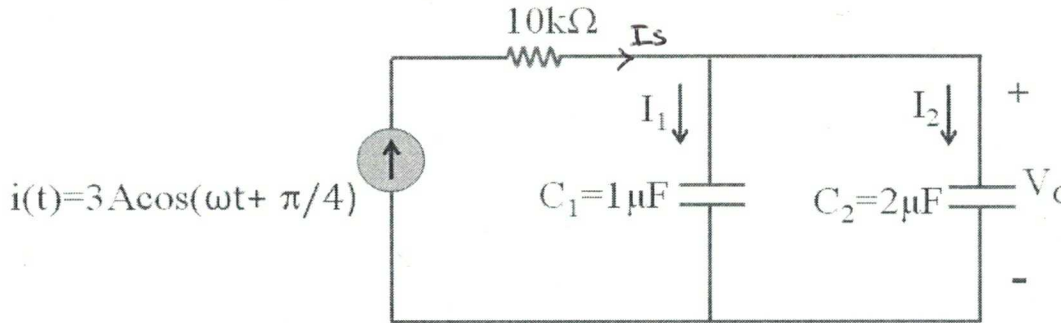(express all angles in **radians** not degrees)



I_1	$1 e^{j\pi/4}$ [A]
I_2	$2 e^{j\pi/4}$ [A]
V_C	$0.1 e^{-j\pi/4}$ [V]
$V_C(t)$	$0.1 \cos(10^7 t - \pi/4)$

$$I_s = 3 e^{j\pi/4}$$

$$I_1 = I_s \cdot \frac{Z_{C2}}{Z_{C1} + Z_{C2}} = I_s \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = I_s \frac{C_1}{C_1 + C_2} = \frac{1}{3} I_s$$

$$I_1 = 1 e^{j\pi/4} \text{ [A]} \quad (3)$$

$$I_2 = I_s \frac{Z_{C1}}{Z_{C1} + Z_{C2}} \rightarrow I_2 = \frac{C_2}{C_1 + C_2} I_s \rightarrow I_2 = 2 e^{j\pi/4} \text{ [A]} \quad (3)$$


$$V_C = I_1 \cdot Z_{C1} \text{ or } I_2 Z_{C2} \rightarrow V_C = I_1 \cdot Z_{C1} = 1 e^{j\pi/4} \cdot \frac{1}{j 10^7 10^{-6}} = -j 0.1 e^{j\pi/4} \rightarrow$$

$$V_C = 0.1 e^{-j\pi/4} \text{ [V]} \quad (3)$$

$$V_C(t) = 0.1 \cos(10^7 t - \pi/4) \quad (2)$$

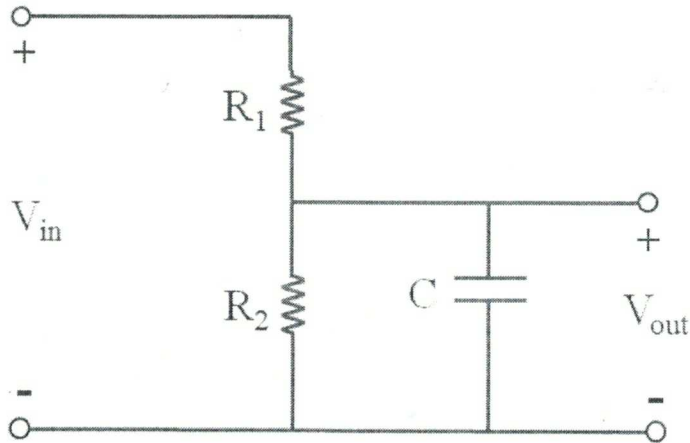PROBLEM 2: (30 points)

In the Circuit below the transfer function is defined as $\mathbf{H}(\omega) = \frac{V_{out}}{V_{in}}$. Find the following.



a) Find $\mathbf{H}(\omega)$ in terms of R_1 , R_2 and C .

$$H(\omega) = \frac{\frac{1}{j\omega C} \parallel R_2}{\left(\frac{1}{j\omega C} \parallel R_2\right) + R_1} = \frac{\frac{R_2}{1+j\omega C R_2}}{\frac{R_2}{1+j\omega C R_2} + R_1}$$

$$\frac{1}{j\omega C} \parallel R_2 = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1+j\omega C R_2}$$

$$H(\omega) = \frac{R_2}{R_2 + R_1(1+j\omega C R_2)} = \frac{R_2}{R_2 + R_1 + j\omega C R_1 R_2}$$

or $H(\omega) = \frac{1}{\left(1 + \frac{R_1}{R_2}\right) + j\omega C R_1}$ or $\frac{R_2}{R_2 + R_1 + j\omega C R_1 R_2}$

$\mathbf{H}(\omega)$	$\frac{R_2}{(R_1 + R_2) + j\omega C R_1 R_2}$
----------------------	---

b) Find $|\mathbf{H}(\omega)|$ in terms of R_1 , R_2 and C .

$$H(\omega) = \frac{R_2}{\sqrt{(R_1 + R_2)^2 + (\omega C R_1 R_2)^2}} \quad (5)$$

or

$$\frac{1}{\sqrt{\left(1 + \frac{R_1}{R_2}\right)^2 + (\omega C R_1)^2}}$$

$ \mathbf{H}(\omega) $	$= \frac{R_2}{\sqrt{(R_1 + R_2)^2 + (\omega C R_1 R_2)^2}}$
------------------------	---

c) Find $\angle \mathbf{H}(\omega)$ in terms of R_1 , R_2 and C .


$$\angle H(\omega) = -\text{Arctg}^{-1} \left(\frac{\omega C R_1 R_2}{R_1 + R_2} \right) \quad (5)$$

or

$$\angle H(\omega) = -\text{Arctg}^{-1} \left(\frac{\omega C R_1 R_2}{1 + \frac{R_1}{R_2}} \right)$$

$\angle \mathbf{H}(\omega)$	$= -\text{Arctg}^{-1} \left(\frac{\omega C R_1 R_2}{R_1 + R_2} \right)$
-----------------------------	--

d) Plot $|\mathbf{H}(\omega)|$ on lin-lin plot. Mark important points on the axes.

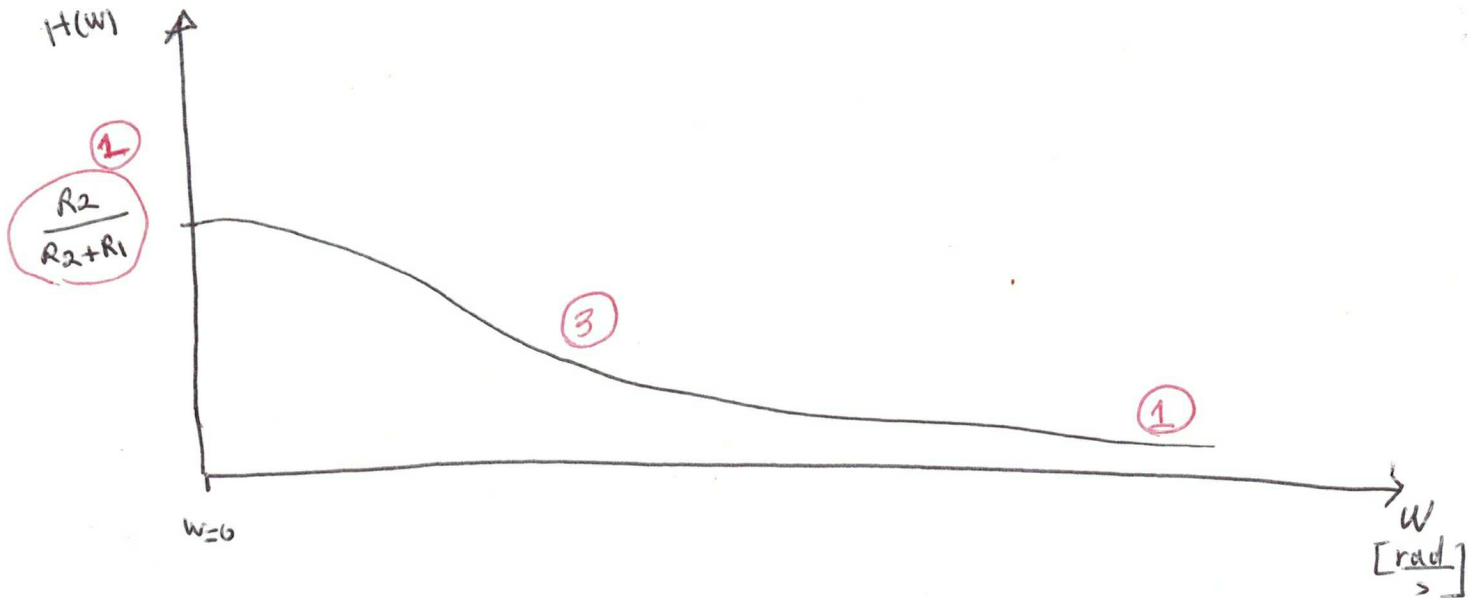

e) What is the value of $|\mathbf{H}(\omega)|$ at $\omega = 0$ and at $\omega \rightarrow \infty$ in terms of R_1 , R_2 and C .

$$H(0) = \frac{R_2}{R_2 + R_1}$$


$$\lim_{\omega \rightarrow \infty} H(\omega) = 0$$

$ \mathbf{H}(0) $	$\frac{R_2}{R_1 + R_2}$	(2.5)
$\lim_{\omega \rightarrow \infty} \mathbf{H}(\omega) $	0	(2.5)

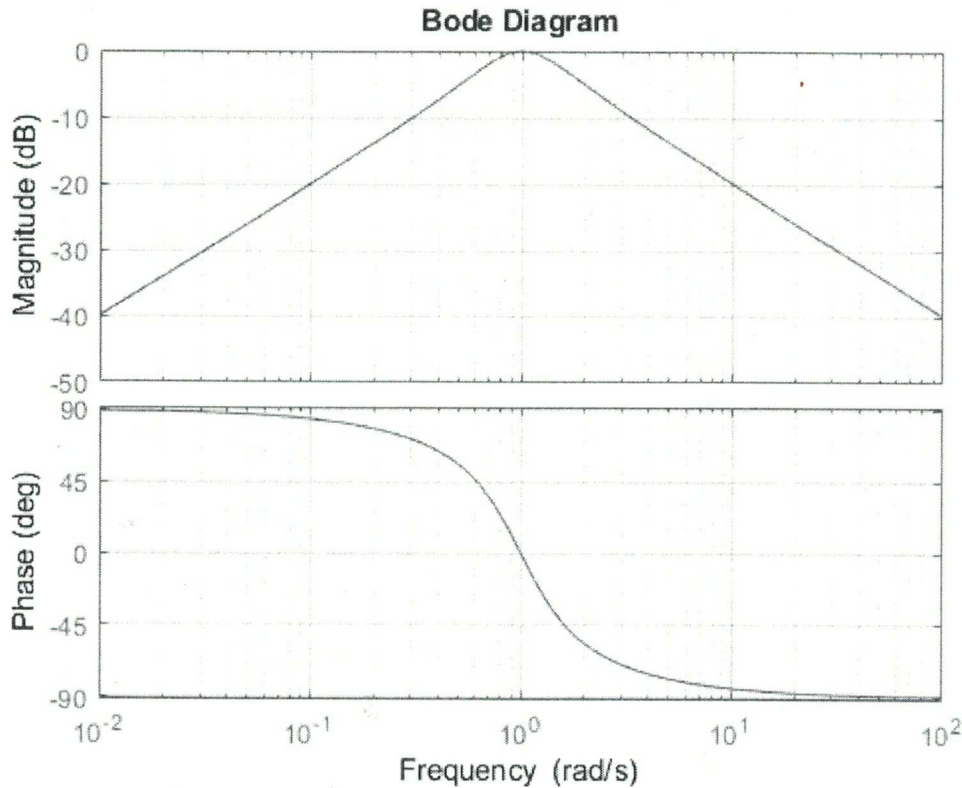PROBLEM 3: (15 points)

The Bode plots of the transfer function is given below, find $V_{out}(t)$ for the following $V_{in}(t)$.

$$V_{in}(t) = 1 \text{ mV} \cos\left(10^{-2} \frac{\text{rad}}{\text{s}} t + \frac{\pi}{4}\right) + 10 \text{ mV} \cos\left(10^0 \frac{\text{rad}}{\text{s}} t + \frac{\pi}{4}\right) + 100 \text{ mV} \cos\left(10^{+2} \frac{\text{rad}}{\text{s}} t + \frac{\pi}{4}\right)$$



*

$$V_{in1}(t) = 1 \text{ mV} \cos\left(10^{-2} t + \frac{\pi}{4}\right) \xrightarrow{\text{Phasor}} V_{in1} = 10^{-3} e^{+j\frac{\pi}{4}}$$

$$20 \log(|H(\omega)|_{\omega=10^{-2}}) = -40 \text{ dB} \rightarrow |H(\omega)|_{\omega=10^{-2}} = 10^{-2}$$

$$\angle H(\omega)|_{\omega=10^{-2}} = 90^\circ$$

$$H(\omega)|_{\omega=10^{-2}} = 10^{-2} e^{+j\frac{\pi}{2}} \quad (2)$$

$$V_{out1} = H(\omega)|_{\omega=10^{-2}} \cdot V_{in1} = 10^{-2} e^{+j\frac{\pi}{2}} \cdot 10^{-3} e^{+j\frac{\pi}{4}} = 10^{-5} e^{+j\frac{3\pi}{4}} \quad (2)$$

$$V_{out1}(t) = 10^{-5} \text{ V} \cos\left(10^{-2} t + \frac{3\pi}{4}\right) \quad (1)$$

$$* V_{in2} = 10 \text{ mV} e^{j\frac{\pi}{4}} \text{ or } 10^{-2} e^{j\frac{\pi}{4}}$$

$$20 \log |H(\omega)| \Big|_{\omega=10^0} = 0 \text{ dB} \rightarrow |H(10^0)| = 1 \rightarrow \boxed{H(\omega) \Big|_{\omega=10^0} = 1} \quad (2)$$

$$\Delta H(10^0) = 0^\circ$$

$$V_{out2} = V_{in2} \cdot H(\omega) \Big|_{\omega=10^0} = 10^{-2} e^{j\frac{\pi}{4}} \quad (2)$$

$$V_{out2}(t) = 10^{-2} \cos(10^0 t + \frac{\pi}{4}) \text{ or } 10 \text{ mV} \cos(10^0 t + \frac{\pi}{4}) \quad (1)$$

$$* V_{in3} = 100 \text{ mV} e^{j\frac{\pi}{4}} \text{ or } 10^{-1} e^{j\frac{\pi}{4}}$$

$$20 \log |H(\omega)| \Big|_{\omega=10^2} = -40 \text{ dB} \rightarrow |H(\omega) \Big|_{\omega=10^2} = 10^{-2} \rightarrow \boxed{H(\omega) \Big|_{\omega=10^2} = 10^{-2} e^{-j\frac{\pi}{2}}} \quad (2)$$

$$\Delta H(\omega) \Big|_{\omega=10^2} = -90^\circ$$

$$V_{out3} = V_{in3} \cdot H(\omega) \Big|_{\omega=10^2} = 10^{-3} e^{-j\frac{\pi}{2}} \quad (2)$$


$$V_{out3}(t) = 10^{-3} \cos(10^2 t - \frac{\pi}{4}) \text{ or } 1 \text{ mV} \cos(10^2 t - \frac{\pi}{4}) \quad (1)$$

$$V_{out}(t) = V_{out1}(t) + V_{out2}(t) + V_{out3}(t)$$


$V_{out}(t)$	$10^{-5} \cos(10^{-2} t + \frac{3\pi}{4}) + 10^{-2} \cos(10^0 t + \frac{\pi}{4}) + 10^{-3} \cos(10^2 t - \frac{\pi}{4})$
--------------	--

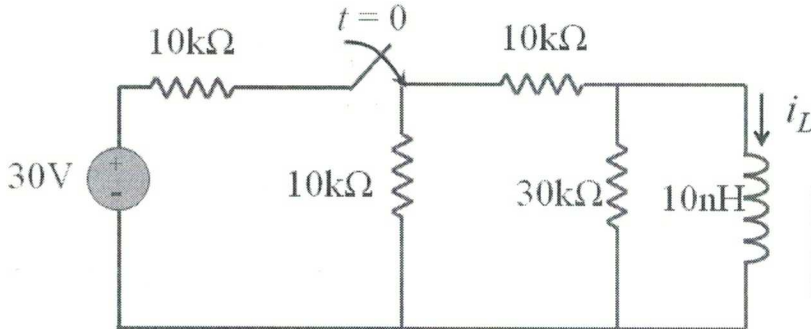PROBLEM 4: (15 points)



In the circuit below the switch closes at $t=0$. Find $i_L(t)$.



$i_L(t)$	$(1 - e^{-\frac{t}{10^{-12}}}) \text{ [mA]}$
----------	--

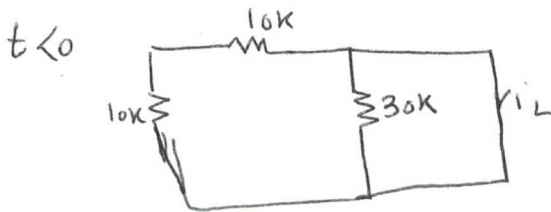


$i_L(0) = 0$ (3)

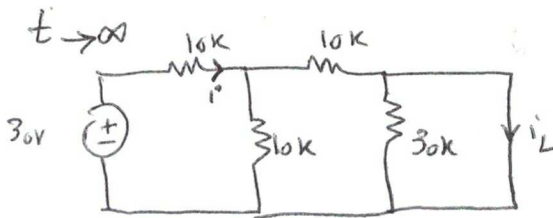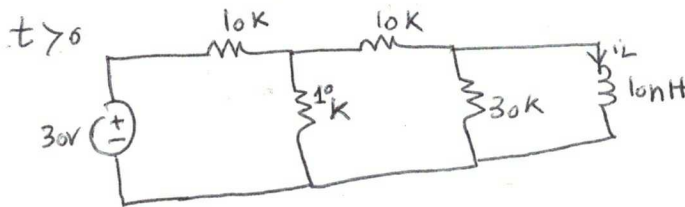

$i = \frac{30V}{10k + (10k \parallel 10k)} = 2 \text{ mA}$

$i_L(\infty) = \frac{10k}{10k + 10k} \times i = 1 \text{ mA}$ (5)

$i_L(\infty) = 1 \text{ mA}$

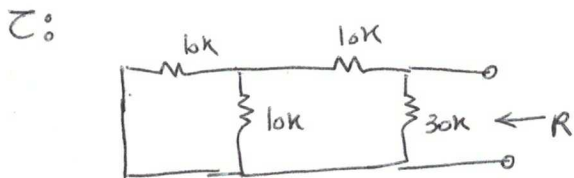

$R = 30k \parallel [10k + (10k \parallel 10k)] = 30k \parallel 15k = 10k\Omega$ (3)

$\tau = \frac{L}{R} = \frac{10 \text{ nH}}{10 \text{ k}\Omega} = 10^{-12} \text{ s} = 1 \text{ ps}$


$\tau = 10^{-12} \text{ s} = 1 \text{ ps}$

$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{t}{\tau}}$

$i_L(t) = (1 - e^{-\frac{t}{10^{-12}}}) \text{ [mA]}$ (2)

POBLEM 5: (10 points)

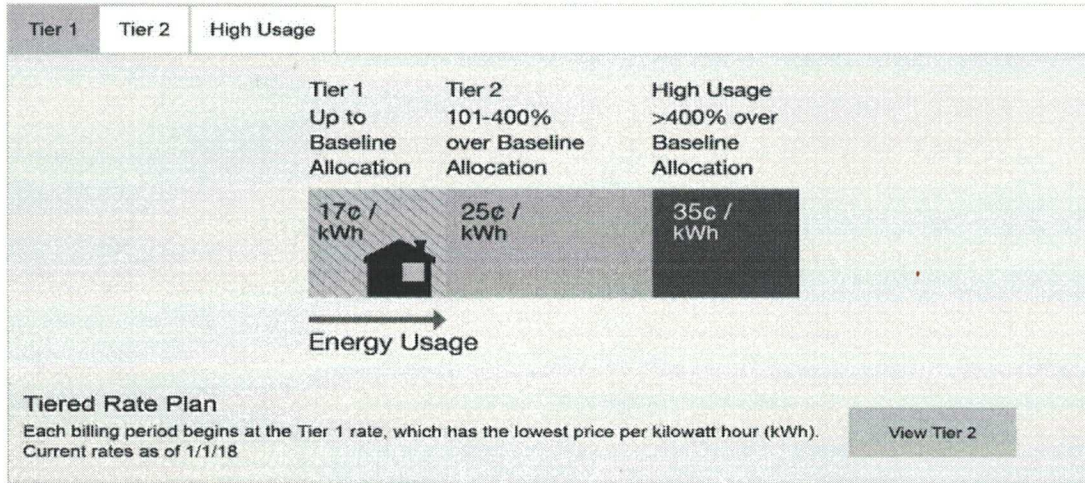Shown below is the Southern California Edison rate for electricity.



- a) How much money does it cost to run a **100 W** light bulb for 1 month?
 Assume your household is frugal with electricity usage, so you are in Tier 1.

$$\text{Energy for 1 month} = P \cdot t = 100\text{W} \times 24\text{h} \times 30 = 24 \times 3 \text{ kWh} = \boxed{72 \text{ kWh}} \text{ (3)}$$

$$\text{Cost} = 72 \text{ kWh} \times \frac{17 \text{¢}}{\text{kWh}} = 1224 \text{¢} = \cancel{1224 \text{¢}} = \boxed{12.24 \text{ \$}} \text{ (1)}$$

Monthly cost of running 1 light bulb	1224¢ or 12.24\$
--------------------------------------	------------------

- b) If you only use this light bulb, would you still be in the lowest tier? Assume that the tier 1 baseline allocation is **400 kWh** per month.

yes because $72 \text{ kWh} < 400 \text{ kWh}$ (1)

- c) What is the minimum number light bulbs you need to use to be in tier 2? Assume that the light bulbs are on 24/7 and tier 1 baseline allocation is **400 kWh** per month.

each light bulb as calculate in section a, consumes 72 kWh per month. In order to be in Tier 2 we need to consume more than 400 kWh .

$$n \cdot 72 \text{ kWh} > 400 \text{ kWh} \rightarrow n > \frac{400 \text{ kWh}}{72 \text{ kWh}} = \boxed{5.5} \text{ (3)}$$

The minimum number of light bulbs is $n = \boxed{6}$ (3)
(if $n=6$ is provided + full grade should be assigned)

Number of light bulbs	6
-----------------------	---


PROBLEM 6: (15 points)

Find the Thevenin equivalent circuit at terminals AB by finding V_{oc} and I_{sc} .

Assume $\omega = 10^3 \frac{rad}{s}$. $V_{oc} = V_{AB}$ (open) and $I_{sc} = I_{AB}$ (short A to B).


(express your answers for phasors in polar form $re^{j\theta}$)

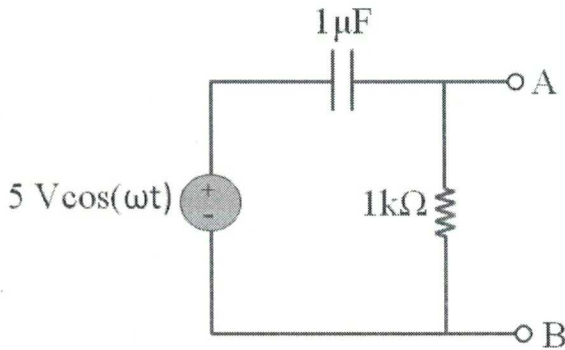(express all angles in **radians** not degrees)




V_{oc}	$\frac{5}{2} \sqrt{2} e^{j \frac{\pi}{4}}$ [V]
I_{sc}	$5 \text{mA} e^{j \frac{\pi}{2}}$
V_{Th}	$\frac{5}{2} \sqrt{2} e^{j \frac{\pi}{4}}$ [V]
Z_{Th}	$\frac{\sqrt{2}}{2} e^{-j \frac{\pi}{4}}$ [kΩ]
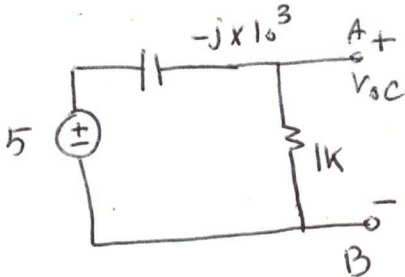
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j 10^3 \times 10^{-6}} = \frac{10^3}{j} = -j 10^3 \Omega \quad (3)$$



$$V_{oc} = \frac{1k}{1k + (-j \times 10^3)} \cdot 5 = 5 \times \frac{1}{1-j}$$
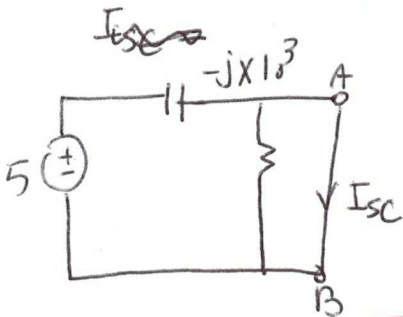
$$V_{oc} = \frac{5(1+j)}{2} = \frac{5}{2} \cdot \sqrt{2} e^{j \frac{\pi}{4}} \quad (3)$$



$$I_{sc} = \frac{5}{-j \times 10^3} = 5 \times 10^{-3} j = 5 \text{mA} e^{j \frac{\pi}{2}} \quad (3)$$

$$V_{th} = V_{oc} = \frac{5}{2} \sqrt{2} e^{j \frac{\pi}{4}} \quad (2)$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{5}{2} \sqrt{2} e^{j \frac{\pi}{4}}}{5 \times 10^{-3} e^{j \frac{\pi}{2}}} = \frac{\sqrt{2}}{2} \times 10^3 e^{-j \frac{\pi}{4}} \Omega$$

or (3)

$$\frac{\sqrt{2}}{2} e^{-j \frac{\pi}{4}} \text{ k}\Omega$$