

Q1	Q2	Q3	Q4	Q5	Total
/10	/10	/40	/30	/10	/100

EECS / CSE 70A Midterm Exam #1

DO NOT BEGIN THE EXAM UNTIL YOU ARE TOLD TO DO SO.

Print your name on all pages.

Write your solutions in clear steps with concise explanations.

PROBLEM 1: (10 points) BITCOIN MINING


What is the hourly profit or loss if you spend money only on electricity with the Antminer S9 to mine bitcoin? Show your work!

Hourly income (mining) = € 36

Hourly cost (electricity) = € 22.4


Hourly profit/loss (circle profit or loss) = € 13.9

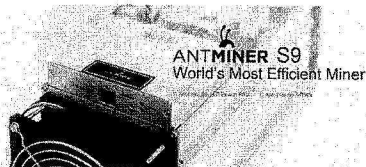- Hash Rate 13TH/s (this is a measure of the number of hash “computations” per second the S9 can perform). Recall T=tera=10¹²



- Power Consumption 1300W
- Assume Bitcoin Value of 10000\$

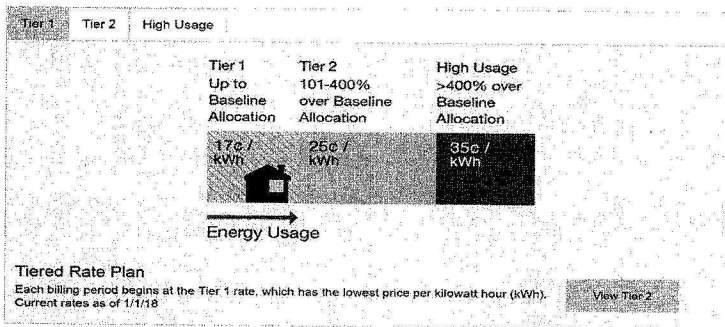Shown below is the Southern California Edison rate for electricity, current as of 5/1/2018. Assume your household is frugal with electricity usage, so you are in Tier 1.



I will calculate the number of hashes it takes to mine 1 bitcoin for you: The global hash rate (the combined computational capability of all active mining computers in the world) as of 5/1/2018 is 28,791,021,184 GH/s. # hashes to mine 1 bitcoin = global hash rate times ten minutes /25 = (28,791,021,184 * 10⁹ H/s) * (60 sec/min) 10 min /12.5 = (2.9 * 6/1.25) * 10⁹(10+9+1+1-1) = approx. 1.3 * 10²¹.

So: 1.3 * 10²¹ hashes earns one bitcoin. Use this to determine how many bitcoins per second the Antminer S9 mines, based on its hash rate of 13 TH/s. (H=hash T=Tera)

The electricity cost should be calculated based on the Antminer S9 power consumption of 1300 W.

PROBLEM 1:

Hourly income:

$$\text{Antminer Processing Speed} = 13 \frac{\text{TH}}{\text{s}} = 13 \times 10^{12} \frac{\text{H}}{\text{s}}$$

$$1 \text{ bitcoin} = 1.3 \times 10^{21} \text{ H}$$

$$\text{Antminer bitcoin earning rate} = \frac{13 \times 10^{12}}{1.3 \times 10^{21}} \frac{\text{bitcoin}}{\text{s}} = 10^{-8} \frac{\text{bitcoin}}{\text{s}}$$

$$\text{Bitcoin earned per hour} = 10^{-8} \times 60 \times 60 = 3.6 \times 10^{-5}$$

$$\text{Hourly income} = 3.6 \times 10^{-5} \times 10^4 \text{ \$} = 3.6 \times 10^{-5} \times 10^6 \text{ ¢} = 36 \text{ ¢}$$

Hourly Cost





$$= 1.3 \text{ kW} \times \frac{17 \text{ ¢}}{\text{kWh}} = 22.1 \frac{\text{¢}}{\text{hour}}$$

$$\text{Hourly cost} = 22.1 \text{ ¢}$$


$$\text{Hourly Profit} = 36 \text{ ¢} - 22.1 \text{ ¢} = 13.9 \text{ ¢}$$

PROBLEM 2: (10 points)

Find R_{eq} :

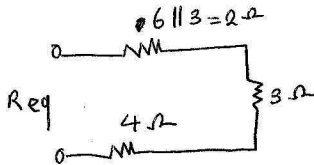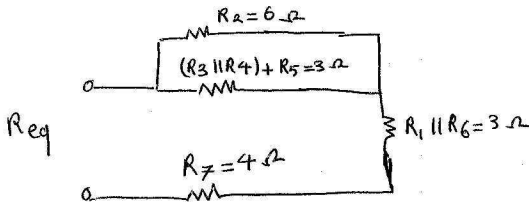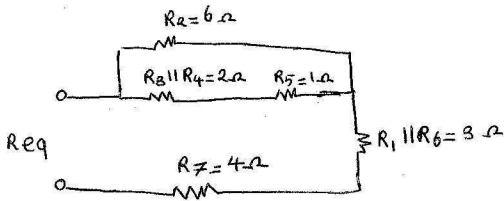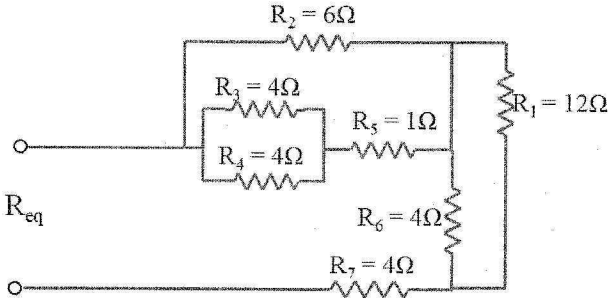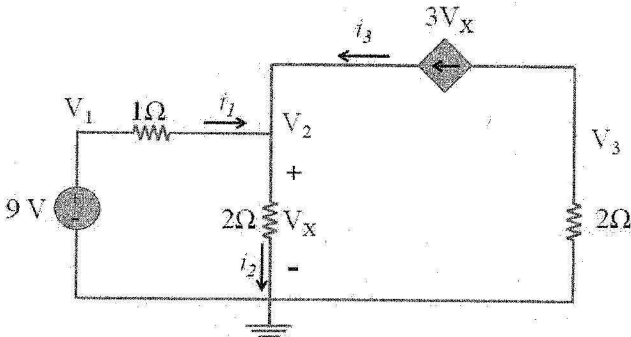

$$R_{eq} = 2 + \frac{3}{2} + 4 = 9\Omega$$

PROBLEM 3: (40 points)Use nodal analysis to find V_1 through V_3 and i_1 through i_3 :a) What is the value of V_1 (2pts)

$$V_1 = 9V$$

b) KCL Equations (20pts)

Write KCL @ Node V_2 to find an equation in terms of the unknown nodal voltages of V_1 through V_3 (10pts)

$$i_1 + i_3 = i_2 \rightarrow \frac{V_1 - V_2}{1} + 3V_x = \frac{V_2}{2}$$

$$V_x = V_2 \Rightarrow \frac{V_1 - V_2}{1} + 3V_2 = \frac{V_2}{2} \rightarrow V_1 + 1.5V_2 = 0$$

$$\left. \begin{array}{l} \text{or} \\ 9 + 1.5V_2 = 0 \\ \text{or} \\ V_2 = -6V \end{array} \right\}$$

Write KCL @ Node V_3 to find an equation in terms of the unknown nodal voltages of V_1 through V_3 (10pts)

$$3V_2 + \frac{V_3}{2} = 0 \rightarrow 3V_2 + \frac{V_3}{2} = 0$$

$$\Rightarrow V_3 = -6V_2 = +36V$$

c) Solve V_1 to V_3 (3pts)

V_1	$9V$
V_2	$-6V$
V_3	$+36V$

d) Find expressions for currents i_1 , i_2 and i_3 in terms of V_1 through V_3 (12pts)

i_1	$V_1 - V_2$
i_2	$\frac{V_2}{2}$
i_3	$3V_2$ or $-\frac{V_3}{2}$

$$i_1 = \frac{V_1 - V_2}{1}$$

$$i_2 = \frac{V_2}{2}$$

$$i_3 = 3V_2 \text{ or } i_3 = -\frac{V_3}{2}$$


e) Solve i_1 through i_3 (3pts)

i_1	15 A
i_2	-3 A
i_3	-18 A

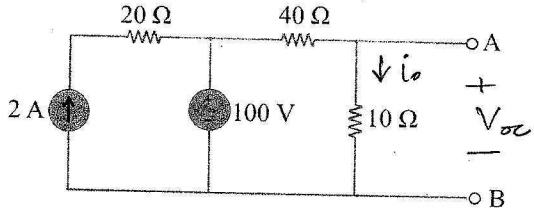PROBLEM 4: (points) **30**

Find the Thevenin equivalent circuit at terminals AB by finding V_{oc} and I_{sc} .

$V_{oc} \equiv V_{ab}(\text{open})$ $I_{sc} \equiv I_{ab}(\text{short at } a \text{ to } b)$



V_{oc}	20V
I_{sc}	2.5A
V_{Th}	20V
R_{Th}	8Ω


* Method 1 for V_{oc} (voltage divider):

$$V_{Th} = V_{oc} = 100 \cdot \frac{10}{50} = 20V$$

* Method 2 for V_{oc} (KVL):

$$-100 + 50 i_o = 0 \Rightarrow i_o = 2A$$

$$V_{oc} = 10 \cdot i_o = 20V$$

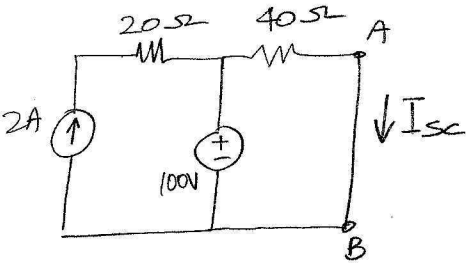


$$-100 + 40 I_{sc} = 0 \Rightarrow I_{sc} = 2.5A$$


$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{20}{2.5} = 8\Omega$$

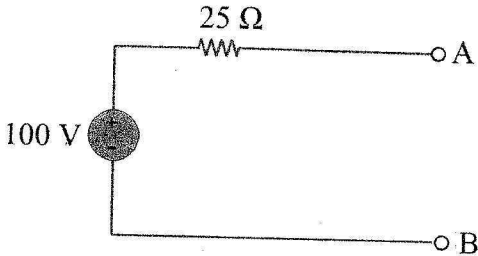PROBLEM 5: (10 points)

Find the Norton equivalent circuit at terminals AB by using the given Thevenin circuit.



I_N	4 A
R_N	25 Ω

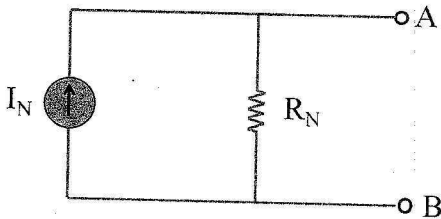

$$R_N = R_{Th}$$

$$I_N = V_{Th}/R_{Th}$$

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{100}{25} = 4A$$

$$R_N = R_{Th} = 25\Omega$$