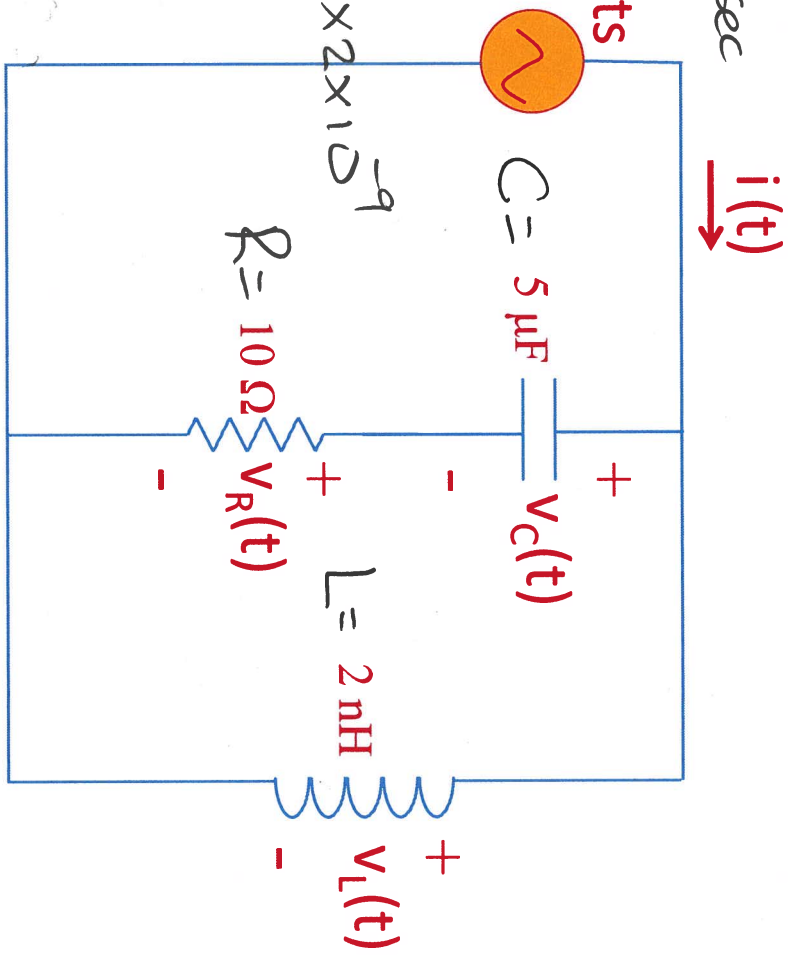


Problem 1: (10 pts)

For the circuit shown below, find $i(t)$, $v_L(t)$, $v_C(t)$ and $v_R(t)$.

$v_s(t) = 4 \cos(100t + 60^\circ)$ volts
 $\omega = 100$ rad/sec



$$\overline{V}_s = 4 \angle 60^\circ \text{ V}$$

$$\overline{Z}_{eq} = \left(\frac{1}{j(100)(5 \times 10^{-6})} + 10 \right) \parallel j(100) \times 2 \times 10^{-9}$$

$$= 2 \times 10^{-7} \angle 90^\circ \Omega$$

$$\overline{I} = \frac{\overline{V}_s}{\overline{Z}_{eq}} = 2 \times 10^7 \angle -30^\circ \text{ A}$$

$$i(t) = 2 \times 10^7 \cos(100t - 30^\circ) \text{ A}$$

$$\bar{V}_c = \bar{V}_s \frac{\frac{1}{j\omega c}}{\frac{1}{j\omega c} + R} = 4 \angle 59.71^\circ \text{ V}$$

$$V_c(t) = 4 \cos(100t + 59.71^\circ) \text{ V}$$

$$V_R = V_s \frac{R}{R + \frac{1}{j\omega c}} = 0.02 \angle 149.71^\circ \text{ V}$$


$$V_R(t) = 0.02 \cos(100t + 149.71^\circ) \text{ V}$$

$$V_L(t) = V_s(t) = 4 \cos(100t + 60^\circ) \text{ V}$$

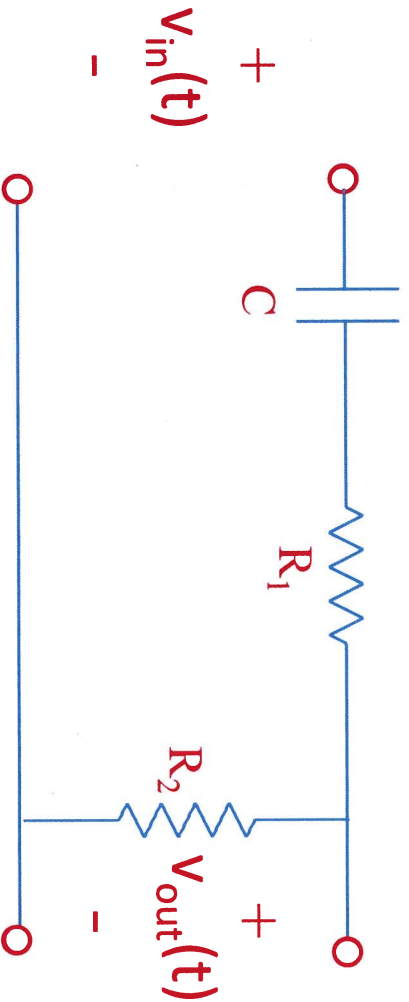Problem 2: (10 pts)

Determine the type of the filter shown below based on C , R_1 and R_2 .



Plot $V_{out}(t)$ versus $V_{in}(t)$ for $\omega \rightarrow 0$ and $\omega \rightarrow \infty$.



$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{j\omega R_2 C}{j\omega R_1 C + j\omega R_2 C + 1}$$

$$\lim_{\omega \rightarrow 0} \frac{V_{out}}{V_{in}} = 0$$

$$\lim_{\omega \rightarrow \infty} \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

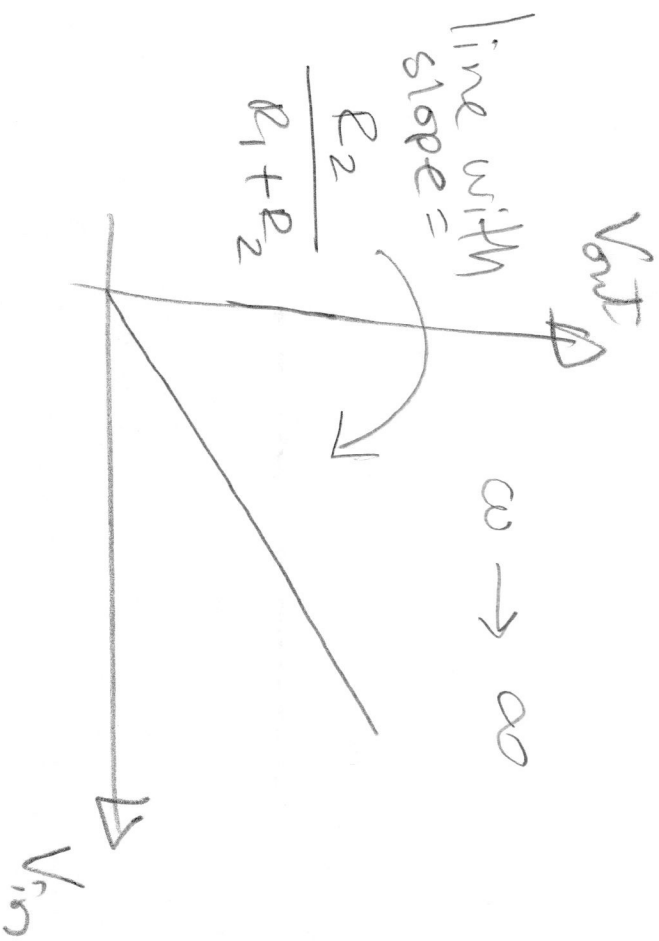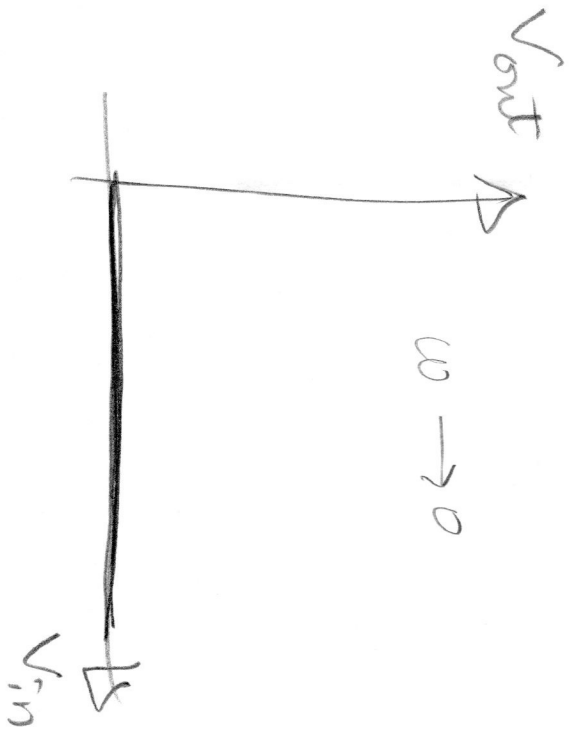


Problem 3a: (10 pts)

Find the transfer function $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$.

Plot $|H(\omega)|$ on linear-linear and log-log scales.

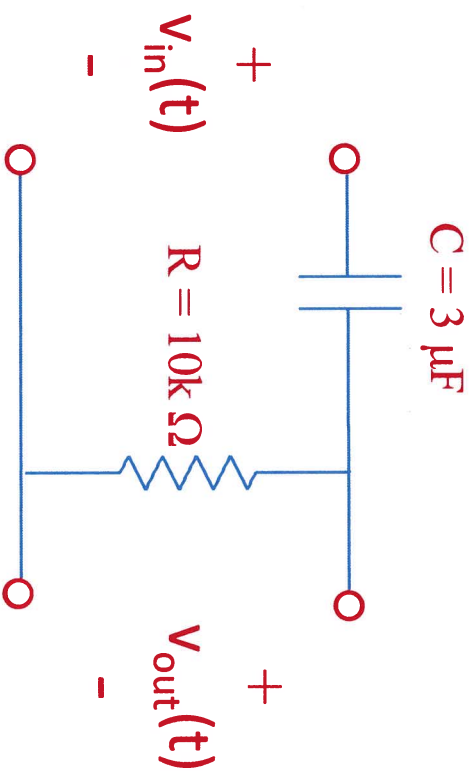Plot $\angle H(\omega)$ on linear-log scales.




$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C}}$$
$$= \frac{j\omega RC + 1}{j\omega RC + 1}$$


$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(\omega) = 90^\circ - \tan^{-1}(\omega RC)$$

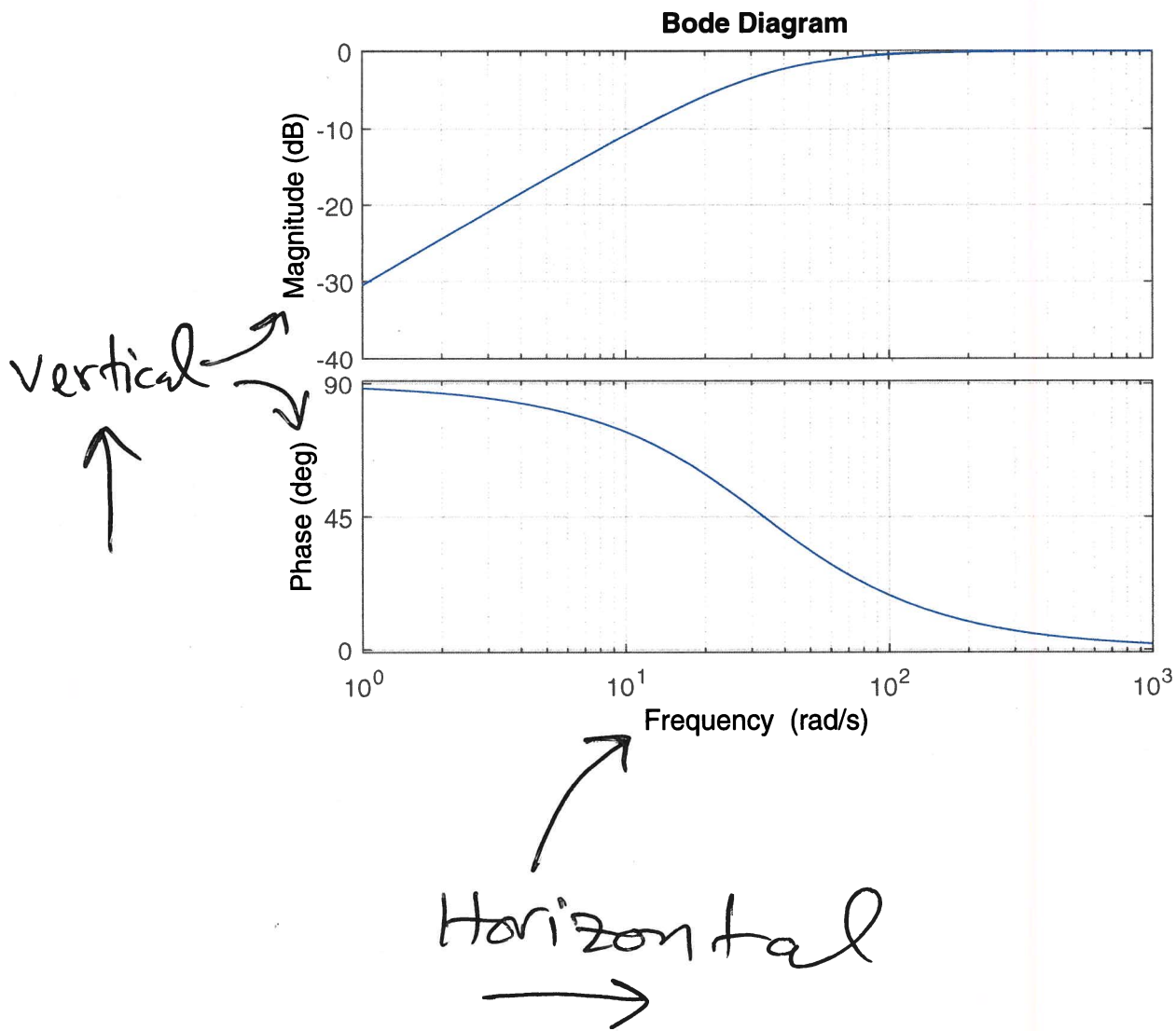For all plots, rotate
view to have frequency
axis horizontal.



Bode Diagram

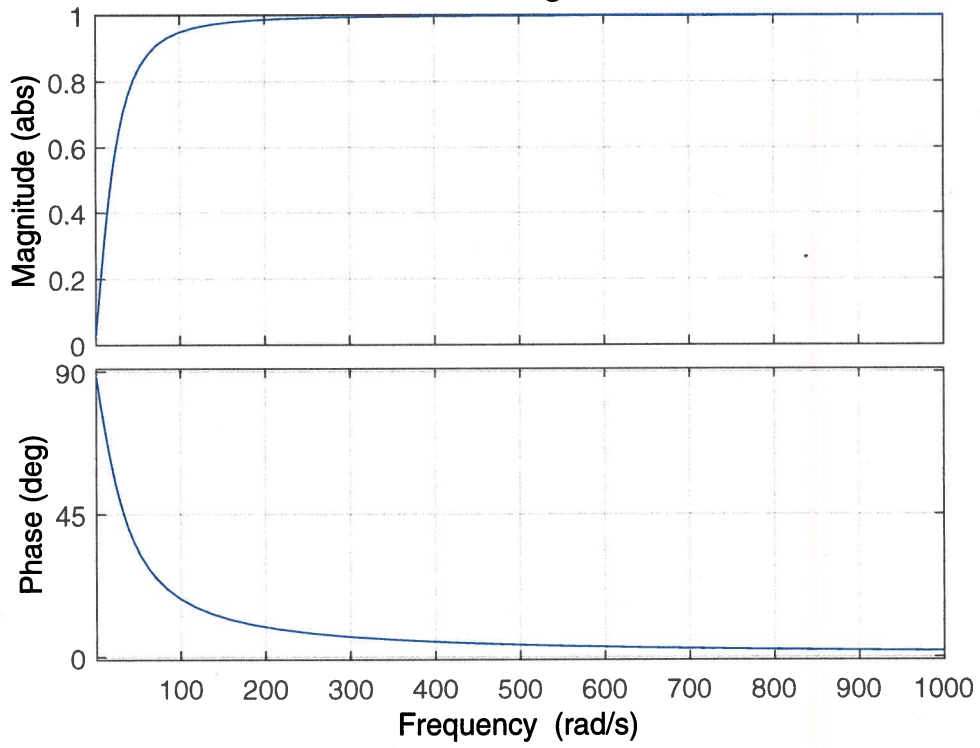


Problem 3b: (10 pts)

Find the transfer function $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$.

Plot $|H(\omega)|$ on linear-linear and log-log scales.

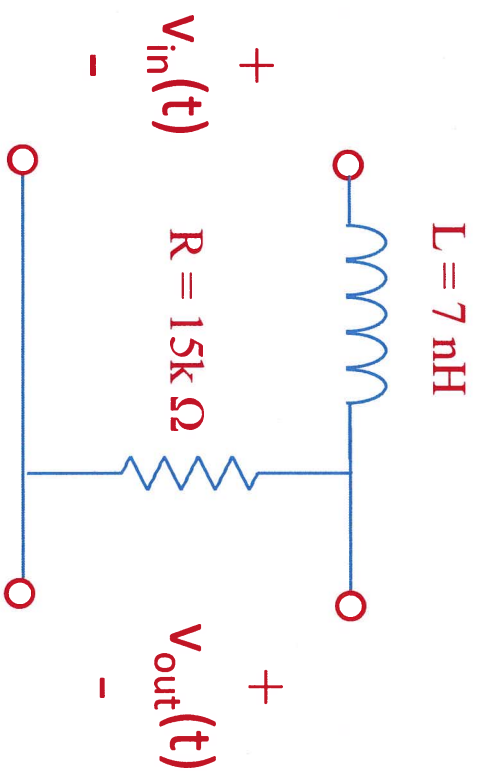Plot $\angle H(\omega)$ on linear-log scales.




$$H(\omega) = \frac{R}{R + j\omega L}$$


$$|H(\omega)| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$\angle H(\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

Bode Diagram

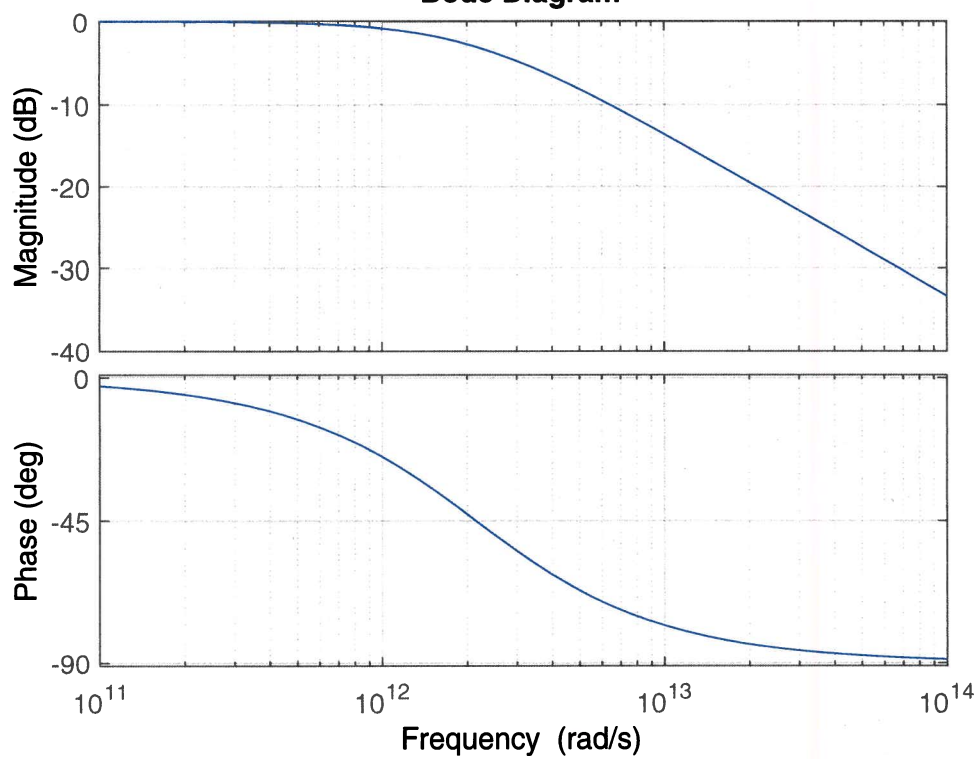

Bode Diagram

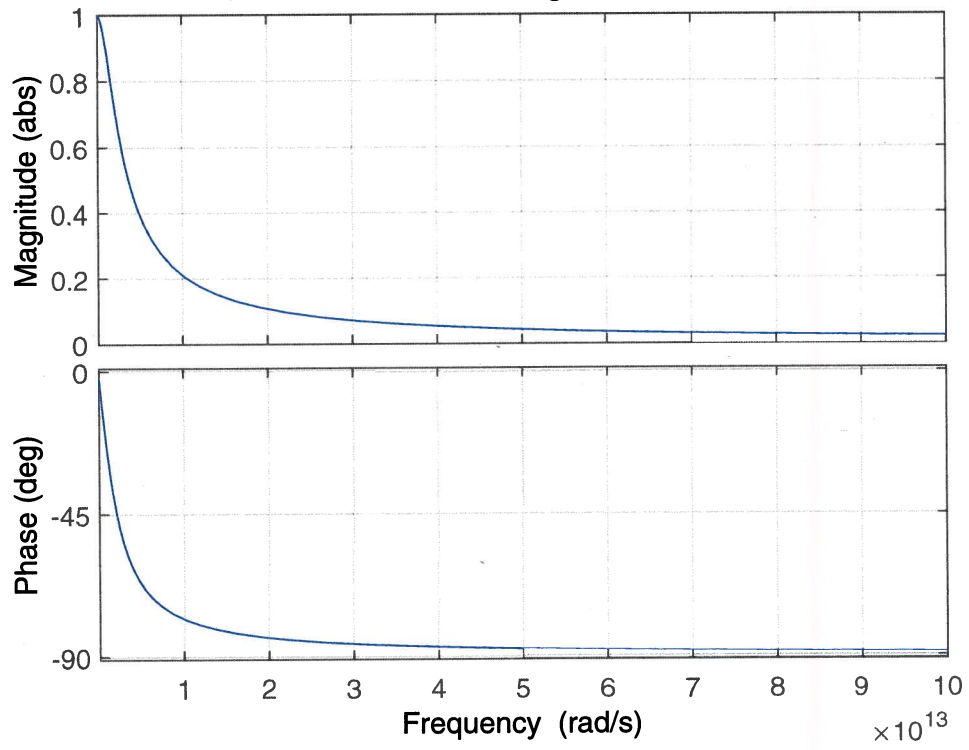


Problem 4: (10 pts)

Find the transfer function $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$.

Plot $|H(\omega)|$ on linear-linear and log-log scales.

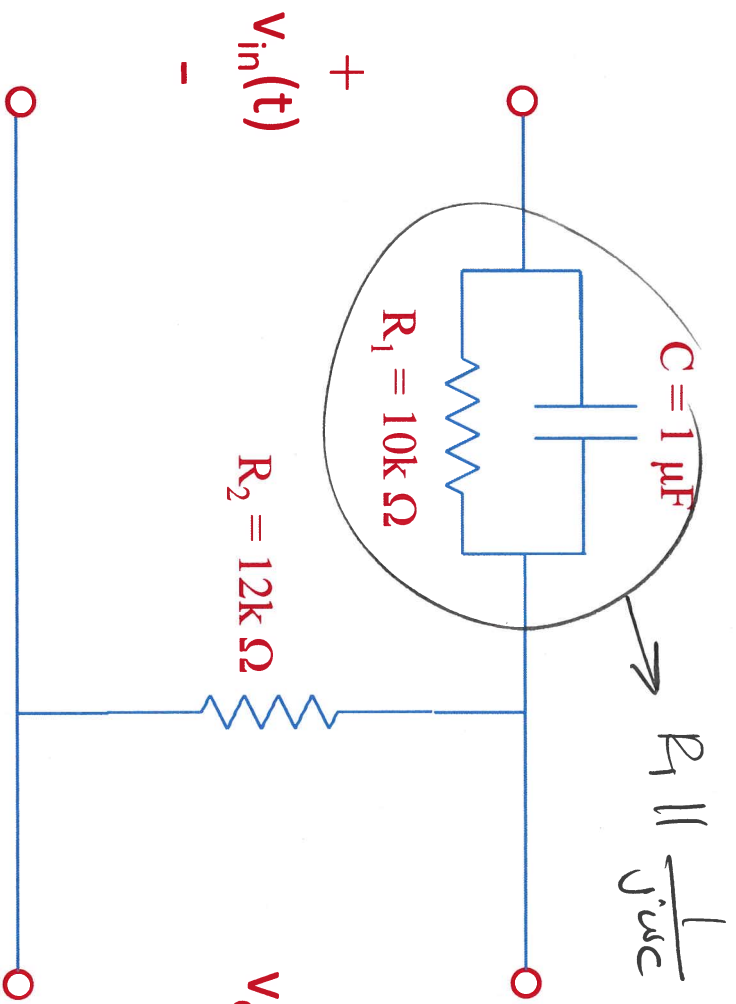Plot $\angle H(\omega)$ on linear-log scales.



$$R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}}$$

$$= \frac{\frac{R_1}{j\omega C}}{\frac{j\omega R_1 C + 1}{j\omega C}}$$

$$= \frac{R_1}{j\omega C} \cdot \frac{j\omega C}{1 + j\omega R_1 C}$$

$$= \frac{R_1}{1 + j\omega R_1 C}$$

$$H(\omega) = \frac{R_2}{R_2 + \frac{R_1}{1 + j\omega R_1 C}}$$

$$= \frac{R_2}{R_2 + j\omega R_1 R_2 C + R_1}$$


$$= \frac{R_2 + j\omega R_1 R_2 C}{1 + j\omega R_1 C}$$

$$= \frac{R_2 + j\omega R_1 R_2 C}{R_1 + R_2 + j\omega R_1 R_2 C}$$


$$|H(\omega)| = \frac{\sqrt{(R_2)^2 + (\omega R_1 R_2 C)^2}}{\sqrt{(R_1 + R_2)^2 + (\omega R_1 R_2 C)^2}}$$

$$\angle H(\omega) = \tan^{-1} \left(\frac{\omega R_1 R_2 C}{R_2} \right) - \tan^{-1} \left(\frac{\omega R_1 R_2 C}{R_1 + R_2} \right)$$

Bode Diagram

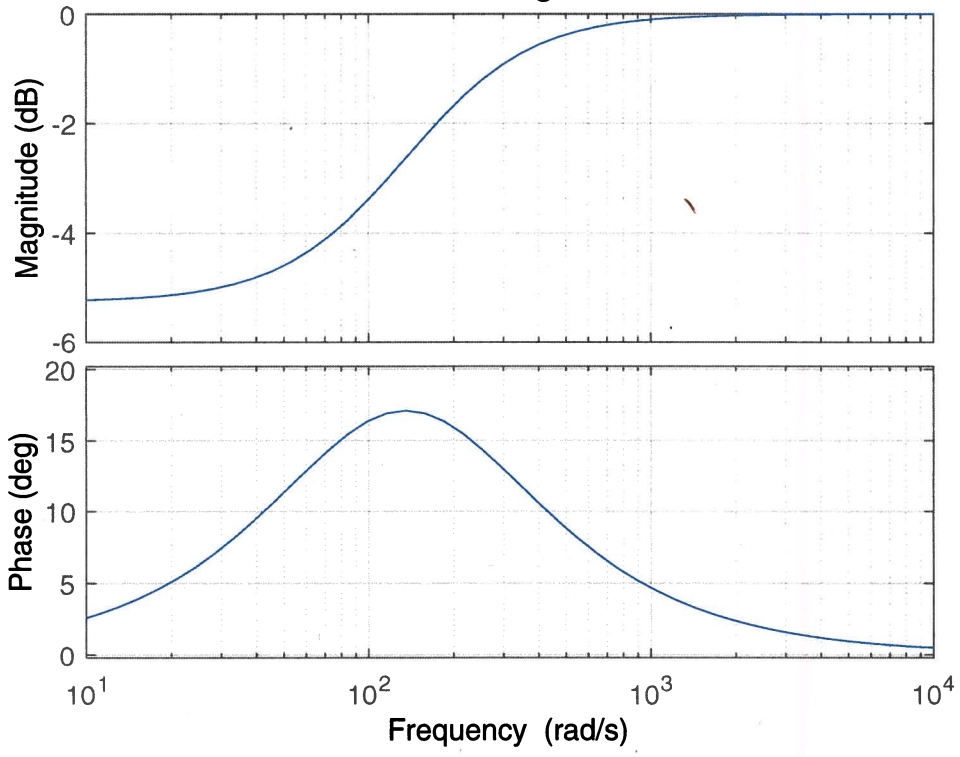

Bode Diagram

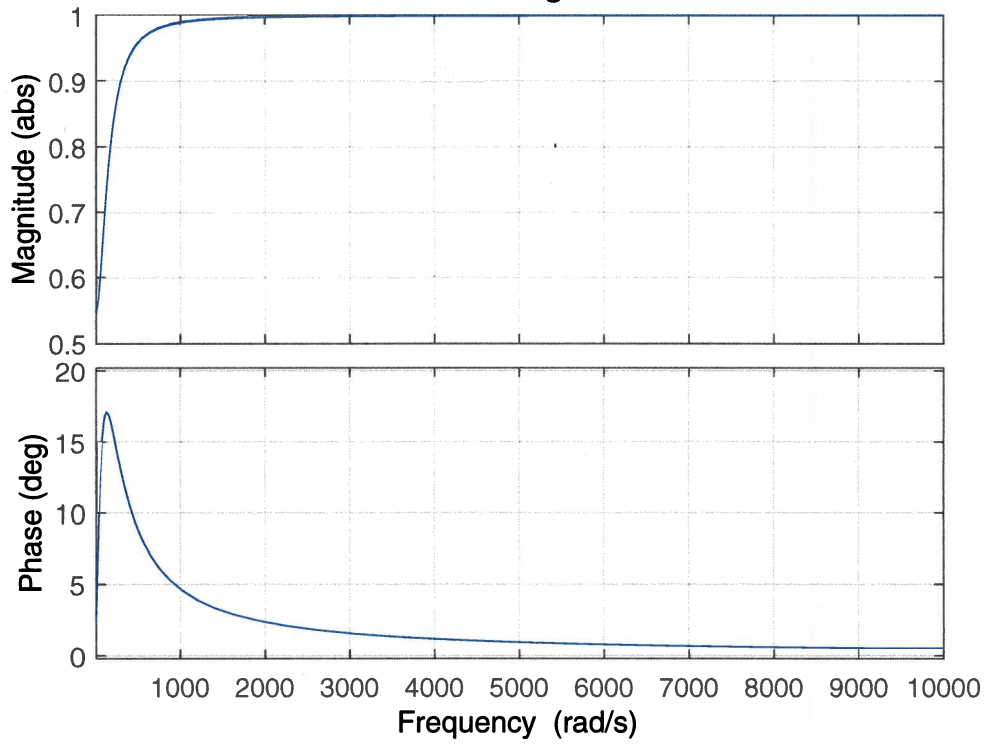


Problem 5: (10pts)

For $f = 1, 10, 100, 1k, 10k,$ and $100k$ Hz, find the output voltage as

$V_{out}(t) = A \cos(2\pi ft + \phi)$ where ϕ is the phase if the input voltage is

$$V_{in}(t) = 10 \cos(2\pi ft + \pi/3)$$

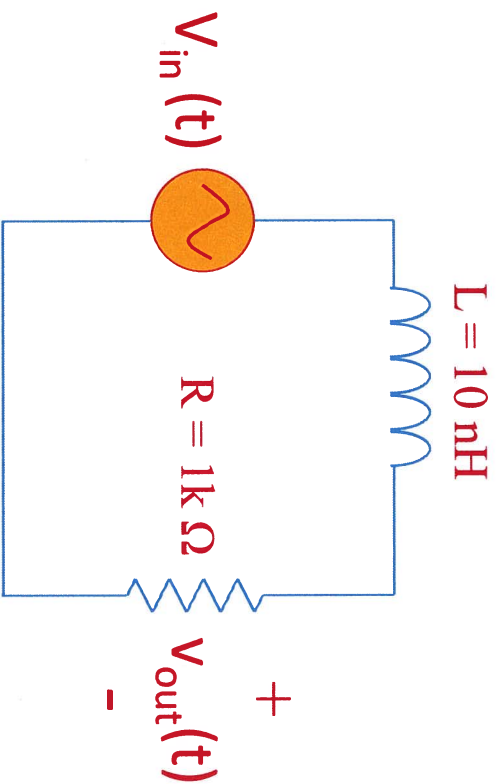

$$\overline{V_{in}} = 10 e^{j\pi/3}$$

$$\overline{V_{out}} = \overline{V_{in}} \frac{R}{R + j\omega L}$$

$$= 10 e^{j\pi/3} \frac{1 \times 10^3}{1 \times 10^3 + j(2\pi f) \times 10 \times 10^{-9}}$$

or $\pi/2$ rad

f (Hz)

V_{out}

V_{out} (t) =

1

use
the

$V_1(t) = 10 \cos(2\pi t + 60^\circ)$

10

V_{out}

$V_2(t) = 10 \cos(20\pi t + 60^\circ)$

100

equation
on the

$V_3(t) = 10 \cos(200\pi t + 60^\circ)$

1K

previous
page

$V_4(t) = 10 \cos(2000\pi t + 60^\circ)$

10K

$V_5(t) = 10 \cos(20,000\pi t + 60^\circ)$


100K

$V_6(t) = 10 \cos(200,000\pi t + 60^\circ)$

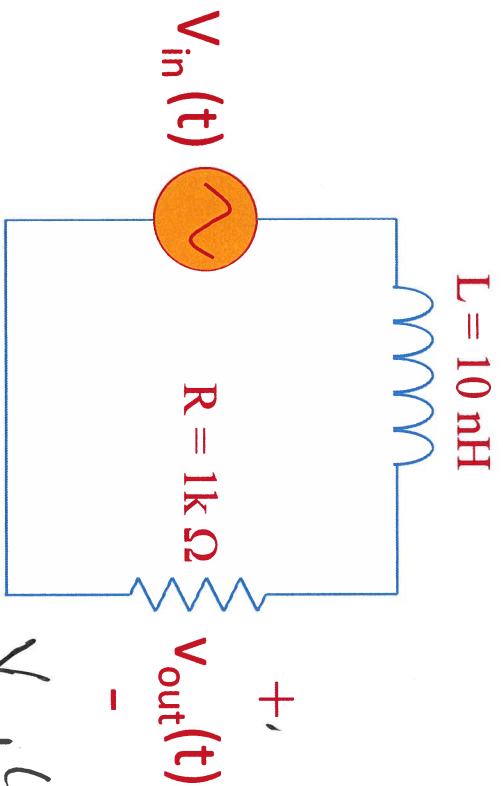Problem 6: (10pts)

Find the output voltage as

$V_{\text{out}}(t) = A \cos(2\pi f t + \phi)$ where ϕ is the phase if the input voltage is $V_{\text{in}}(t) = 10 \Sigma_i \cos(2\pi f_i t + \pi/3)$, $f_i = 1, 10, 100, 1k, 10k$, and $100k$ Hz



Linear circuit \rightarrow the output is the superposition of the input signals.

From Problem 5,

$$V_{\text{out}}(t) = V_1(t) + V_2(t) + V_3(t) + V_4(t) + V_5(t) + V_6(t)$$

Problem 7: (10pts)

Sketch the Bode plot (magnitude only) for the following transfer function

$$H(\omega) = 1/((1+j\omega\tau) \cdot (1+j\omega\tau))$$

