

## EECS/CSE 70A Network Analysis I


### Homework #3 *Solutions*

Due on or before

4/26/2018, Thursday at 10:00AM

(You can submit your homework in any of the discussion sessions on either Tuesday 4/24 or Thursday 4/26)

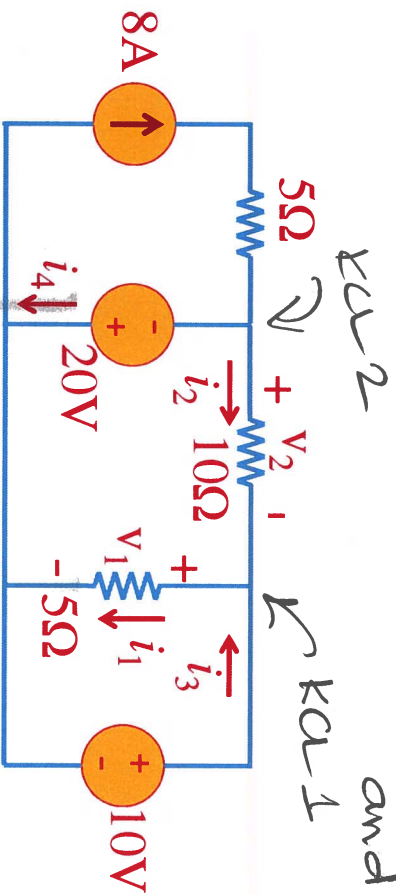Problem 1: (KCL, KVL, Ohm's Law) Find currents  $i_1$ ,  $i_2$ ,  $i_3$ , and  $i_4$  (10pts.)  
and voltages  $V_1$  and  $V_2$ .



$$\boxed{V_1 = 10V}$$

$$i_1 = \frac{V_1}{5} = 10/5 \Rightarrow \boxed{i_1 = 2A}$$

Applying KVL @ middle loop,

$$+20 + V_2 + V_1 = 0 \Rightarrow +20 + V_2 + 10 = 0$$

$$\Rightarrow \boxed{V_2 = -30V} \quad i_2 = \frac{V_2}{10} \Rightarrow \boxed{i_2 = -3A}$$

Applying KCL at top right node,

$$i_2 + i_3 = i_1 \Rightarrow i_3 = i_1 - i_2 = 2 + 3$$

$$\Rightarrow \boxed{i_3 = 5A}$$


KCL at middle left node,

$$8 = i_2 + i_4 \Rightarrow i_4 = 8 - i_2 = 8 + 3$$

$$\Rightarrow \boxed{i_4 = 11A}$$

$V_3$ , and  $V_4$

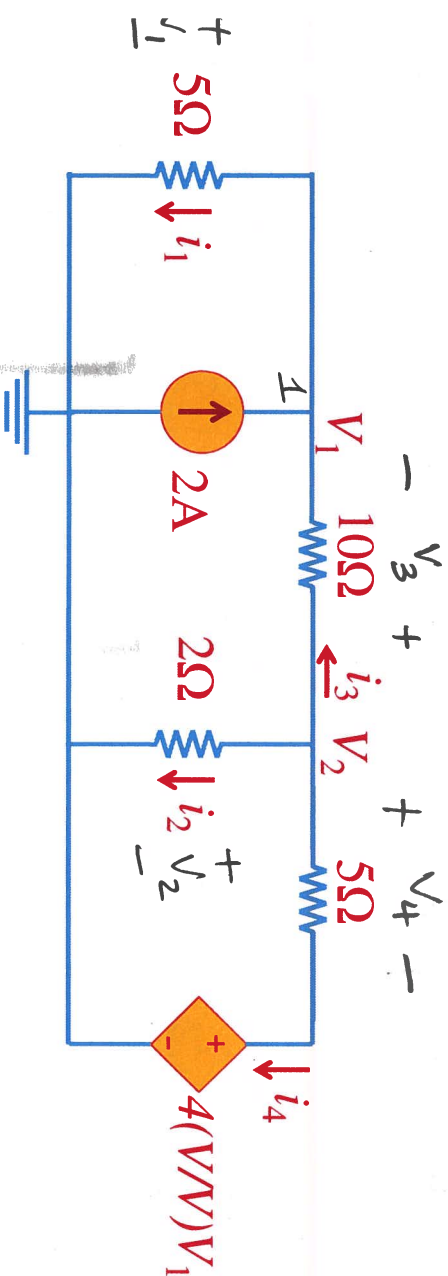Problem 2: Use nodal analysis and find  $V_1$  and  $V_2$  and  $i_1$  through  $i_4$  (10pts.)



@ Node 1  $\frac{V_1 - 0}{5} - 2 + \frac{V_1 - V_2}{10} = 0$

Multiply by 10,

$2V_1 - 20 + V_1 - V_2 = 0 \Rightarrow 3V_1 - V_2 = 20$  — (1)

@ node 2,  $\frac{V_2 - V_1}{10} + \frac{V_2 - 0}{2} + \frac{V_2 - 4V_1}{5} = 0$

Multiply by 10,

$V_2 - V_1 + 5V_2 + 2V_2 - 8V_1 = 0$

$-9V_1 + 8V_2 = 0$  — (2)

Multiply (1) by 3,

$9V_1 - 3V_2 = 60$  — (\*)

(2) + (\*)  $\Rightarrow +5V_2 = 60$

$\Rightarrow V_2 = 12V$

From (1),  $V_1 = \frac{20 + V_2}{3}$

$\Rightarrow V_1 = 10.67V$

$i_1 = \frac{V_1}{5} \Rightarrow i_1 = 2.13A$

$i_2 = \frac{V_2}{2} \Rightarrow i_2 = 6A$

$V_3 = V_2 - V_1 \Rightarrow$

$V_3 = +1.33V$

$i_3 = \frac{V_3}{10} \Rightarrow i_3 = 0.13A$


$V_4 = V_2 - 4V_1 = -30.68V$

$i_4 = \frac{V_4}{5} = -6.14A$

corrected

and  $V_3$

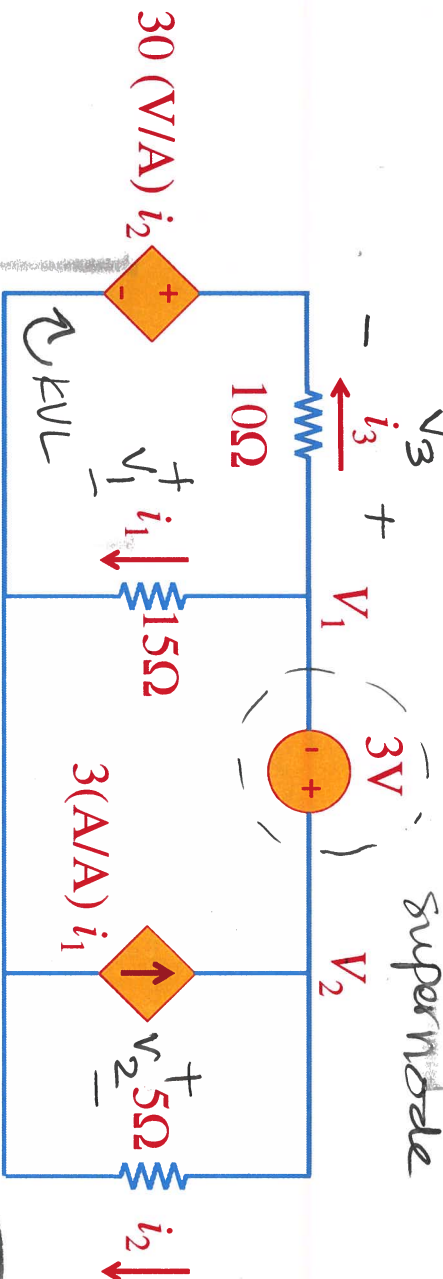Problem 3: Use nodal analysis and find  $V_1$  and  $V_2$  and  $i_1$  through  $i_3$  (10pts.)



$$-V_1 - 12V_2 = 0$$

$$V_1 + 12V_2 = 0 \quad (*)$$

@ supernode,

$$V_2 = V_1 + 3$$

$$-V_1 + V_2 = 3 \quad (**)$$

$$(*) + (**)$$

$$13V_2 = 3 \Rightarrow V_2 = 3/13V$$

$$\text{From } (*), V_1 = -12V_2$$

$$\Rightarrow V_1 = -36/13V$$

$$i_1 = \frac{V_1}{15} \Rightarrow i_1 = -12/65A$$

$$i_2 = \frac{V_2}{5} \Rightarrow i_2 = 3/65A$$

$$\text{KVL @ left loop, } -30i_2 - V_3 + V_1 = 0$$

$$\Rightarrow V_3 = V_1 - 30i_2 = -36/13 - 30 \cdot 3/65$$

$$\Rightarrow V_3 = -54/13V \quad i_3 = 3/10 \Rightarrow i_3 = -54/130A$$

KCL @ supernode,

$$\frac{V_1 - 30i_2}{10} + \frac{V_1}{15} - 3i_1 + \frac{V_2}{5} = 0 \quad (1)$$

$$i_1 = \frac{V_1}{15} \text{ and } i_2 = \frac{V_2}{5}$$


put  $i_1$  and  $i_2$  in (1),

$$\frac{V_1 - 6V_2}{10} + \frac{V_1}{15} - \frac{V_1}{5} + \frac{V_2}{5} = 0$$

multiply by 30

$$3V_1 - 18V_2 + 2V_1 - 6V_1 + 6V_2 = 0$$

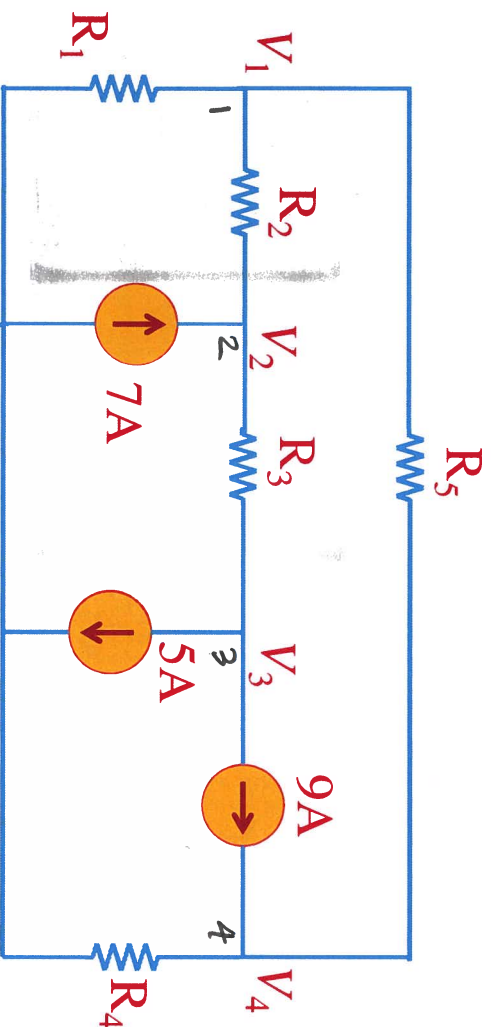Problem 4: Write all nodal voltage equations and put them in the matrix form (you do not need to solve for voltages  $V_1$  through  $V_4$ ) (10pts.)



$$\textcircled{a} \text{ node 4, } \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_4}{R_5} = 0$$


$$\textcircled{a} \text{ node 2, } \frac{V_2 - V_1}{R_2} - 7 + \frac{V_2 - V_3}{R_3} = 0$$

$$\textcircled{a} \text{ node 3, } \frac{V_3 - V_2}{R_3} + 5 + 9 = 0$$

$$\textcircled{a} \text{ node 4, } -9 + \frac{V_4}{R_4} + \frac{V_4 - V_1}{R_5} = 0$$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5}\right) & \left(\frac{-1}{R_2}\right) & 0 & \left(\frac{-1}{R_5}\right) \\ \left(\frac{-1}{R_2}\right) & \left(\frac{1}{R_2} + \frac{1}{R_3}\right) & \left(\frac{-1}{R_3}\right) & 0 \\ 0 & \left(\frac{-1}{R_3}\right) & \left(\frac{1}{R_3}\right) & 0 \\ \left(\frac{-1}{R_5}\right) & 0 & 0 & \left(\frac{1}{R_4} + \frac{1}{R_5}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 7 \\ -14 \\ 9 \end{bmatrix}$$

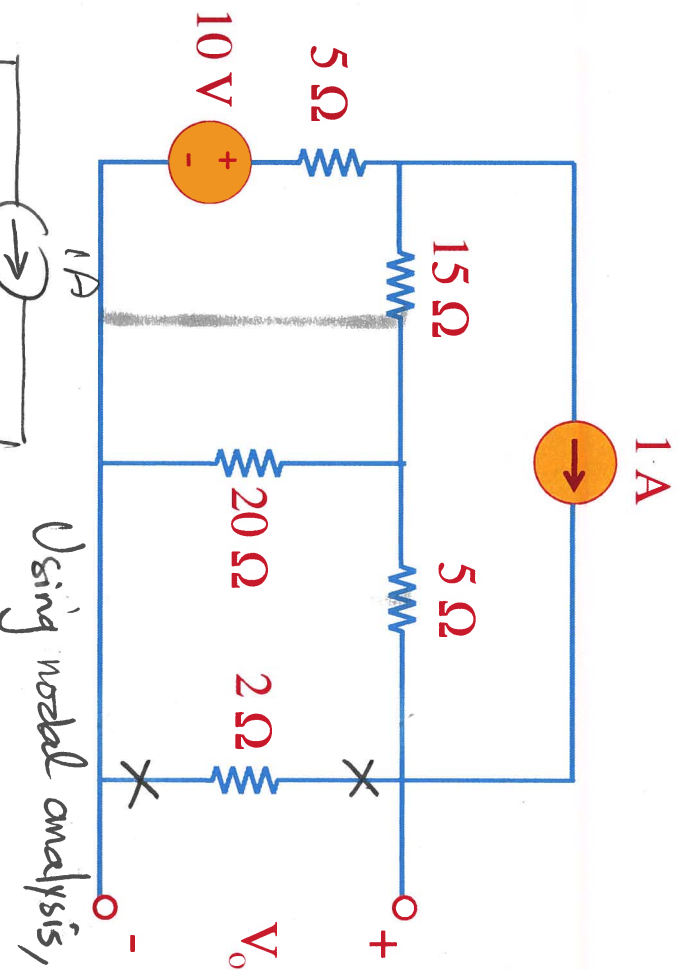Problem 5: Find  $V_o$  using Thévenin theorem (10pts.)



Using nodal analysis,


@ node 1,

$$\frac{V_1 - 10}{5} + \frac{V_1 - V_2}{15} + 1 = 0$$

Multiply by 15,

$$3V_1 - 30 + V_1 - V_2 + 15 = 0$$
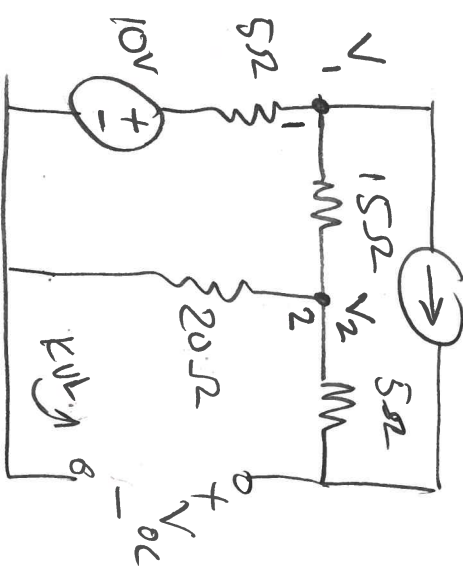
$$+ 4V_1 - V_2 = +15 \quad \text{--- (1)}$$



@ node 2,

$$\frac{V_2 - V_1}{15} + \frac{V_2}{20} - 1 = 0$$

Multiply by 60,


$$4V_2 - 4V_1 + 3V_2 - 60 = 0$$

$$-4V_1 + 7V_2 = 60 \quad \text{--- (2)}$$

$$\textcircled{1} + \textcircled{2} \Rightarrow V_2 = 12.5V$$


Using KVL,  $-V_o + 5 + 12.5 = 0$

$$\Rightarrow V_o = 17.5V$$

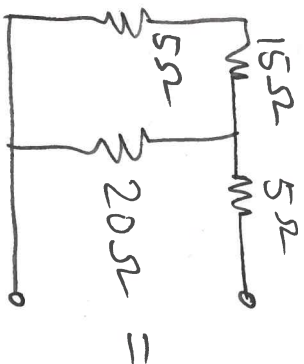

$$15\Omega = R_{th}$$

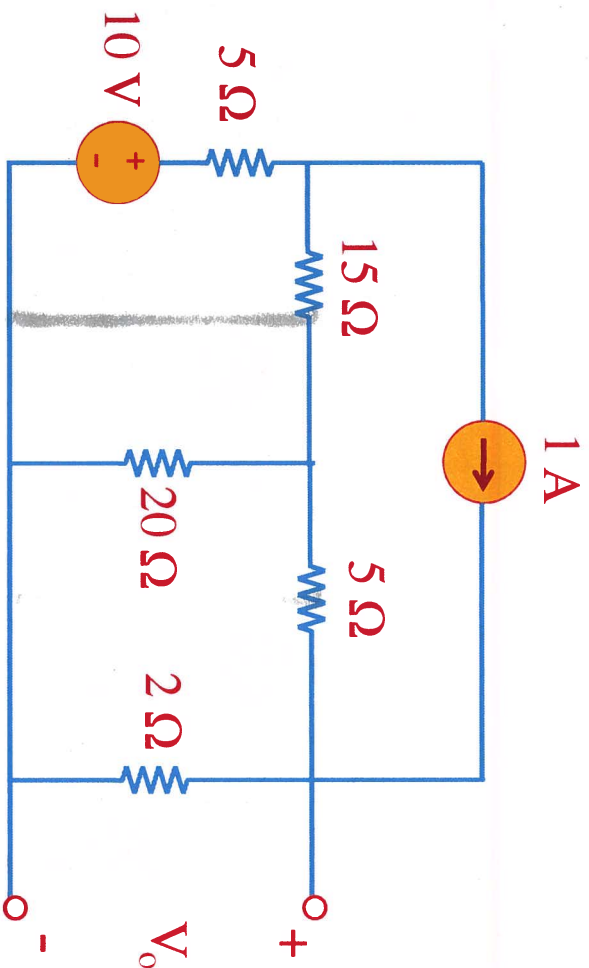
Problem 5: Find  $V_o$  using Thévenin theorem (10pts.)



Using voltage divider,


$$V_o = 17.5 \cdot \frac{2}{15 + 2}$$

$$\Rightarrow \boxed{V_o = 2.06\text{V}}$$

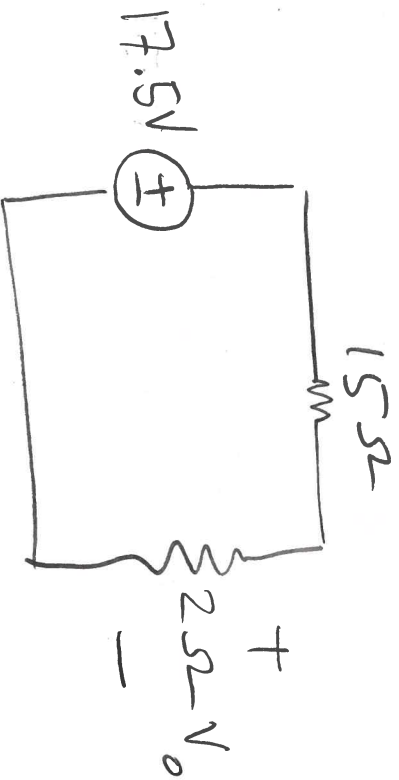



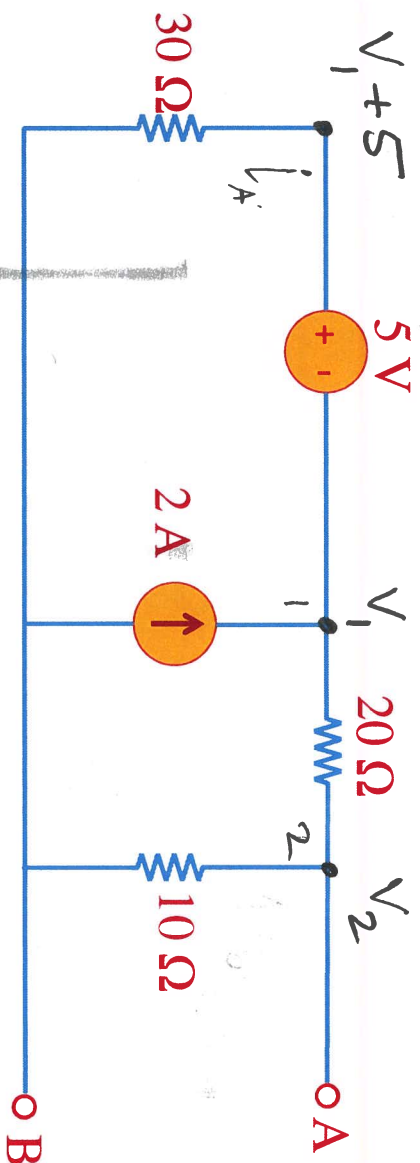Problem 6: Find both the Thevenin and Norton equivalent circuits at terminals AB.  
(10pts.)



$$i_A = \frac{V_1 + 5}{30}$$

Applying nodal analysis @ node 1,

$$\frac{V_1 + 5}{30} - 2 + \frac{V_1 - V_2}{20} = 0$$

Multiply by 60,

$$2V_1 + 10 - 120 + 3V_1 - 3V_2 = 0$$

$$5V_1 - 3V_2 = 110 \quad \text{--- (1)}$$

At node 2,

$$\frac{V_2 - V_1}{20} + \frac{V_2}{10} = 0$$

Multiply by 20,

$$V_2 - V_1 + 2V_2 = 0$$


$$-V_1 + 3V_2 = 0 \quad \text{--- (2)}$$

Multiply (2) by 5 and add to (1)

$$12V_2 = 110 \Rightarrow V_2 = \frac{55}{6} \text{ V} = V_{oc}$$

$$\Rightarrow V_{Th} = 55/6 \text{ V}$$

To find  $R_{Th}$ , use

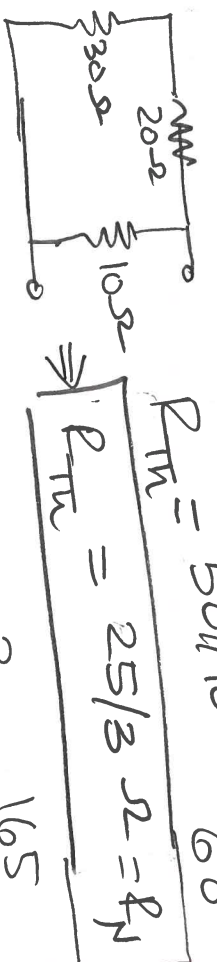

$$R_{Th} = 50 \parallel 10 = \frac{500}{60}$$


$$\Rightarrow R_{Th} = 25/3 \Omega = R_N$$

$$I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{55}{6} \cdot \frac{3}{25} = \frac{165}{150}$$

$$\frac{1}{I_{sc}} = \frac{1}{165/150} = 11/10 \text{ A}^{-1}$$



Problem 6. AIT. method to find  $R_{Th}$

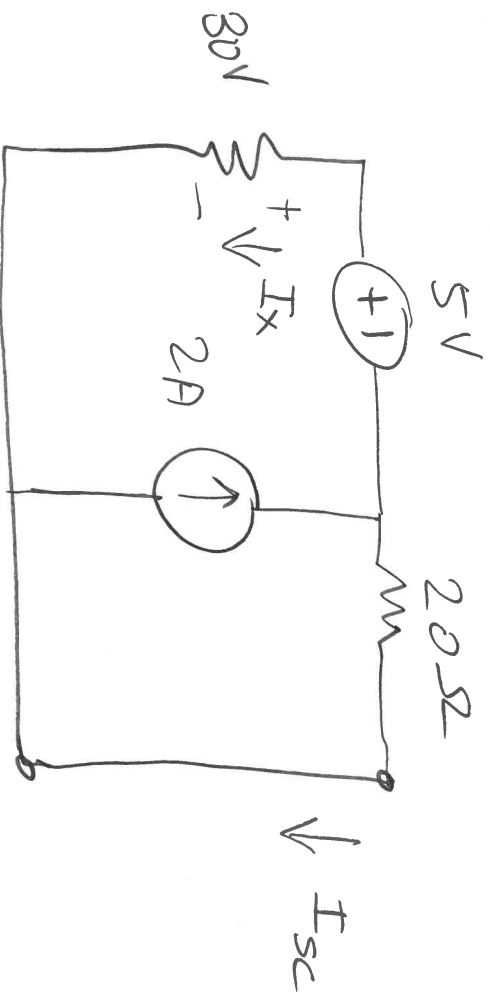

$$-30 I_x + 5 + 20 I_{sc} = 0$$

$$\Rightarrow 4 I_{sc} - 6 I_x = -1 \quad \text{--- (1)}$$

$$2 = I_x + I_x \Rightarrow I_x = 2 - I_{sc} \quad \text{--- (2)}$$

② in ①


$$4 I_{sc} - 6 (2 - I_{sc}) = -1$$

$$10 I_{sc} = 11 \Rightarrow$$

$$I_{sc} = 11/10 \text{ A}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{5}{3}}{\frac{11}{10}} = \frac{25}{3} \Omega = R_N$$

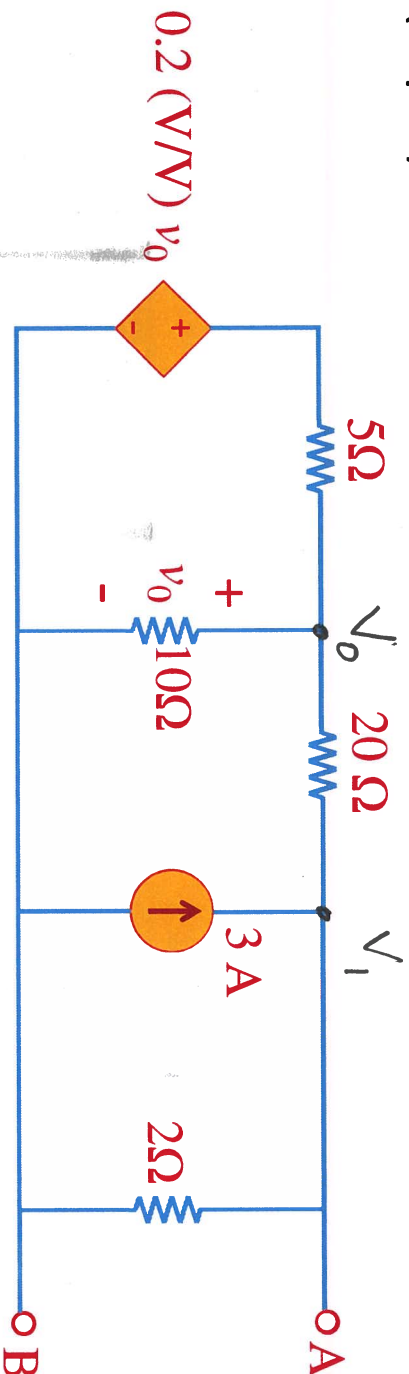Problem 7: Find both the Thevenin and Norton equivalent circuits at terminals AB.  
(10pts.)



Nodal analysis @  $V_o$ ,

$$\frac{V_o - 0.2V_o}{5} + \frac{V_o}{10} + \frac{V_o - V_1}{20} = 0$$

$$0.31V_o - 0.05V_1 = 0 \quad (1)$$

@  $V_1$ ,

$$\frac{V_1 - V_o}{20} - 3 + \frac{V_1}{2} = 0$$


$$-0.05V_o + 0.55V_1 = 3 \quad (2)$$

Multiply (1) by 11


$$3.41V_o - 0.55V_1 = 0 \quad (1)$$

$$(1) + (2) \quad 3.36V_o = 3 \Rightarrow V_o = 0.89V$$

From (1),  $V_1 = 5.52V = V_{oc} = V_{th}$

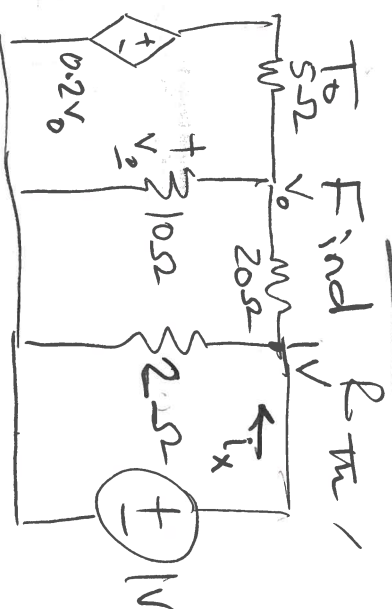

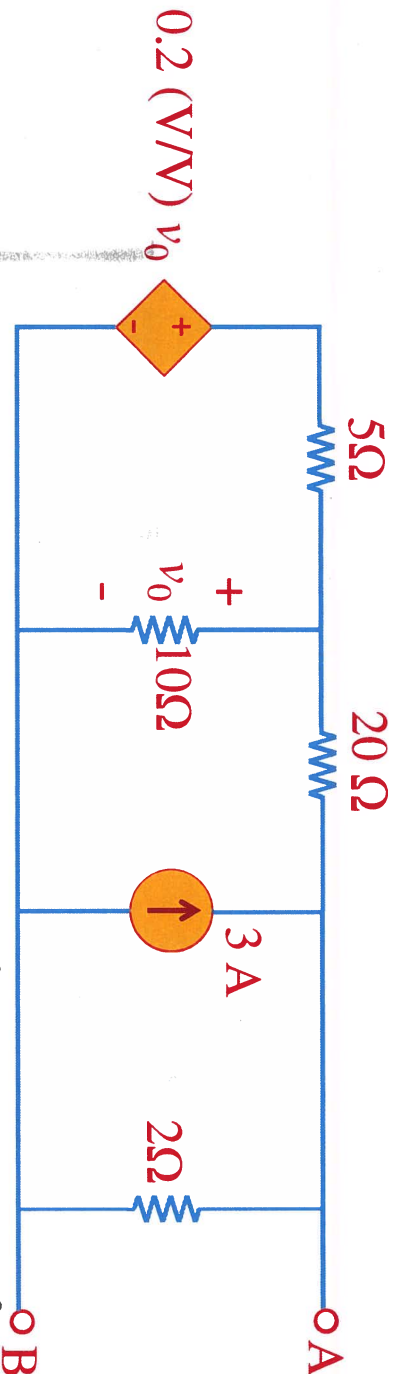Problem 7: Find both the Thevenin and Norton equivalent circuits at terminals AB.  
(10pts.)



Nodal analysis @  $V_o$ ,

$$\frac{V_o - 0.2V_o}{5} + \frac{V_o}{10} + \frac{V_o - 1}{20} = 0$$

Multiply by 20,

$$4V_o - 0.8V_o + 2V_o + V_o - 1 = 0$$

$$V_o = 0.16 \text{ V}$$

@ 1V node,

$$\frac{1 - V_o}{20} + \frac{1}{2} - i_x = 0$$

$$\Rightarrow i_x = 0.542 \text{ A}$$

$$R_{Th} = \frac{1 \text{ V}}{0.542} = 1.85 \Omega = R_N$$

$$I_{sc} = \frac{V_{Th}}{R_N} = 2.93 \text{ A}$$