

## EECS/CSE 70A Network Analysis I

---

### Homework #5

Due on or before

**5/22/2018, Tuesday at 5:00PM**

(You can submit homework in either of the discussion sessions only on Tuesday 5/22 or put it in the box near EH 4404 on 5/22 by 5:00PM)

Problem 1: (10 pts)

$$u = \frac{A + jB}{C + jD} \times \frac{C - jD}{C - jD} = \frac{(AC + BD) + j(BC - AD)}{C^2 + D^2}$$

$$= \frac{AC + BD}{C^2 + D^2} + j \frac{BC - AD}{C^2 + D^2}$$

$$\frac{A + jB}{C - jD} = \frac{AC + jBC}{-jAD + BD} = \frac{(AC + BD) + j(BC - AD)}{C^2 + D^2}$$

A, B, C, and D are real.

2) a) Find  $\text{Re}(u) = \frac{AC + BD}{C^2 + D^2}$

2) b) Find  $\text{Im}(u) = \frac{BC - AD}{C^2 + D^2}$

2) c) Express  $u$  as  $(X + jY)$

$$\left( \frac{AC + BD}{C^2 + D^2} \right)^2 + \left( \frac{BC - AD}{C^2 + D^2} \right)^2, \quad \theta = \tan^{-1} \left( \frac{BC - AD}{AC + BD} \right)$$

2) d) Express  $u$  as  $(r e^{j\theta})$   $r =$

2) e) Find  $\text{Re}(u e^{j\omega t}) = \text{Re} \{ r e^{j(\omega t + \theta)} \}$

$$= \text{Re} \{ r \cos(\omega t + \theta) + j r \sin(\omega t + \theta) \}$$

$$= r \cos(\omega t + \theta)$$

Problem 2a: (10 pts)

Given  $v(t) = 10\cos(\omega t - \pi/4)$  volts. Find the phasor  $V$  that represents  $v(t)$ . Express  $V$  as both  $x+iy$  and  $re^{j\theta}$ .

$$\bar{V} = 10 \angle -\pi/4 = 10 e^{-j\pi/4} \quad \boxed{5}$$

$$x = r \cos \theta = 10 \cos(-\pi/4) = 5\sqrt{2}$$

$$y = r \sin \theta = 10 \sin(-\pi/4) = -5\sqrt{2}$$

$$\bar{V} = +5\sqrt{2} - j 5\sqrt{2} \text{ V}$$

$\boxed{5}$

Problem 2b: (10 pts)

Given  $i(t) = 2\sin(5t + \pi/6)$  amps. Find the phasor  $\mathbf{I}$  that represents  $i(t)$ . Express  $\mathbf{I}$  as both  $x+jy$  and  $re^{j\theta}$ .

$$i(t) = 2 \cos(5t + \pi/6 - \pi/2) = 2 \cos(5t - \pi/3) \text{ A}$$

$$\mathbf{I} = 2 \angle_{- \pi/3} = 2 e^{j \pi/3} \text{ A} \quad [5]$$

$$x = r \cos \theta = 2 \cos(-\pi/3) = 1$$


$$y = r \sin \theta = 2 \sin(-\pi/3) = -\sqrt{3}$$

$$\mathbf{I} = 1 - j\sqrt{3} \text{ A}$$

[5]

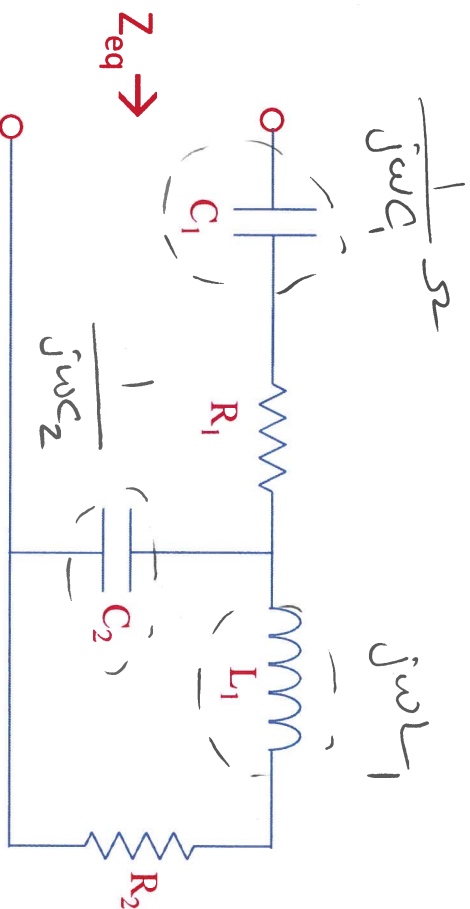Problem 3a: (10 pts)

Find the impedance  $Z_{eq}$  if  $L$  is the inductance,  $C$  is the capacitance, and  $R$  is the resistance. No need to simplify your answer as  $x+jy$  or  $re^{j\theta}$ .




$$Z_{eq} = \left[ (j\omega L_1 + R_2) \parallel \left( C \frac{1}{j\omega C_2} \right) \right] + \left[ R_1 + \frac{1}{j\omega C_1} \right] \quad [5]$$

$$= \left[ \frac{j\omega L_1 + R_2 + \frac{1}{j\omega C_2}}{j\omega L_1 + R_2 + \frac{1}{j\omega C_2}} + R_1 + \frac{1}{j\omega C_1} \right] \quad [5]$$

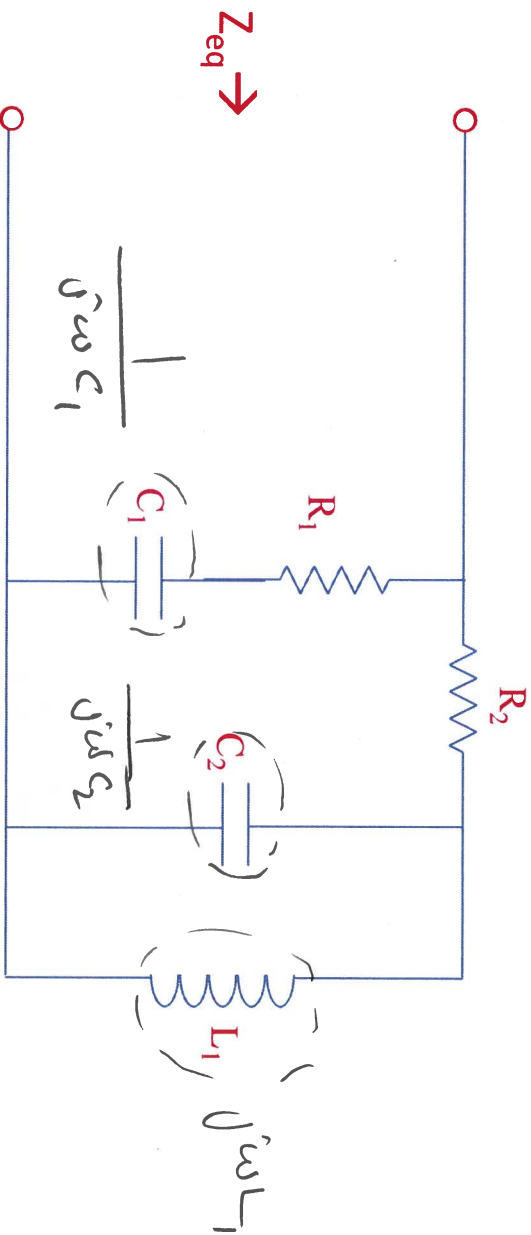Problem 3b: (10 pts)

Find the impedance  $Z_{eq}$  if  $L$  is the inductance,  $C$  is the capacitance, and  $R$  is the resistance. No need to simplify your answer as  $x+jy$  or  $re^{j\theta}$ .



$$\begin{aligned}
 Z_{eq} &= \left[ (j\omega L_1 \parallel \frac{1}{j\omega C_2}) + R_2 \right] \parallel \left[ R_1 + \frac{1}{j\omega C_1} \right] \\
 &= \left[ \frac{j\omega L_1 \cdot \frac{1}{j\omega C_2}}{j\omega L_1 + \frac{1}{j\omega C_2}} + R_2 \right] \parallel \left[ R_1 + \frac{1}{j\omega C_1} \right] \\
 &= \frac{A \cdot B}{A + B}
 \end{aligned}$$

[5]
[5]


Problem 3c: (10 pts)

$$\omega = 2\pi f$$

Find the impedance  $Z_{eq}$  if  $f = 1$  MHz. Express the answer as both  $x+jy$  and  $re^{j\theta}$ .

$$j\omega L = j(2\pi \times 10^6)(5 \times 10^{-9})$$

$$= j\pi \times 10^{-2} \Omega$$

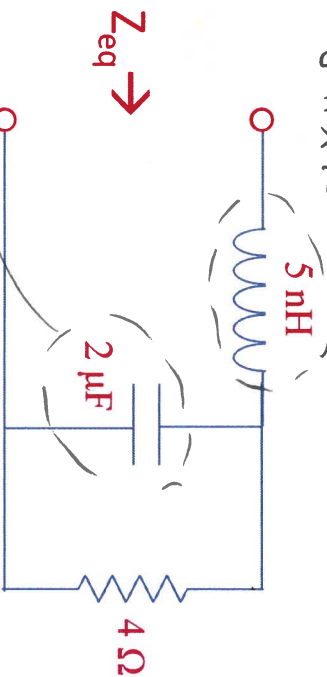

$$Z_{eq} = \left( 4 \parallel \frac{1}{j4\pi} \right) + j\pi \times 10^{-2}$$

$$= \frac{1}{\frac{1}{4} + (j4\pi)} + j\pi \times 10^{-2}$$

$$\frac{1}{j\omega C} = \frac{1}{j(2\pi \times 10^6)(2 \times 10^{-6})}$$


$$= \frac{1}{j4\pi} \Omega$$

$$= 0.00158 + j0.04813 \Omega \quad [5]$$

$$= 0.04816 \angle +88.12^\circ \Omega \quad [5]$$

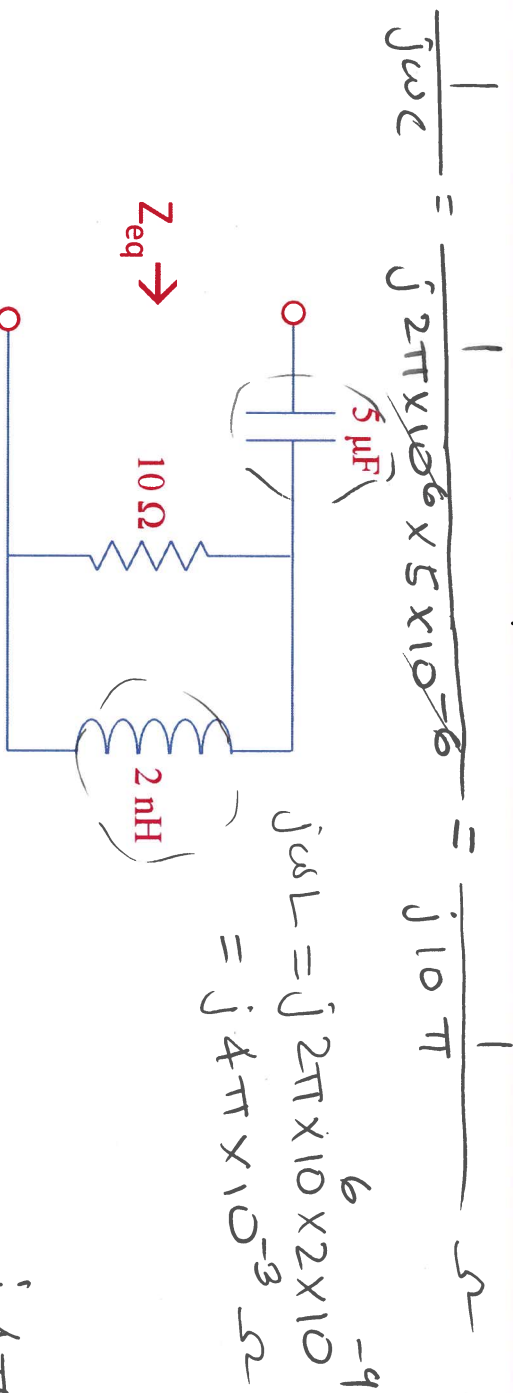Problem 3d: (10 pts)

Find the impedance  $Z_{eq}$  if  $f = 1$  MHz. Express the answer as both  $x+iy$  and  $re^{j\theta}$ .



$$\frac{1}{j\omega C} = \frac{1}{j2\pi \times 10^6 \times 5 \times 10^{-6}} = \frac{1}{j10\pi} \Omega$$


$$Z_{eq} = (10 \parallel j4\pi \times 10^{-3}) + \frac{1}{j10\pi} = \frac{j4\pi \times 10^{-2}}{10 + j4\pi \times 10^{-3}} + \frac{1}{j10\pi}$$

$$= 0.000016 - j0.019 \Omega \quad \boxed{5}$$

$$= 0.019 \angle -89.95^\circ \Omega \quad \boxed{5}$$



Problem 4a: (10 pts)

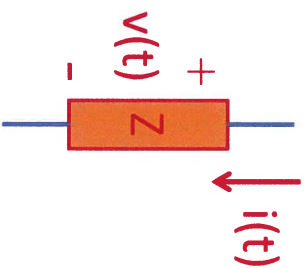


Given  $Z = 3 \angle 10^\circ$  ohms. Find  $i(t)$  if  $v(t) = 8 \cos(2t + \pi/4)$  volts.

$$\overline{V} = 8 \angle \pi/4$$

$$\overline{I} = \frac{\overline{V}}{Z} = \frac{8 \angle 45^\circ}{3 \angle 10^\circ} = \frac{8}{3} \angle 35^\circ \text{ A} \quad \boxed{5}$$

$$i(t) = \frac{8}{3} \cos(2t + 35^\circ) \text{ A} \quad \boxed{5}$$

Problem 4b: (10 pts)

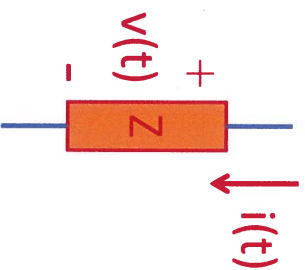

Given  $Z = 3 \angle 10^\circ$  ohms. Find  $v(t)$  if  $i(t) = 4 \cos(20t - \pi/3)$  amps.

$$\underline{I} = 4 \angle^{-60^\circ} \text{ A} \quad \underline{V} = \underline{I} \underline{Z} = (4 \angle^{-60^\circ}) (3 \angle 10^\circ) = 12 \angle^{-50^\circ} \text{ V} \quad \boxed{5}$$


$$v(t) = 12 \cos(20t - 50^\circ) \text{ V} \quad \boxed{5}$$

Problem 5a: (10pts)

Find  $i_c(t)$ . Hint: convert the voltage source into a phasor, then convert back to  $i_c(t)$ .

$$\omega = 2\pi f = 40$$
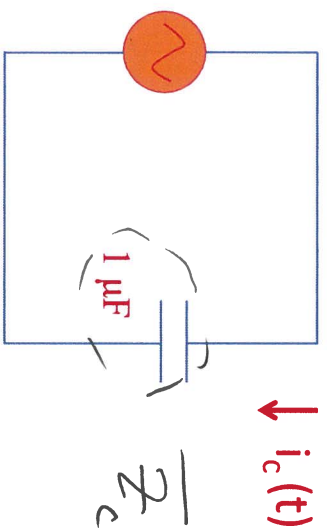
$$V_s(t) = 100 \cos(40t + 30^\circ) \text{ volts}$$



$$\underline{V}_s = 100 \angle 30^\circ$$

$$\underline{I}_c = \frac{\underline{V}_s}{\underline{Z}_c} = \frac{100 \angle 30^\circ}{25,000 \angle -90^\circ}$$

$$= \frac{1}{250} \angle 120^\circ \text{ A} \quad [5]$$

$$\underline{Z}_c = \frac{1}{j\omega C} = \frac{1}{j(40)(1 \times 10^{-6})} = \frac{1}{j4 \times 10^{-5}} = -j25,000 \angle -90^\circ \Omega \quad [3]$$

$$\Rightarrow i_c(t) = \frac{1}{250} \cos(40t + 120^\circ) \text{ A} \quad [2]$$

Problem 5b: (10pts)


Find  $i_L(t)$ . Hint: convert the voltage source into a phasor, then find the current phasor for the inductor, then convert back to  $i_L(t)$ .

$$\omega = 10$$

[3]

$$V_s(t) = 60 \cos(10t + 45^\circ) \text{ volts}$$

$$\bar{V}_s = 60 \angle 45^\circ$$

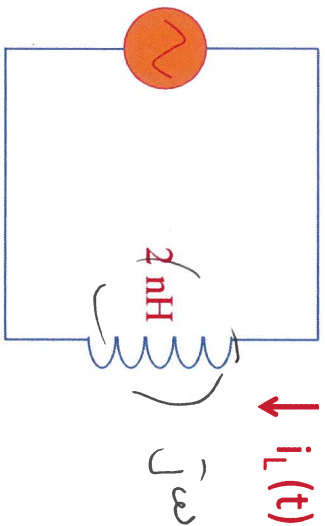

$$\begin{aligned} j\omega L &= j(10) \times 2 \times 10^{-3} \\ &= j 2 \times 10^{-2} \Omega \\ &= 2 \times 10^{-2} \angle 90^\circ \Omega \end{aligned}$$

$$I_L = \frac{\bar{V}_s}{Z_L} = \frac{60 \angle 45^\circ}{2 \times 10^{-2} \angle 90^\circ}$$

$$= 30 \times 10^2 \angle -45^\circ \text{ A}$$

[5]

$$\Rightarrow i_L(t) = 30 \times 10^2 \cos(10t - 45^\circ) \text{ A}$$

[2]