

# EECS/CSE 70A Network Analysis I

## Homework #6


Due on or before

**Thursday 6/7/2018 at 10:00AM**

**(You can submit your homework in any of the discussion sessions only on either Tuesday 6/5 or Thursday 6/7)**

Problem 1: (10 pts)


For the circuit shown below, find  $i(t)$ ,  $v_L(t)$ ,  $v_C(t)$  and  $v_R(t)$ .

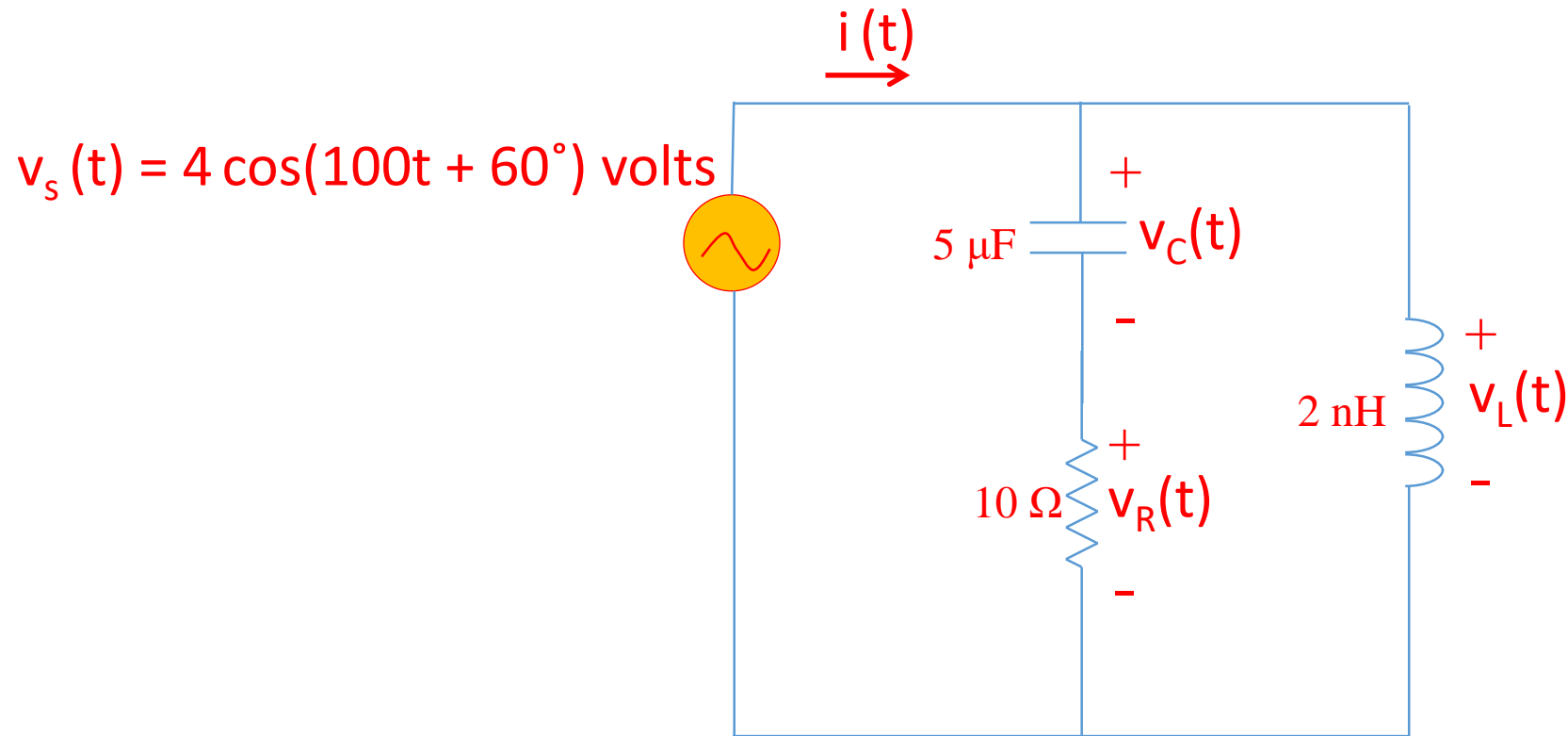

Problem 2: (10 pts)

Determine the type of the filter shown below based on  $C$ ,  $R_1$  and  $R_2$ .

Plot  $V_{\text{out}}(t)$  versus  $V_{\text{in}}(t)$  for  $\omega \rightarrow 0$  and  $\omega \rightarrow \infty$ .

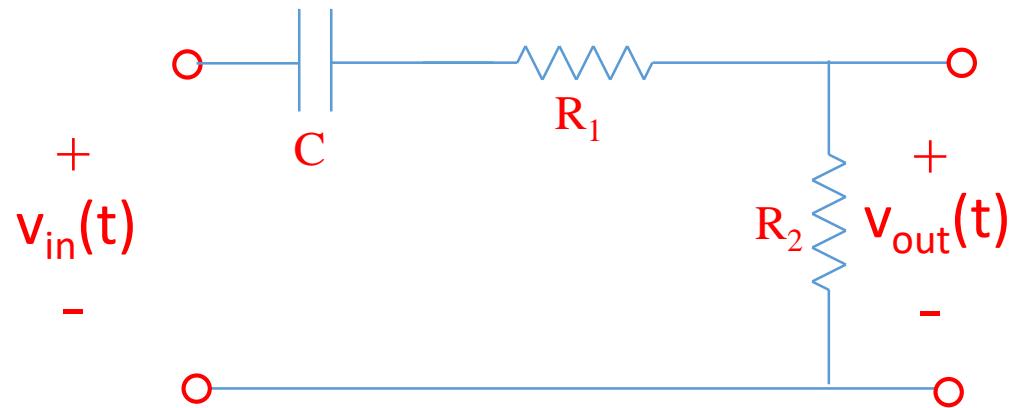


Problem 3a: (10 pts)

Find the transfer function  $H(\omega)$ ,  $|H(\omega)|$  and  $\angle H(\omega)$ .

Plot  $|H(\omega)|$  on linear-linear and log-log scales.

Plot  $\angle H(\omega)$  on linear-log scales.

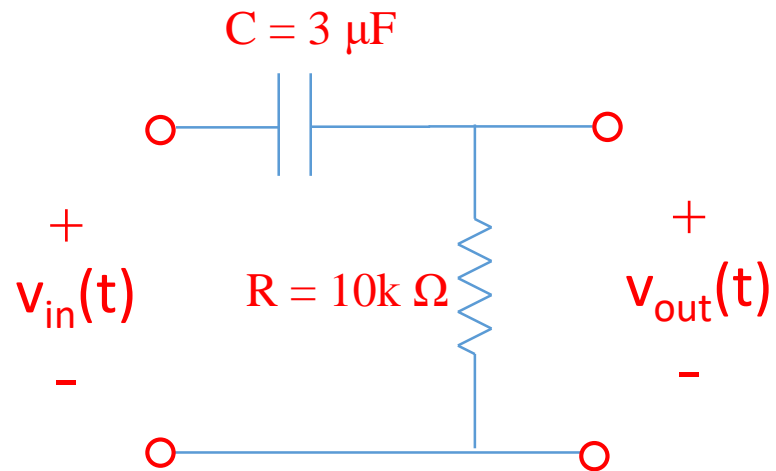


Problem 3b: (10 pts)

Find the transfer function  $H(\omega)$ ,  $|H(\omega)|$  and  $\angle H(\omega)$ .

Plot  $|H(\omega)|$  on linear-linear and log-log scales.

Plot  $\angle H(\omega)$  on linear-log scales.

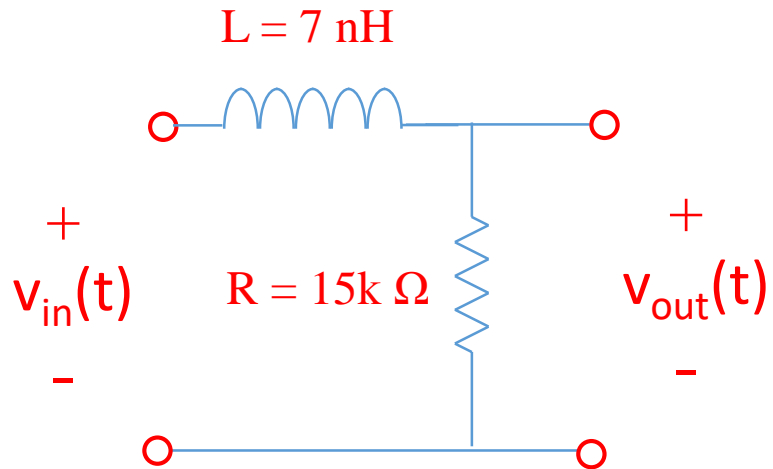


Problem 4: (10 pts)

Find the transfer function  $H(\omega)$ ,  $|H(\omega)|$  and  $\angle H(\omega)$ .

Plot  $|H(\omega)|$  on linear-linear and log-log scales.

Plot  $\angle H(\omega)$  on linear-log scales.

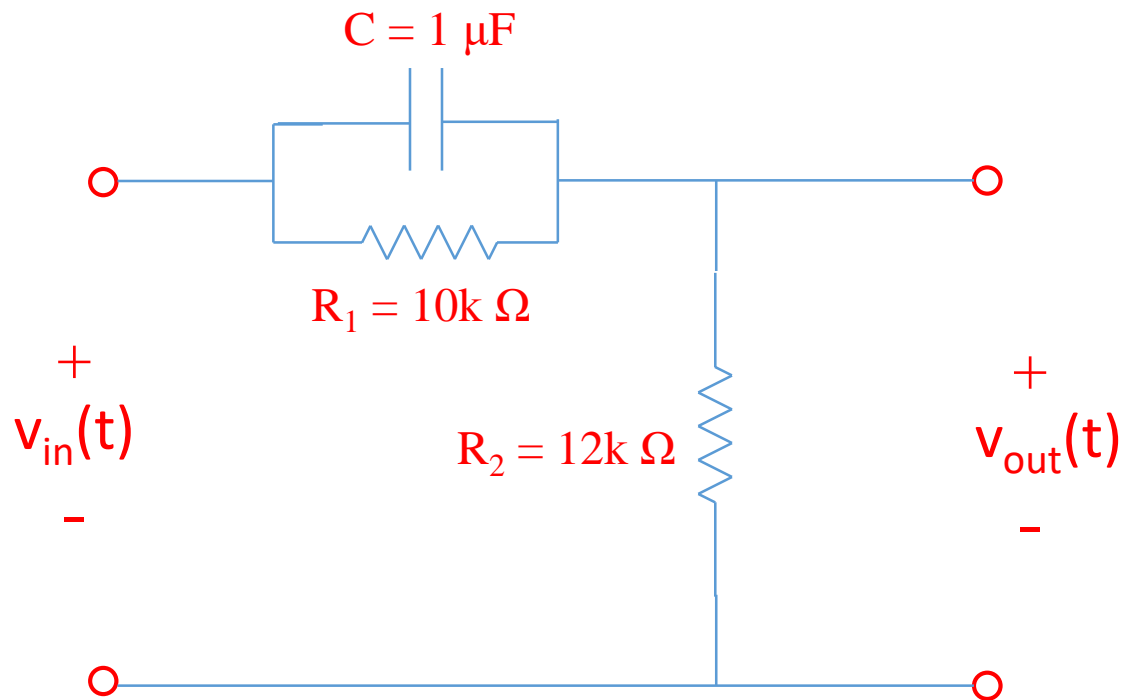


Problem 5: (10pts)

For  $f = 1, 10, 100, 1k, 10k,$  and  $100k$  Hz, find the output voltage as

$V_{out}(t) = A \cos(2\pi ft + \phi)$  where  $\phi$  is the phase if the input voltage is

$$V_{in}(t) = 10 \cos(2\pi ft + \pi/3)$$

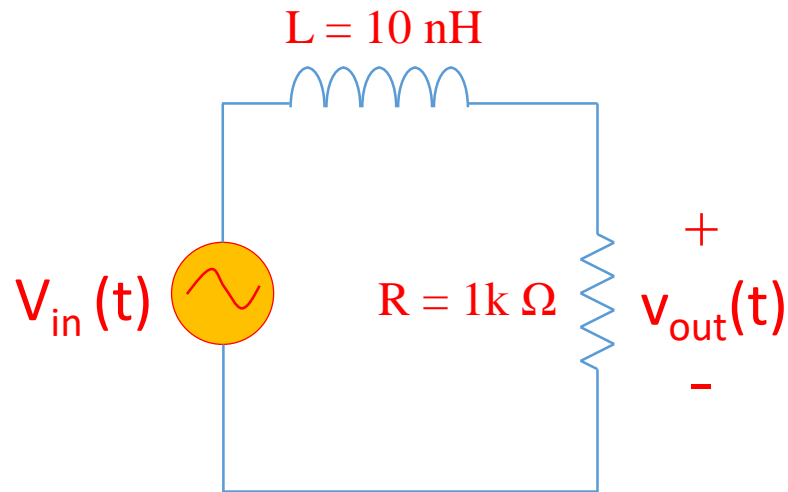


Problem 6: (10pts)

Find the output voltage as

$V_{\text{out}}(t) = A \cos(2\pi ft + \phi)$  where  $\phi$  is the phase if the input voltage is

$V_{\text{in}}(t) = 10 \sum_i \cos(2\pi f_i t + \pi/3)$ ,  $f_i = 1, 10, 100, 1\text{k}, 10\text{k}$ , and  $100\text{k}$  Hz

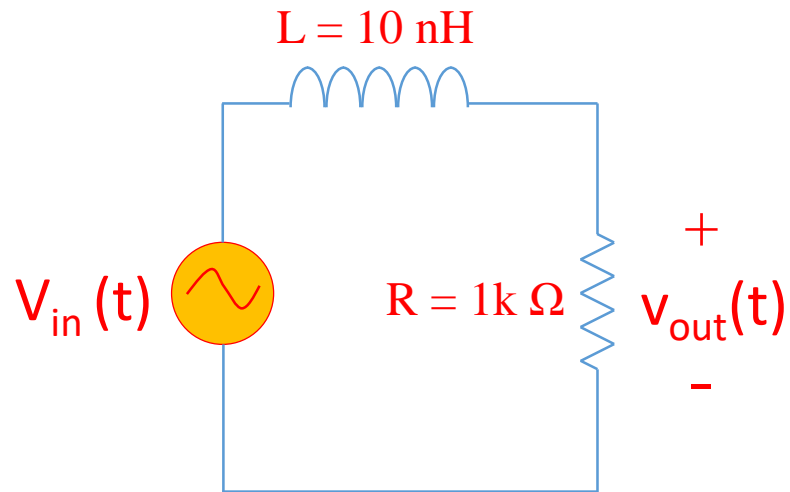



Problem 7: (10pts)

Sketch the Bode plot (magnitude only) for the following transfer function.

$$H(\omega) = 1/((1+j\omega\tau) \cdot (1+j\omega\tau))$$