

# EECS/CSE 70A Network Analysis I


## Homework #2

Due on or before

4/19/2018, Thursday 10 am

(You can submit your homework in any of the Tuesday  
Thursday discussions before or on 4/19/2018)

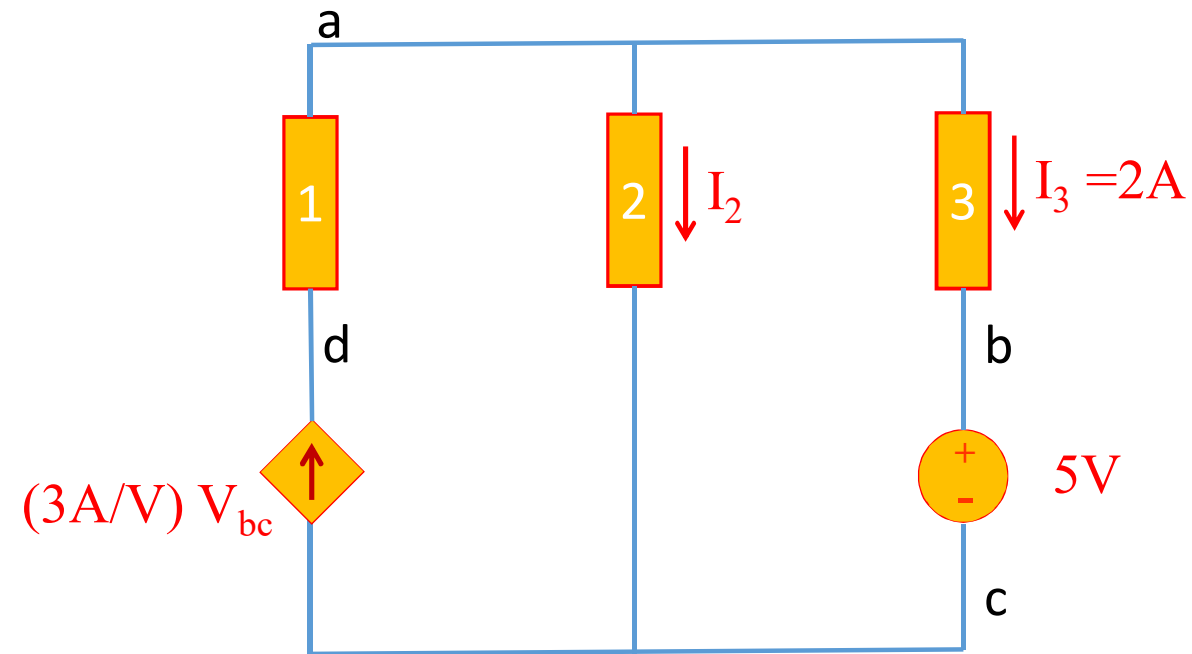Problem 1: (VCCS) Find  $I_2$ . 1.5 points



Solution:

$$V_{bc} = 5V$$

$$\text{VCCS current} = I_{\text{VCCS}} = (3A/V) V_{bc} = 15A$$


$$\text{KCL @ node a: } I_2 + I_3 = I_{\text{VCCS}}$$

$$\rightarrow I_2 = 13A \quad \boxed{0.5}$$

$$\boxed{0.5}$$

$$\boxed{0.5}$$

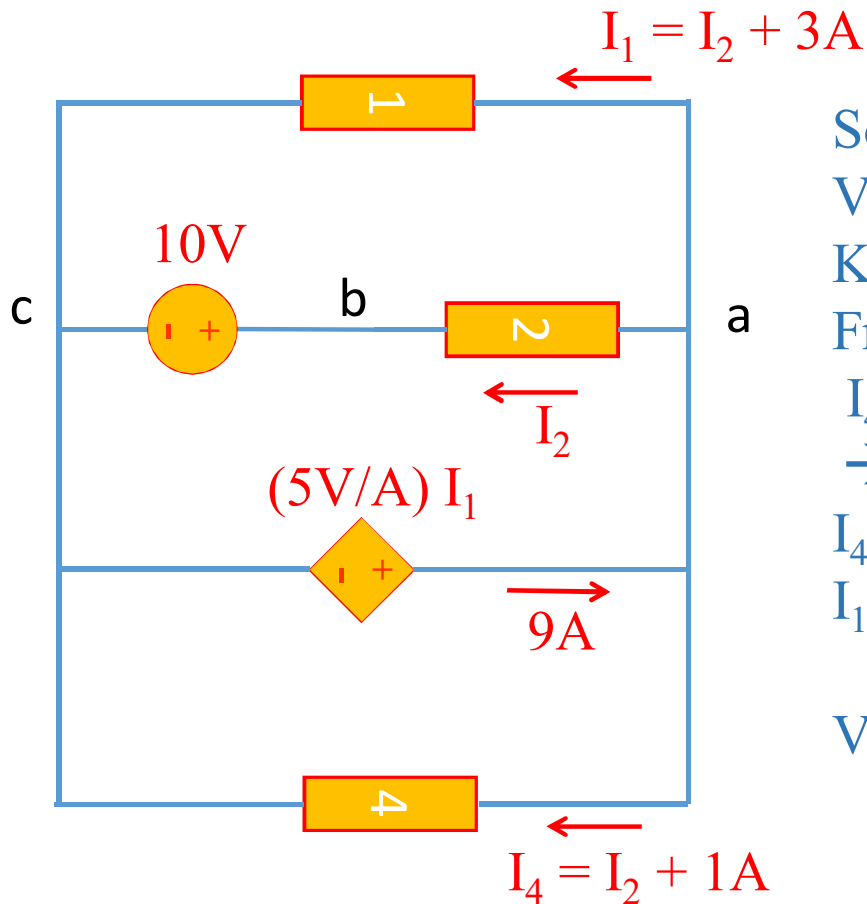Problem 2: (CCVS) Find  $I_2$ ,  $I_4$  and  $V_{ac}$  **3.5 points**



Solution:

$$V_{bc} = 10 \text{ V}$$

$$\text{KCL @ node a: } I_1 + I_2 - 9\text{A} + I_4 = 0 \quad \boxed{1}$$

From the question we know  $I_1 = I_2 + 3\text{A}$  and

$$I_4 = I_2 + 1\text{A}$$


$$\rightarrow (I_2 + 3\text{A}) + I_2 + (I_2 + 1\text{A}) - 9 = 0 \rightarrow I_2 = 5/3 \text{ A} = 1.66\text{A}$$

$$I_4 = I_2 + 1\text{A} = 2.66\text{A} \quad \boxed{0.5}$$

$$I_1 = I_2 + 3\text{A} = 4.66\text{A} \quad \boxed{0.5}$$

$$V_{ac} = 5\text{V/A} * I_1 = 23.3\text{V} \quad \boxed{0.5}$$

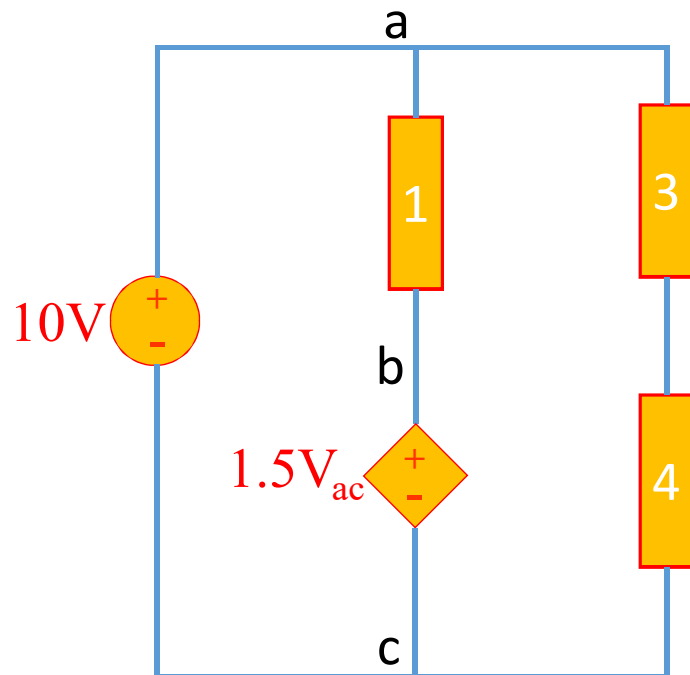Problem 3: (VCVS) Find  $V_{bc}$  and  $V_{ab}$ . 1 points





Solution:

$$V_{ac} = 10V \rightarrow V_{bc} = 1.5 \times V_{ac} = 15V \quad \text{0.5}$$

$$V_{ac} = V_{ab} + V_{bc} \rightarrow V_{ab} = V_{ac} - V_{bc} = -5V \quad \text{0.5}$$


Problem 4: Find  $R_{eq}$ . Please use the parallel sign “//” as discussed in class.

**2 points**

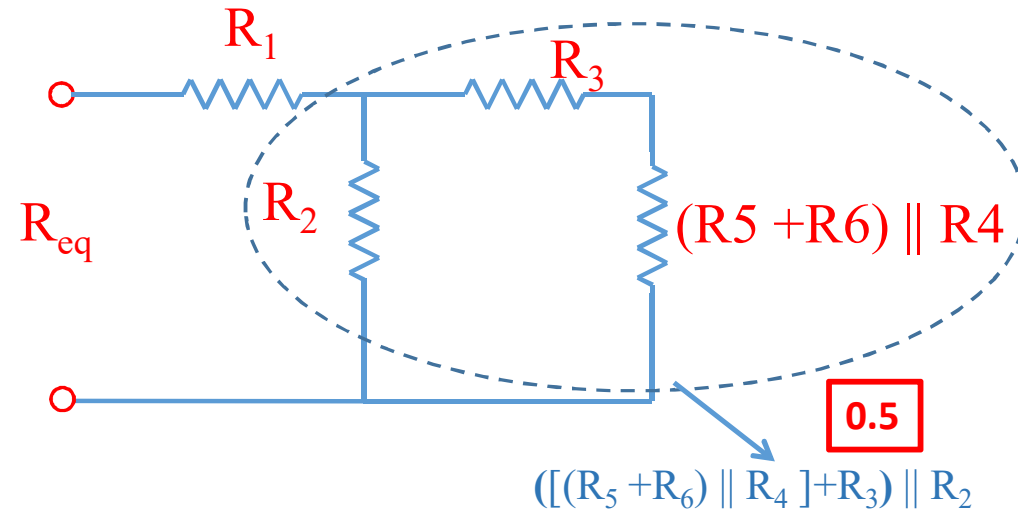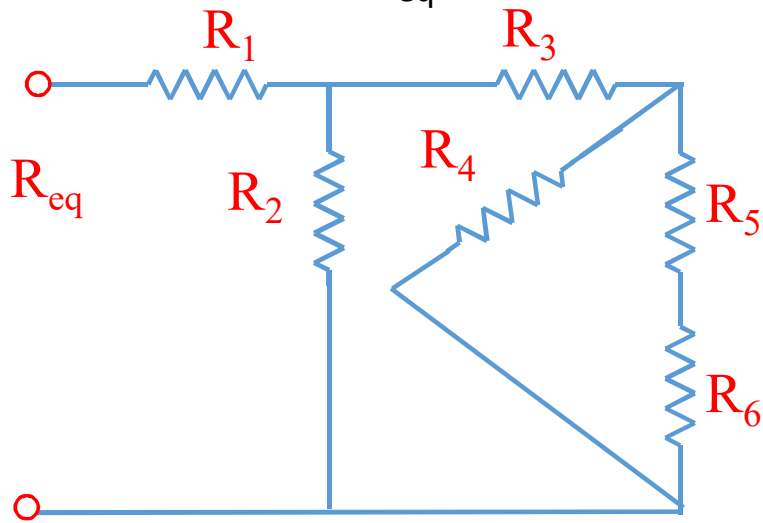

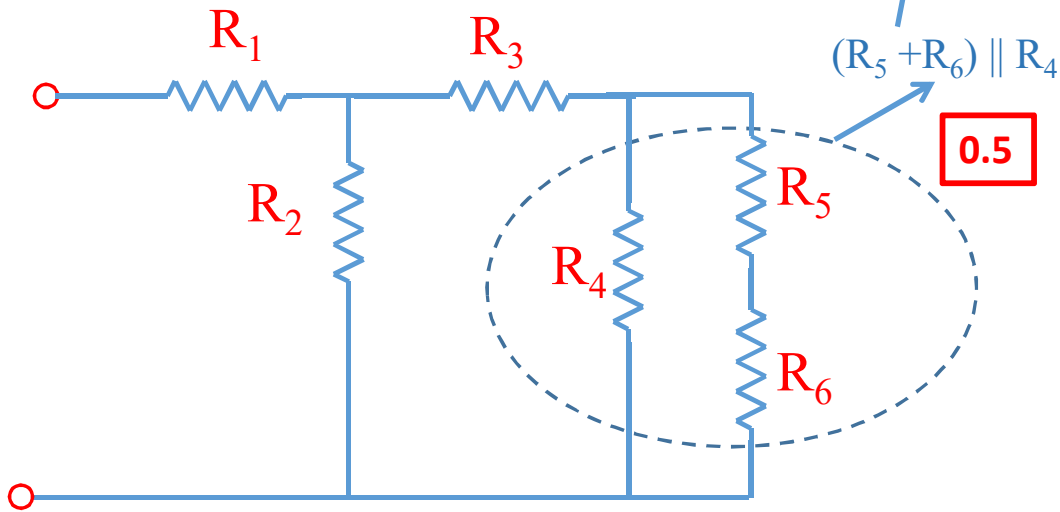**0.5**

$$[(R_5 + R_6) \parallel R_4] + R_3 \parallel R_2$$





**0.5**


$$R_{eq} = R_1 + [((R_5 + R_6) \parallel R_4) + R_3 \parallel R_2]$$

**1**

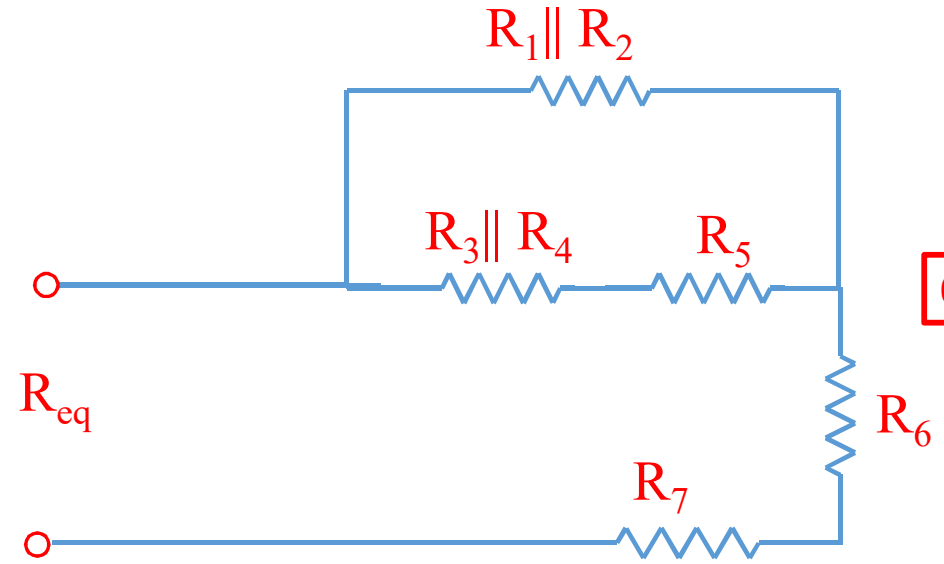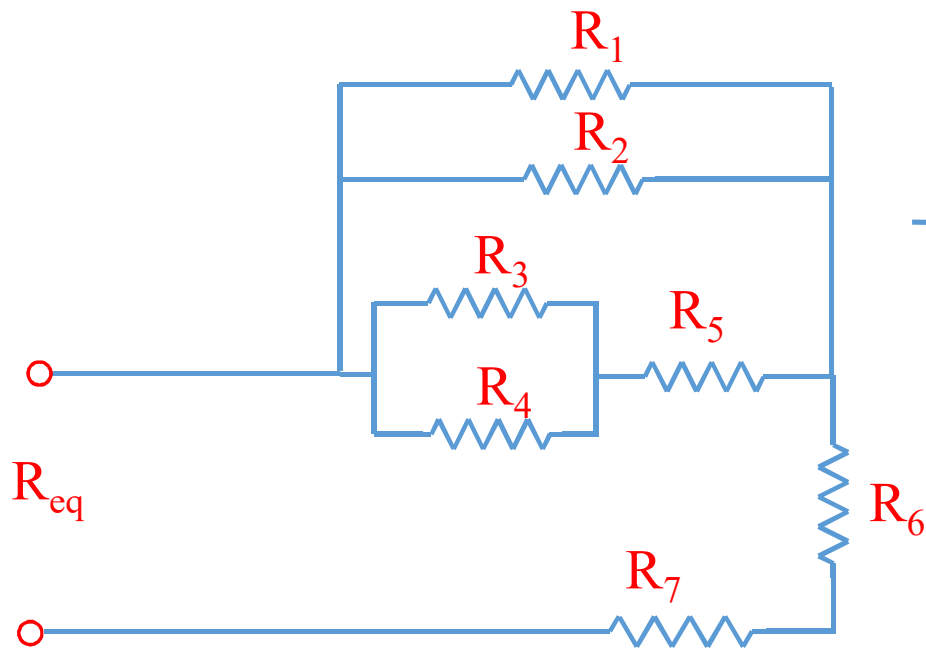Problem 5: Find  $R_{eq}$ . Please use the parallel sign “//” as discussed in class. 2 points



0.5

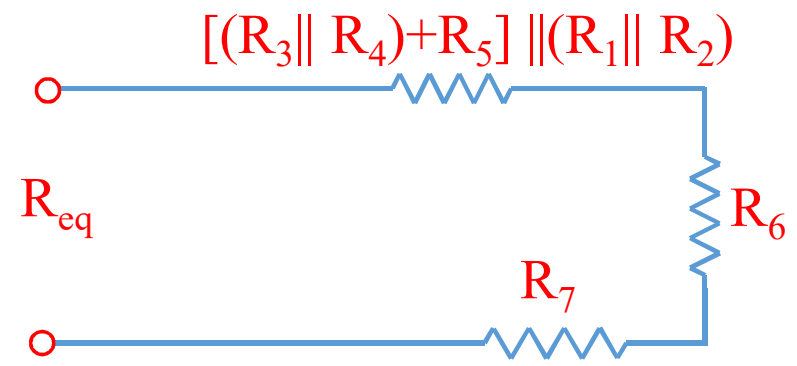


0.5

$$R_{eq} = \left( \left[ (R_3 \parallel R_4) + R_5 \right] \parallel (R_1 \parallel R_2) \right) + R_6 + R_7$$



1

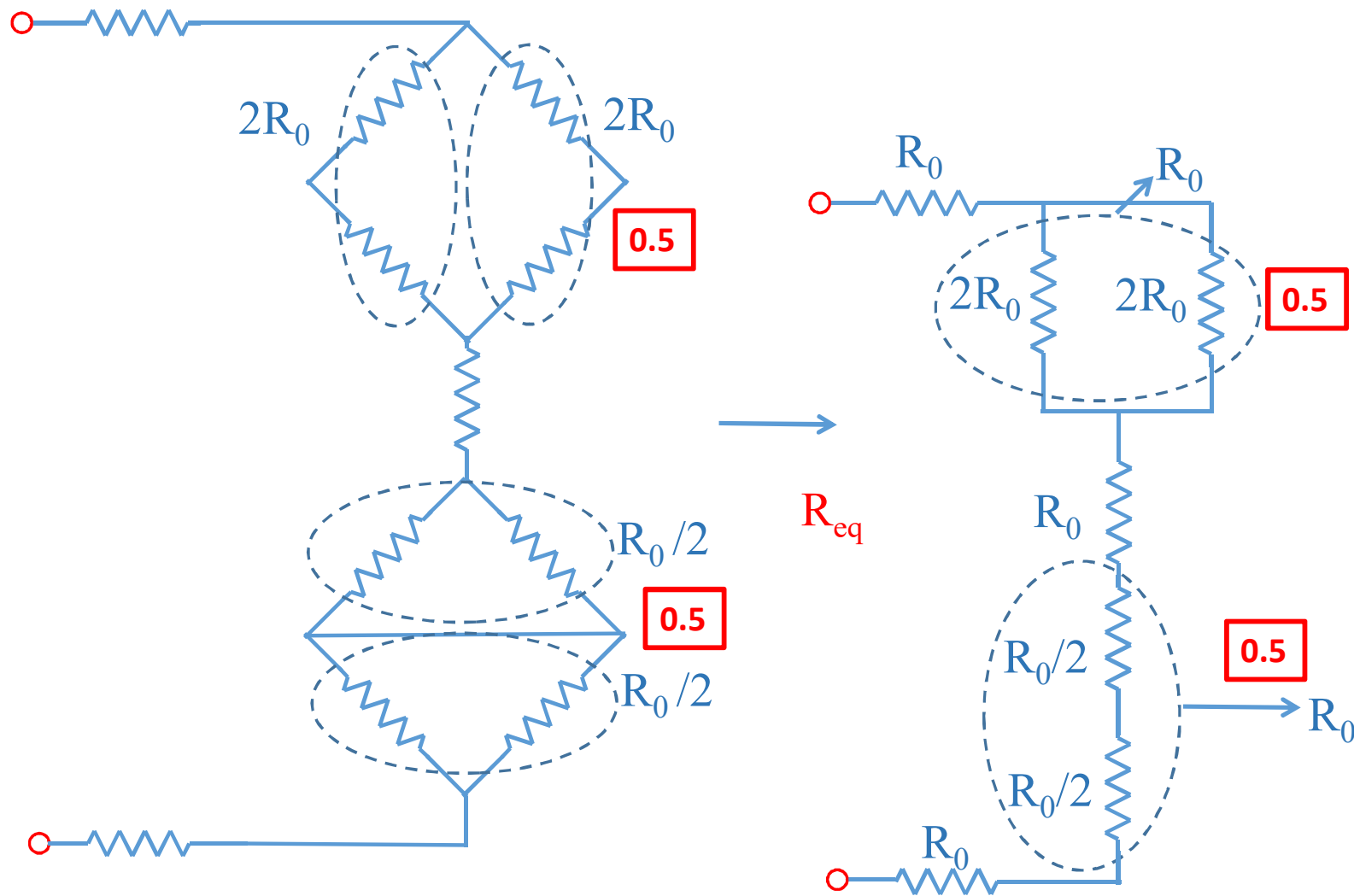Problem 6: All of the resistors below are  $R_0 \Omega$ . Find  $R_{eq}$ . 2.5 points



$$R_{eq} = 5R_0$$
0.5

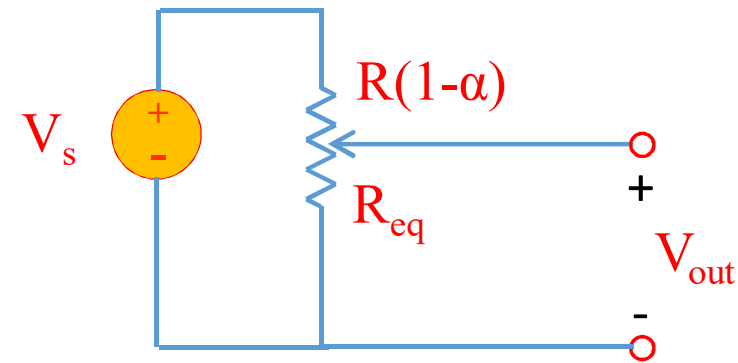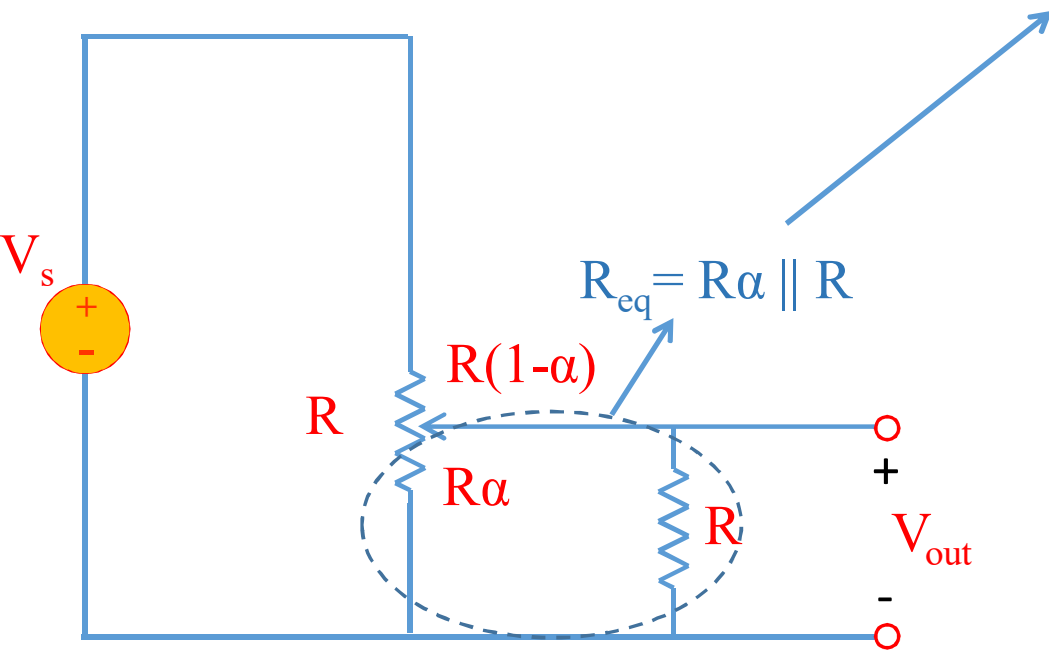Problem 7: (Potentiometer) In the circuit below, the wiper divides the potentiometer resistance  $R$  between two resistances  $R(1-\alpha)$  and  $R\alpha$  where  $0 < \alpha < 1$ .  $\alpha$  is a parameter modeling the wiper's position. Find the value of voltage  $V_{out}$  in terms of  $V_s$  if the value of  $\alpha$  is  $\frac{1}{2}$ . **3 points**



$$I = V_s / (R_{eq} + R(1-\alpha)) \quad \boxed{0.5}$$

$$V_{out} = R_{eq} \times I = \frac{R_{eq}}{R_{eq} + R(1-\alpha)} V_s \quad \boxed{0.5}$$

$$R_{eq} = R\alpha \parallel R = \frac{\alpha R * R}{\alpha R + R} = \frac{\alpha}{\alpha + 1} R \quad \boxed{1}$$

$$\rightarrow V_{out} = \frac{\frac{\alpha}{\alpha + 1}}{\frac{\alpha}{\alpha + 1} + (1-\alpha)} V_s = \frac{\alpha}{\alpha + 1 - \alpha^2} V_s \quad \boxed{0.5}$$

$$\alpha = 1/2 \rightarrow V_{out} = 0.4 V_s \quad \boxed{0.5}$$