

EECS/CSE 70A Network Analysis I




Homework #4

Due on or before

5/11/2018, Friday 5pm in the box in front of EH 4404





(You can submit your homework in any of the Tuesday or Thursday discussions before or on 5/11/2018)

Problem 1: Find C_{eq} (5pts).

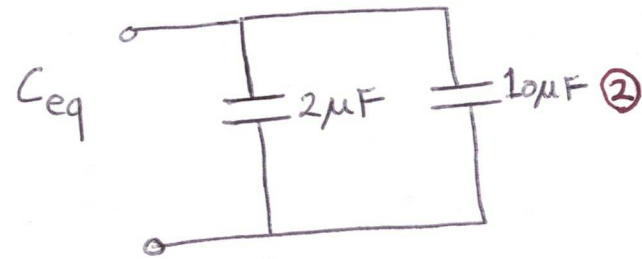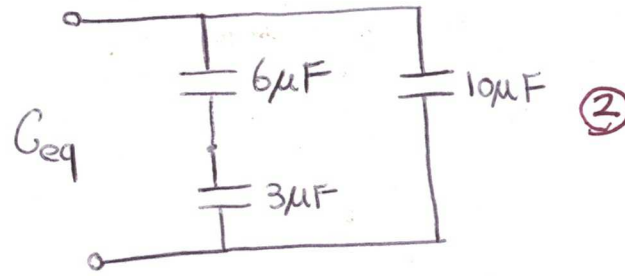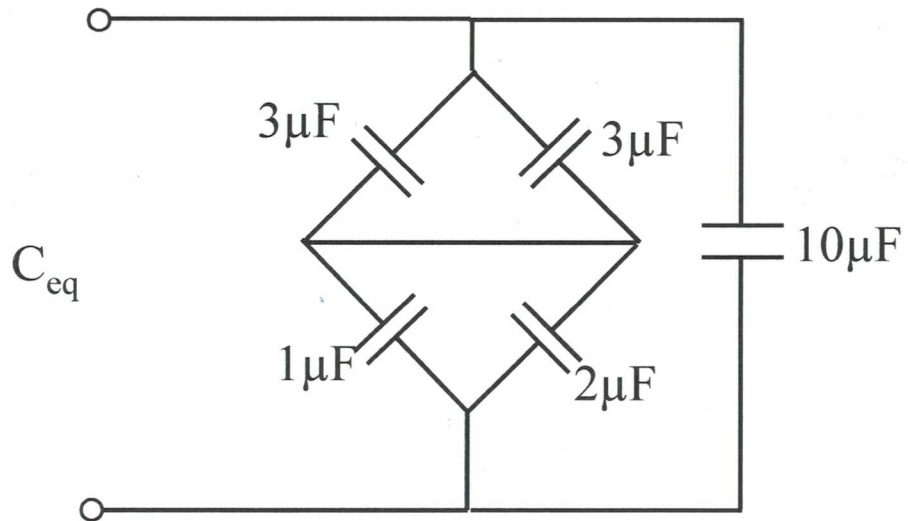

$$C_{eq} = 12\mu\text{F} \text{ (1)}$$

Problem 2: Find L_{eq} (5pts).

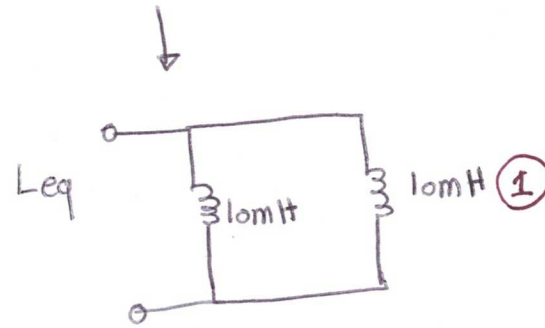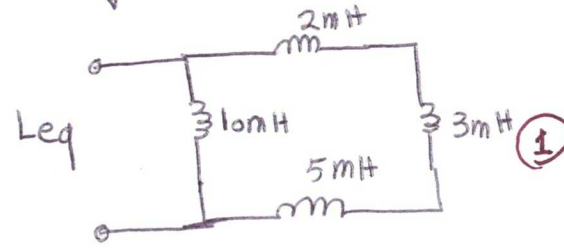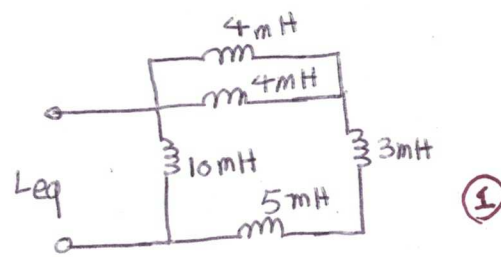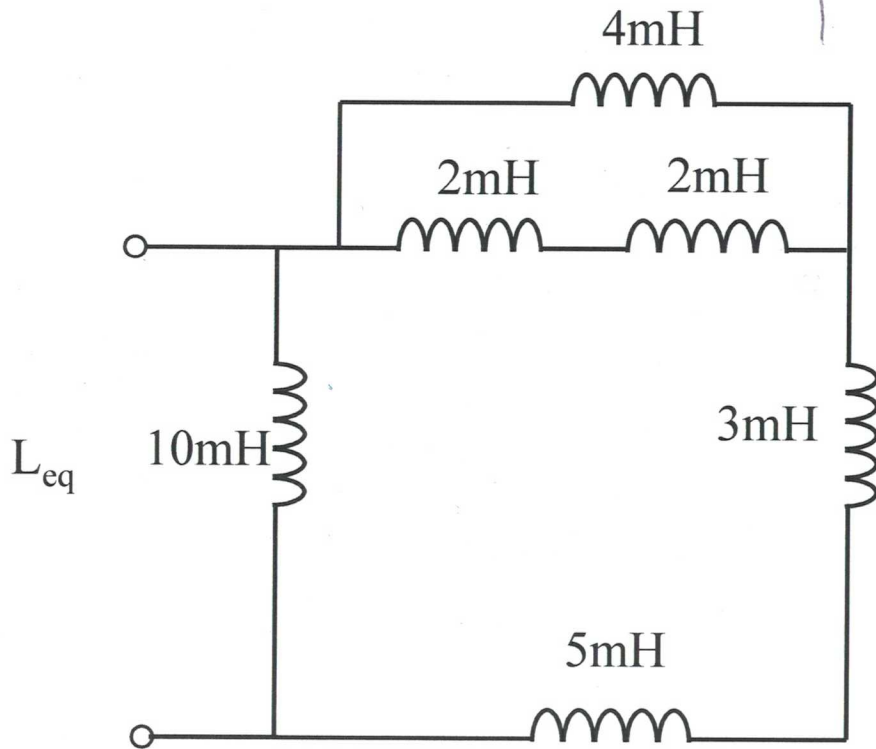



$$L_{eq} = 10\text{mH} \parallel 5\text{mH} = 5\text{mH} \quad (2)$$

Problem 3: The current flowing through the capacitor is given as a function of time in the following figure.

Plot the voltage of the capacitor, $V_C(t)$, and the charge of the capacitor, $q(t)$.

Assume the initial voltage of the capacitor is zero ($V_C(0)=0$).

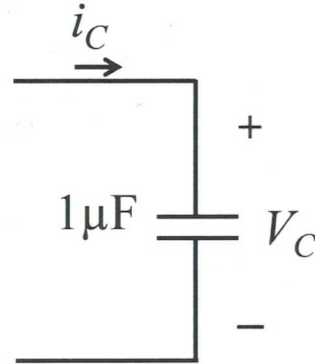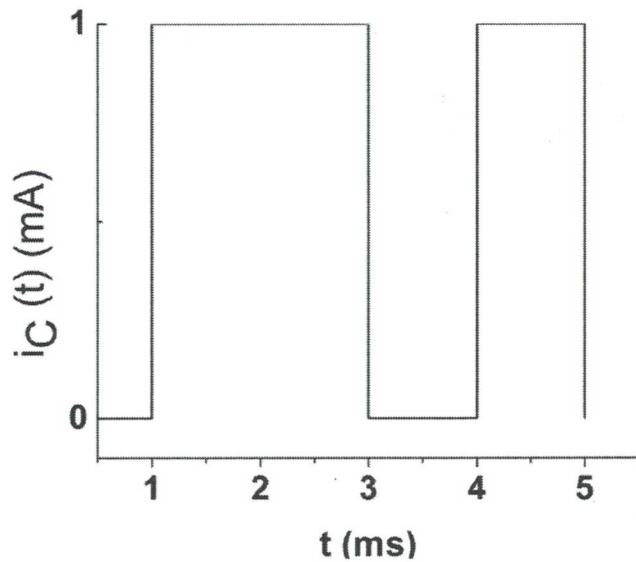
Mark the axis of your plots with numbers and units. (10pts)



$$V_C(t) = V_C(0) + \frac{1}{C} \int_0^t i_C(t') dt'$$


$V_C(t) =$	0	$0 \leq t < 1 \text{ ms}$
	$10^3(t - 10^{-3})$	$1 \text{ ms} \leq t < 3 \text{ ms}$
	2V	$3 \text{ ms} \leq t < 4 \text{ ms}$
	$2V + 10^3(t - 4 \times 10^{-3})$	$4 \text{ ms} \leq t < 5 \text{ ms}$
	3V	$t \geq 5 \text{ ms}$

⑤

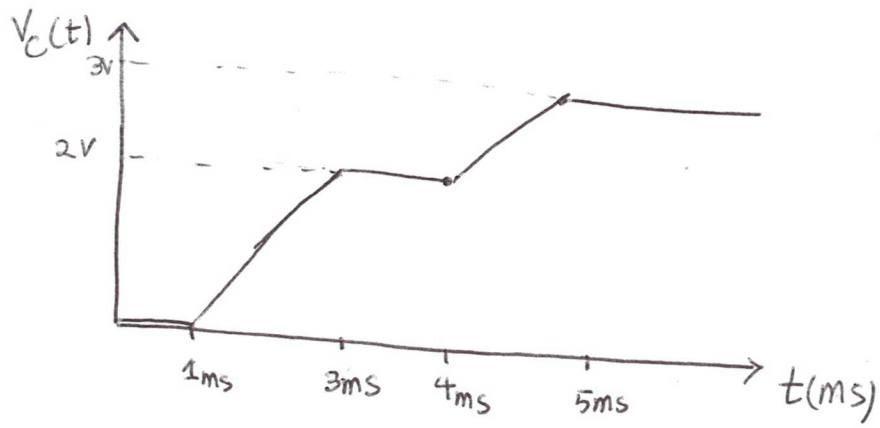

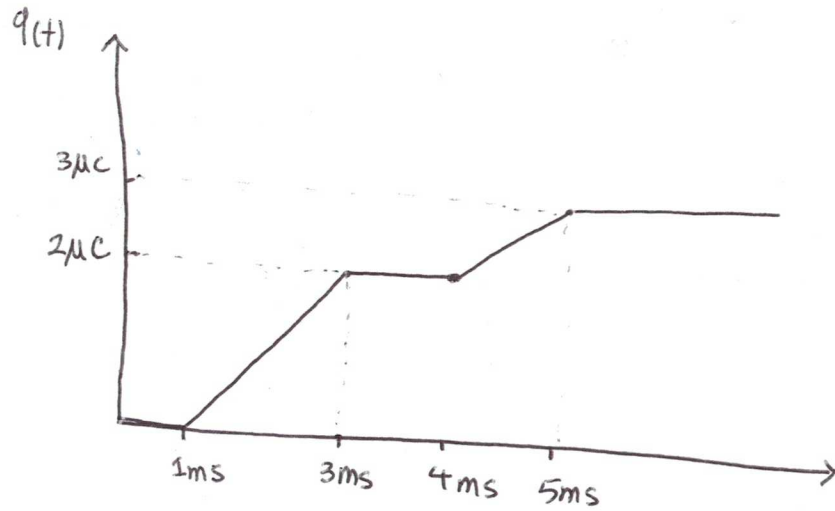(2)



$$q = C \cdot V_C \Rightarrow q(t) = 10^{-6} V_C(t) \quad (1)$$



(2)

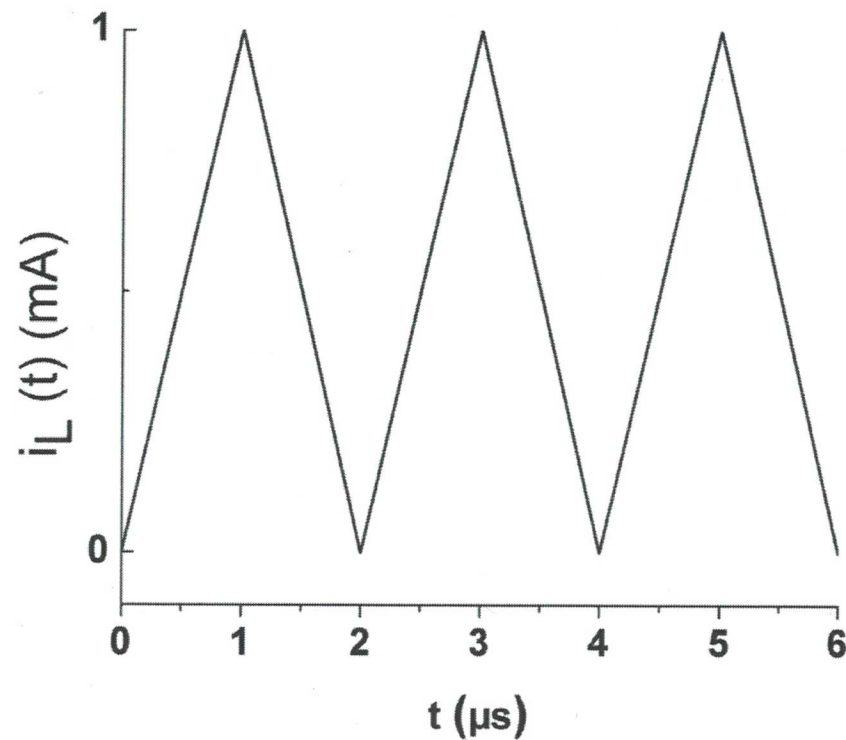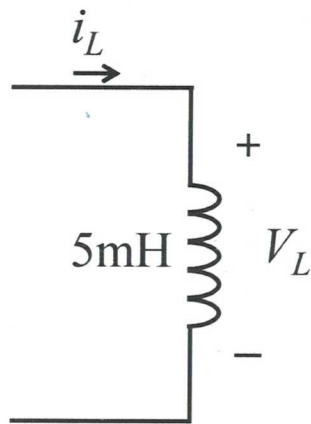Problem 4: The current flowing through the inductor is given as a function of time in the following figure. Plot the voltage of the inductor, $V_L(t)$.

Mark the axis of your plot with numbers and units. (5pts)




$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$


for $0 \leq t \leq 1\mu s$ $V_L(t) = 5 \times 10^{-3} \times \frac{1 \times 10^{-3} - 0}{1 \times 10^{-6}} = 5V$ (1)

for $1\mu s \leq t < 2\mu s$ $V_L(t) = 5 \times 10^{-3} \times \frac{0 - 1 \times 10^{-3}}{1 \times 10^{-6}} = -5V$ (1)

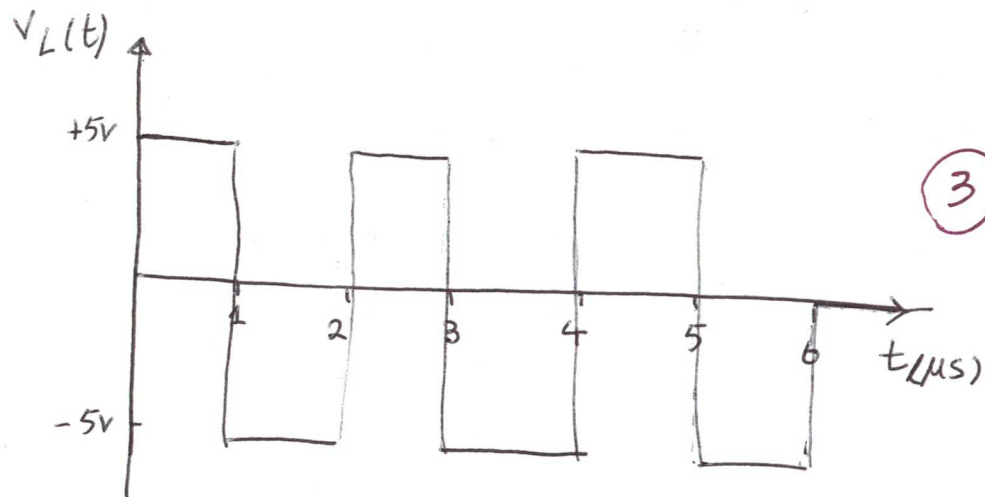and then this repeats up to $t = 6\mu s$. So we have:




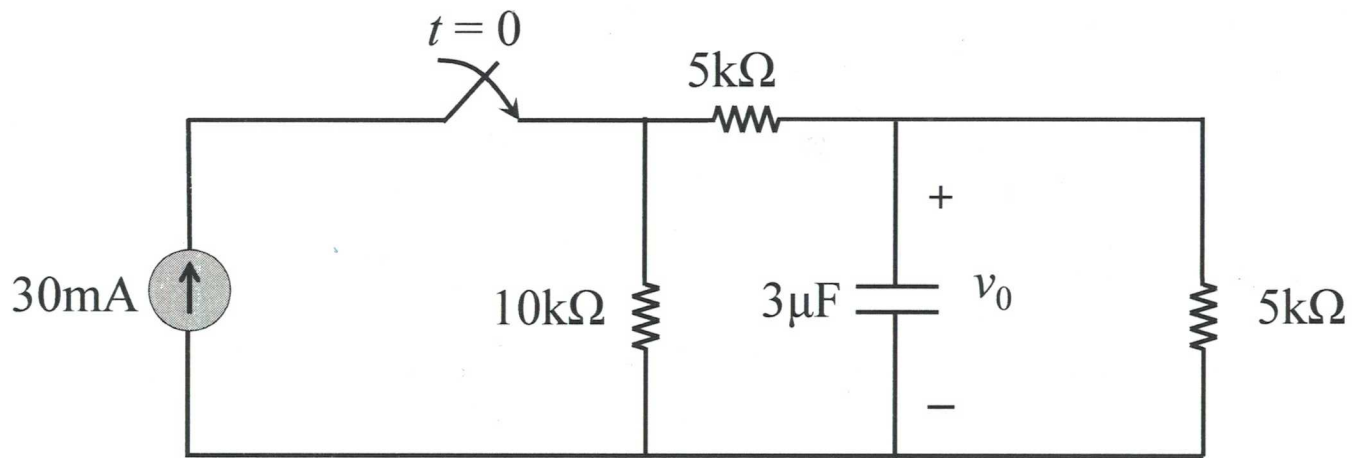Problem 5: (RC circuit) In the circuit below the switch closes at $t=0$. Write the expression for the voltage v_0 for $t>0$. Please clearly show the time constant calculation, initial and steady state voltage across the $3\mu\text{F}$ capacitor (35pts.)




before $t < 0$ $v_c = 0 \Rightarrow v_0(0) = 0$ (10)

$t > 0$

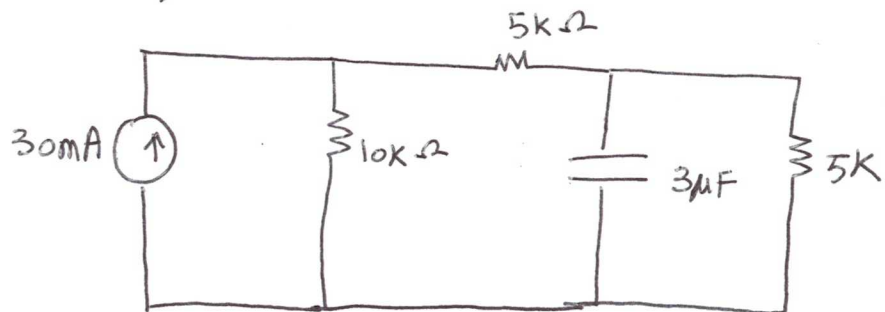


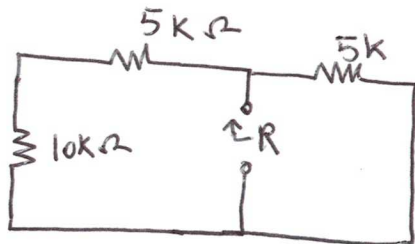to find time constant $\tau = RC$, we need to find the Resistance seen from the terminals of capacitor while canceling independent voltage and current sources. (make independent voltage source wire, make independent current source open)



$$R = 15k \parallel 5k = 3.75k \Omega \Rightarrow \tau = RC = 11.25 \text{ ms}$$

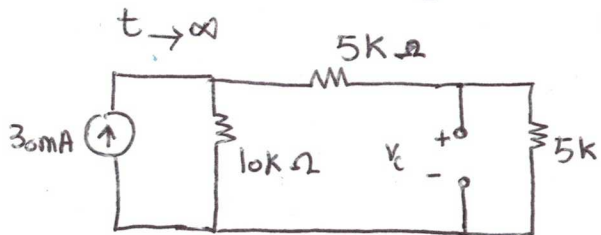To find $V_C(\infty)$ (steady state value), we replace capacitor with open circuit




$$V_C(\infty) = 30 \text{ mA} \times \frac{1}{2} \times 5k \Omega = 75 \text{ V}$$


Finally we have $V_C(t) = V_C(\infty) + (V_C(0) - V_C(\infty)) e^{-\frac{t}{\tau}} \Rightarrow$

$$V_C(t) = 75 \left(1 - e^{-\frac{t}{11.25 \times 10^{-3}}} \right) = V_0(t)$$

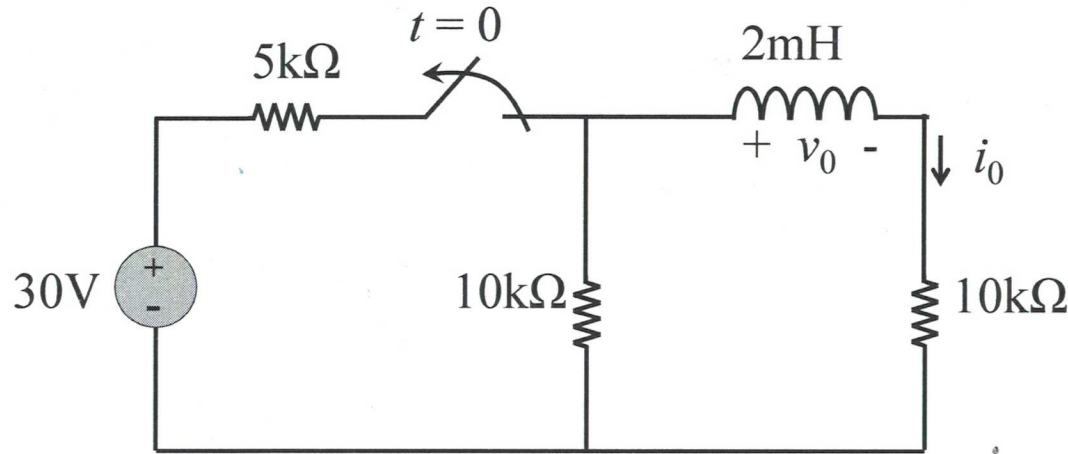Problem 6: (RL circuit) In the circuit below the switch opens at $t=0$. Write the expressions first for the current i_0 and then the voltage v_0 for $t>0$. Please clearly show the time constant calculation, initial and steady state current through the inductor. (40pts.)



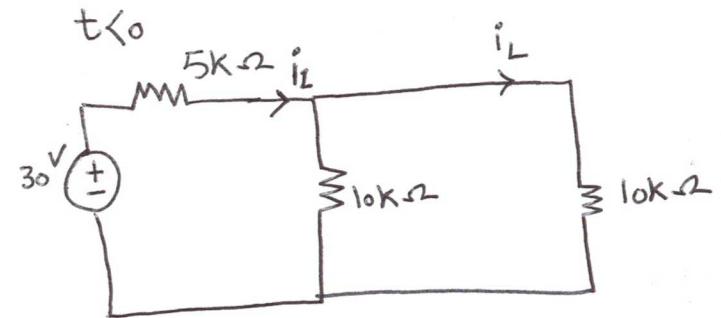@ $t < 0$ the switch was closed and the inductor has reached steady state (so it acts like a short circuit)




$$i_1 = \frac{30V}{(5k\Omega + 10k\Omega \parallel 10k\Omega)} = 3mA$$

Current division formula $i_L = \frac{10k}{10k + 10k} \cdot i_1 = 1.5mA$

so we have $i_L(0) = 1.5mA$ (10)

To find time constant we need to find the resistance seen from the inductor while all independent sources are canceled.


$t > 0$

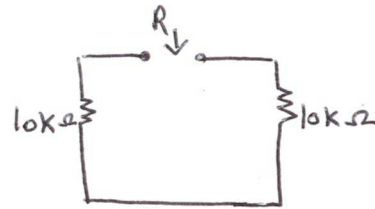

$$R = 10k\Omega + 10k\Omega = 20k\Omega$$

$$\tau = \frac{L}{R} = \frac{2mH}{20k\Omega} = 10^{-7} s = 0.1\mu s \quad (10)$$

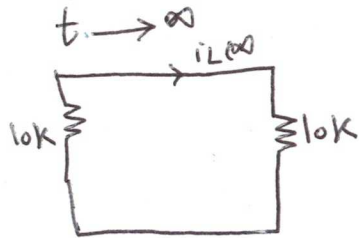for steady state value $i_L(\infty)$, we replace the inductor with wire or short circuit



since there is no source in the circuit, all the values are zero @ $t \rightarrow \infty$.

$$i_L(\infty) = 0 \quad (5)$$

Finally $i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{t}{\tau}} \rightarrow i_L(t) = 1.5 e^{-\frac{t}{10^{-7}}} [mA] \quad (10)$

$$V_L(t) = L \frac{di_L}{dt} = 1.5 \times 10^{-3} \times \left(-\frac{1}{10^{-7}}\right) e^{-\frac{t}{10^{-7}}} \times 2 \times 10^{-3} \Rightarrow$$

$$V_0 = V_L(t) = -30 e^{-\frac{t}{10^{-7}}} [V] \quad (5)$$