



Find $i(t)$, $V_C(t)$, $V_R(t)$ if

$$V_s = 3 \cos(\omega t + 45^\circ) \text{ V}$$

$$f = 2\ \text{MHz} \rightarrow \omega = 2\pi \times 2 \times 10^6$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 2\pi \times 2 \times 10^6 \times \frac{250}{3.14} \times 10^{-9}}$$

$$Z_C = \frac{1}{j \times 10^3 \times 10^6 \times 10^{-9}} = -j\ \Omega = 1 \angle -90^\circ$$

$$V_s(t) = 3 \cos(\omega t + 45^\circ)$$

$$\rightarrow \text{Phasor } V_s = 3 \angle 45^\circ = 3 e^{j\pi/4}$$

$$Z_{eq} = 2 + Z_C = 2 - j = \sqrt{5} \angle -26.56^\circ = 2.24 \angle -26.56^\circ$$

$$I = \frac{V_s}{Z_{eq}} = \frac{3 \angle 45^\circ}{2.24 \angle -26.56^\circ} = 1.34 \angle 71.56^\circ \text{ A}$$

$$\rightarrow i(t) = \text{Re}[I e^{j\omega t}] = 1.34 \cos(\omega t + 71.56^\circ)$$

$$V_C = I \times Z_C = 1.34 \angle 71.56^\circ \times 1 \angle -90^\circ = 1.34 \angle -18.44^\circ$$

$$V_C(t) = \text{Re}[V_C \cdot e^{j\omega t}] = 1.34 \cos(\omega t - 18.44^\circ)$$

$$V_R = I \times Z_R = 1.34 \angle 71.56^\circ \times 2 = 2.68 \angle 71.56^\circ$$

$$V_R(t) = \text{Re}[V_R \cdot e^{j\omega t}] = 2.68 \cos(\omega t + 71.56^\circ)$$